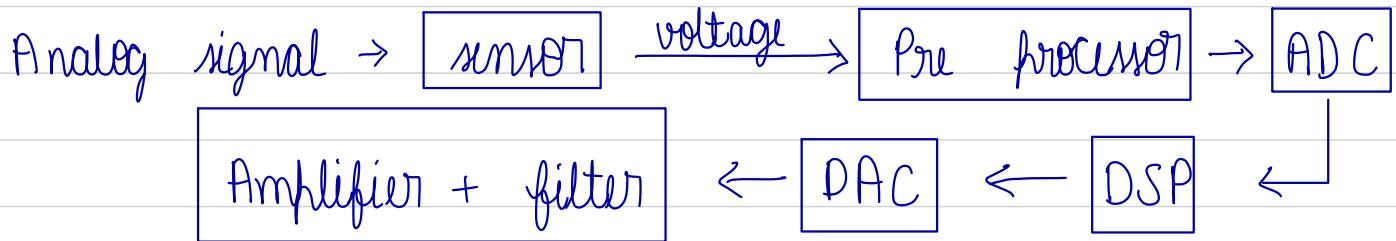


ANALOG

ELECTRONICS

- MANVITH PRABHU


Introduction:



$\text{ADC} \rightarrow$ Analog to digital convertor.
 $\text{DSP} \rightarrow$ Digital signal processing
 $\text{DAC} \rightarrow$ Digital to analog convertor.


AMPLIFIERS:

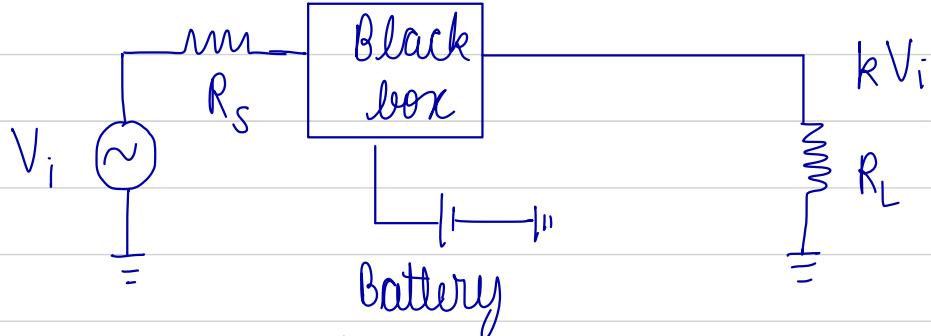- Amplifiers amplify the power of a signal.
- Transformers cannot increase the power of a signal, (as it is in a passive device) so it cannot be an amplifier.



$$\text{Power} = \frac{k^2 V_i^2}{R_L}$$

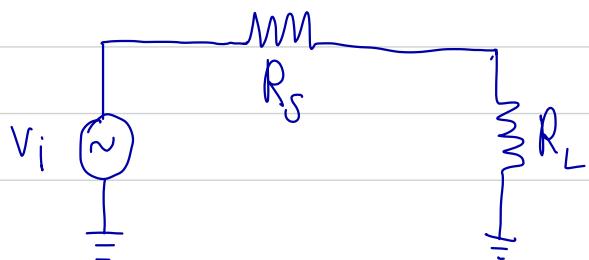According to maximum power transfer theorem: $P_{\max} = \frac{V_s^2}{8R_L}$ when $R_s = R_L$ for



$$\text{i.e } P = \left(\frac{V_i}{\sqrt{2} \times 2R_s} \right)^2 \times R_s$$


Linear and non linear networks

- A linear system obeys superposition principle
- Transfer functions, transforms and convolution integrals are used to study linear networks.
- Incremental linearity is used to study non linear networks.

Superposition principle: $x_1 \rightarrow y_1$, $x_2 \rightarrow y_2$
 $\Rightarrow \alpha x_1 + \beta x_2 \rightarrow \alpha y_1 + \beta y_2$

- Knowing impulse response of a linear system we can understand everything about the system. However it is not true for non linear system.

Eg for non linear system:

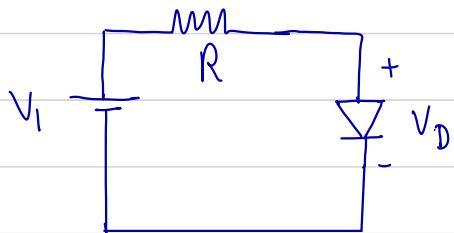

$$V_i = V_R + V_D \\ = IR + V_D$$


But $I = I_s e^{\left(\frac{V_D}{V_T} - 1\right)}$

$$V_T = \frac{kT}{q} = 25 \text{ mV at } T = 25^\circ\text{C}$$

when $V_D \gg V_T$, $I = I_s \exp \frac{V_D}{V_T}$

$$\Rightarrow V_D = V_T \ln \frac{I}{I_s}$$
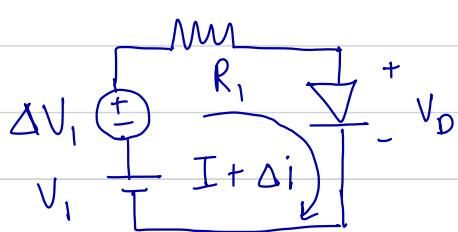
$$\text{So } V_i = IR + V_T \ln \frac{I}{I_s} \rightarrow 1$$



$$(V + \Delta V_1) = (I + \Delta i) R_1 + V_T \ln \left(\frac{I + \Delta i}{I_s} \right) \rightarrow ②$$

$$② - ① \Rightarrow \Delta V_1 = \Delta i R_1 + V_T \left[\ln \frac{I + \Delta i}{I_s} - \ln \frac{I}{I_s} \right]$$

$$\Delta V_1 = \Delta i R_1 + V_T [f(I + \Delta i) - f(I)]$$


where $f(I) = \ln \frac{I}{I_s}$

But $f(I + \Delta i) = f(I) + \left. \frac{df}{dx} \right|_{x=I} \times \Delta i$

$$\Delta V_1 = \Delta i R_1 + V_T \left[f(I) + \left. \frac{df}{dx} \right|_{x=I} \times \Delta i - f(I) \right]$$

$$= \Delta i R_1 + \frac{V_T \Delta i}{I}$$
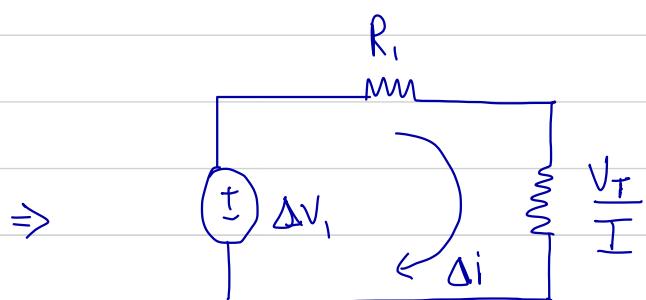
$$\Rightarrow \Delta i = \frac{\Delta V_1}{R_1 + \frac{V_T}{I}}$$



This technique is called linear increment technique.


This can be used for any non linear circuit.

$$V = f(I)$$

$$V + \Delta V = f(I + \Delta i)$$

$$= f(I) + f'(I) \cdot \Delta i$$
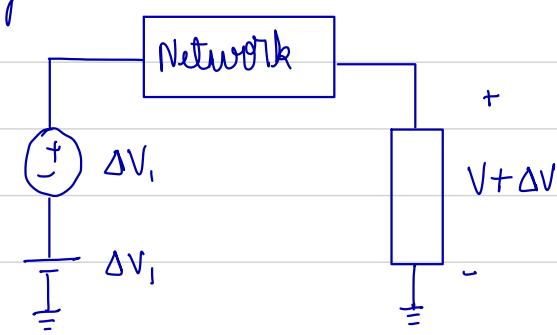
$$\Delta V = f'(I) \Delta i \Rightarrow f'(I) = \frac{\Delta V}{\Delta i} \neq \frac{V}{I}$$




I - Quiescent current

Δi - Incremental current


V - Quiescent voltage

ΔV - Incremental voltage



For diode :

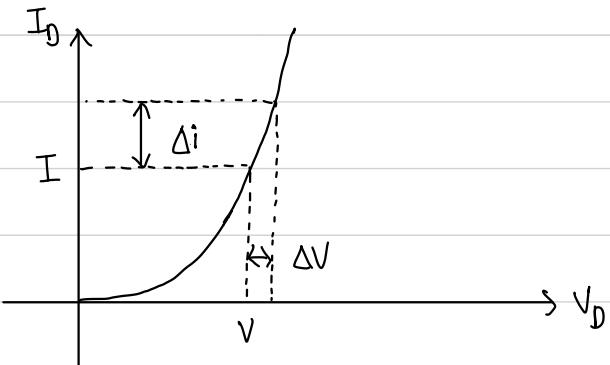

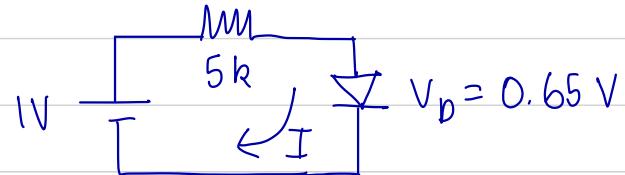Q1) what is the quiescent current in the loop.



Ans

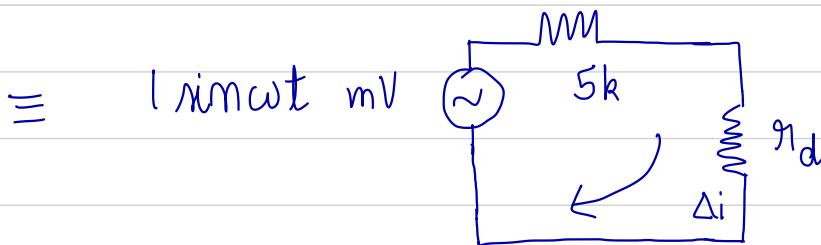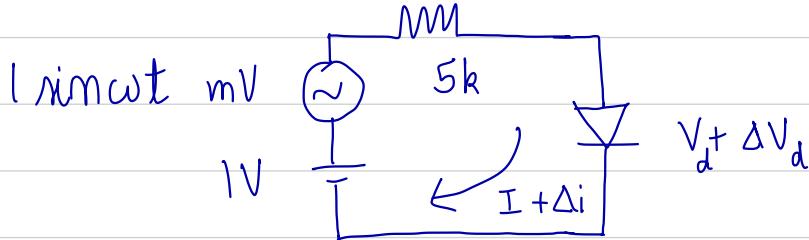

$$I = \frac{1 - 0.65}{5 \times 10^3} = 70 \mu\text{A}_{\parallel}$$

$$\eta_d = \frac{V_I}{I} = \frac{25 \text{ mV}}{70 \mu\text{A}} = 357 \Omega$$

$$\begin{aligned}\Delta V_d &= \frac{\eta_d}{\eta_d + 5k} \Delta V = \frac{357}{5357} \times \text{mimcwt mV} = 0.067 \text{ mimcwt mV}, \\ &= 67 \text{ mimcwt } \mu\text{V}_{\parallel}\end{aligned}$$

$$\therefore V_D + \Delta V_d = (0.65 + 67 \sin \omega t \times 10^{-6}) V_y$$


$$\Delta i = \frac{1 \sin \omega t}{357 + 5k} \text{ mV} = 0.18 \sin \omega t \mu A_{\parallel}$$

$$I + \Delta i = (70 + 0.18 \sin \omega t) \mu A_{\parallel}$$

- Steps:
- 1> Find the operating points (quiescent values)
 - 2> Draw the incremental circuit.
 - 3> Total node voltage / branch current

Quiescent voltage / current + Incremental voltage / current

TWO PORT NETWORKS

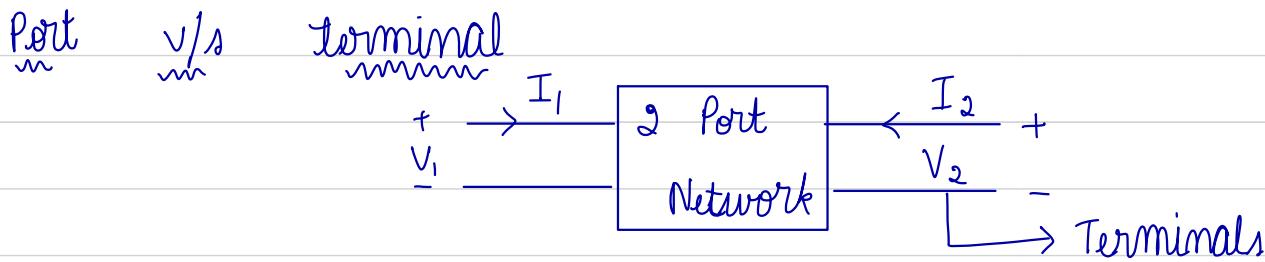


Dependent variables (response)	Independent variables (excitation)	Parameters
V_1, V_2	I_1, I_2	Z - Parameters
I_1, I_2	V_1, V_2	Y - Parameters
V_1, I_2	I_1, V_2	h - Parameters
I_1, V_2	V_1, I_2	g - Parameters
V_1, I_1	V_2, I_2	$ABCD$ or transmission
V_2, I_2	V_1, I_1	Inverse transmission or script $ABCD$

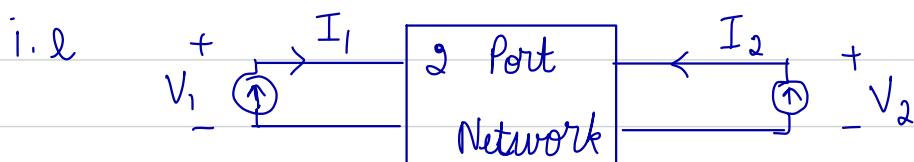i) Z Parameters:

$$\begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned}$$

$$\Rightarrow \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



$$Z_{11} = \left| \frac{V_1}{I_1} \right| \quad I_2 = 0$$

$$Z_{12} = \left| \frac{V_1}{I_2} \right| \quad I_1 = 0$$

$$Z_{21} = \left| \frac{V_2}{I_1} \right| \quad I_2 = 0$$

$$Z_{22} = \left| \frac{V_2}{I_2} \right| \quad I_1 = 0$$

$Z_{11}, Z_{22} \rightarrow$ Driving point impedances

$Z_{21} \rightarrow$ Forward transimpedance.


$Z_{12} \rightarrow$ Reverse transimpedance.

- Reciprocal network $\Rightarrow Z_{12} = Z_{21}$

NOTE: 2 port networks can be 3 terminal as well



Ex1

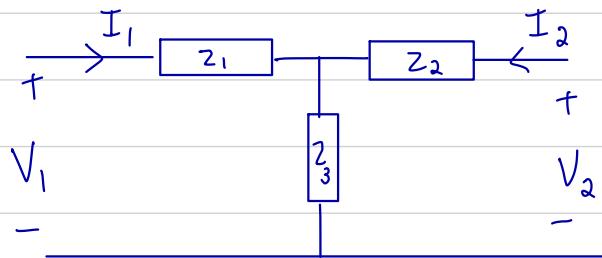

Find $Z_{11}, Z_{22}, Z_{21}, Z_{12}$

Ans


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_1 + Z_3$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_2 + Z_3$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = Z_3$$


$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_3$$

Ex2

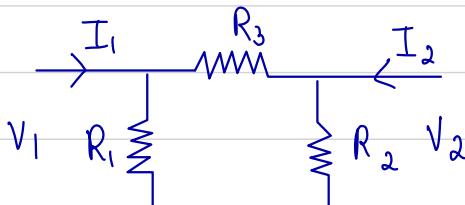

Find $Z_{11}, Z_{12}, Z_{21}, Z_{22}$

Ans The given circuit is equivalent to:

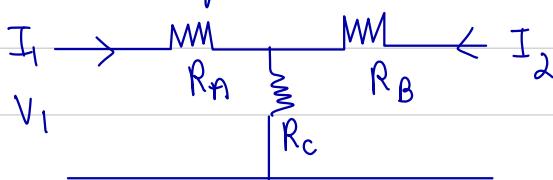

$$R_A = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$


⇒ From last question

$$Z_{11} = R_A + R_C = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$

$$Z_{12} = R_C = \frac{R_1 R_2}{R_1 + R_2 + R_3} = Z_{21}$$

$$Z_{22} = R_B + R_C = \frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3}$$

Ex 3

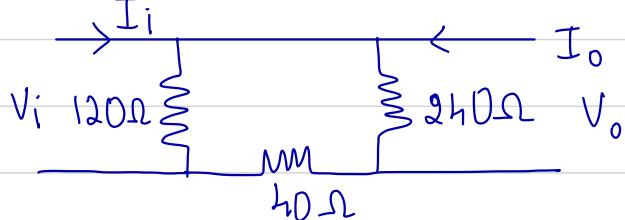


Find $Z_{11}, Z_{12}, Z_{21}, Z_{22}$

Ans

$$Z_{11} = \left| \frac{V_i}{I_i} \right| \quad | I_o = 0$$

→

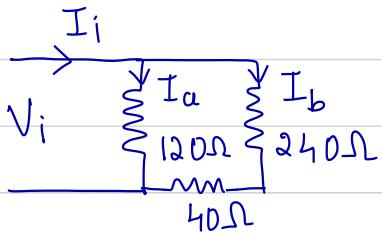


$$V_i = 120I_a$$

$$I_a = \frac{280}{400} \cdot I_i$$

$$V_i = 84 I_i \quad \Rightarrow \quad Z_{11} = 84 \Omega_{\parallel}$$

$$Z_{22} = \left| \frac{V_o}{I_o} \right| \quad | I_i = 0$$

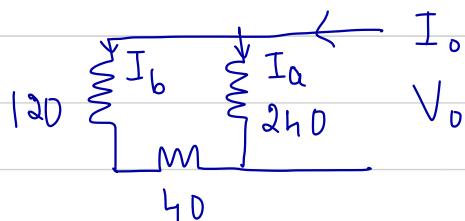

$$V_o = 240I_a$$

$$I_a = \frac{160}{400} = \frac{2}{5} I_o$$


$$V_o = 240 \times \frac{1}{10} I_o$$

$$V_o = 96 I_o$$

$$\therefore Z_{22} = 96 \Omega_{\parallel}$$

$$Z_{12} = \left. \frac{V_i}{I_o} \right|_{I_1=0}$$

\Rightarrow

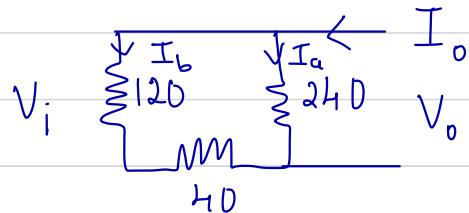

$$V_i = I_b \times 12\Omega$$

$$V_i = \frac{6}{10} \times 12\Omega I_o$$

$$I_b = \frac{240}{400} I_o = \frac{6}{10} I_o$$



$$V_i = 72 I_o \quad \Rightarrow \quad Z_{12} = 72 \Omega_{\parallel}$$

$$\text{III by } Z_{21} = 72 \Omega_{\parallel}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 84 & 72 \\ 72 & 96 \end{bmatrix}$$

4) Find $Z_{11}, Z_{12}, Z_{21}, Z_{22}$

Ans $Z_{11} = \left. \frac{V_i}{I_i} \right|_{I_o=0}$

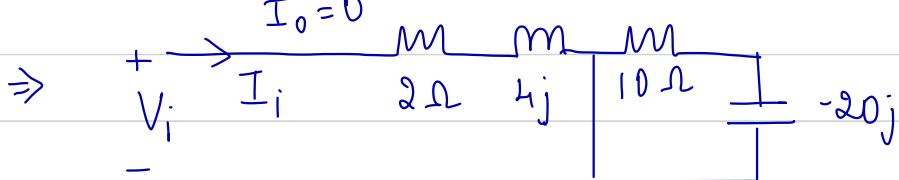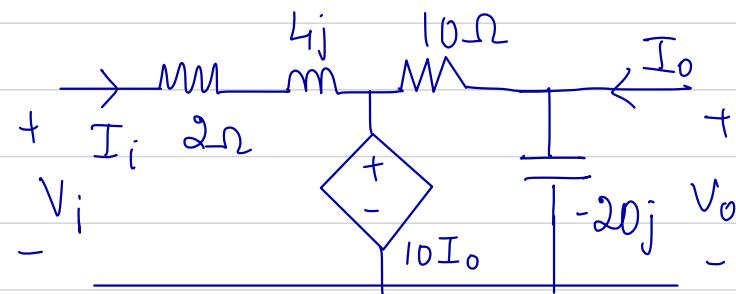


$$\frac{V_i}{I_i} = 2 + 4j$$

$$\Rightarrow Z_{11} = 2 + 4j$$

$$Z_{22} = \left. \frac{V_o}{I_o} \right|_{I_i=0}$$

\Rightarrow

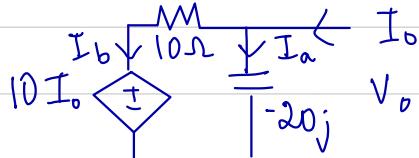


$$I_o = \frac{V_o}{-20j} + \frac{V_o - 10I_o}{10} = \frac{V_o}{10} \left(1 + \frac{j}{2} \right) - I_o$$

$$2I_o = V_o \left(\frac{2+j}{20} \right)$$

$$\frac{V_o}{I_o} = \frac{40}{(2+j)(2-j)} (2-j) = \frac{40}{5} (2-j) = 8 (2-j) = 16 - 8j \parallel$$

$$Z_{22} = 16 - 8j \parallel$$


$$Z_{12} = \left| \frac{V_i}{I_o} \right| \quad I_i = 0$$

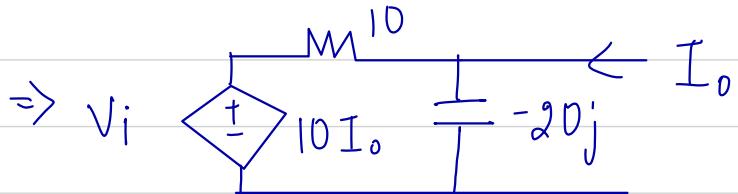

$$V_i = 10 I_o$$

$$\therefore Z_{12} = 10 \parallel$$

$$Z_{21} = \left| \frac{V_o}{I_i} \right| \quad I_o = 0$$

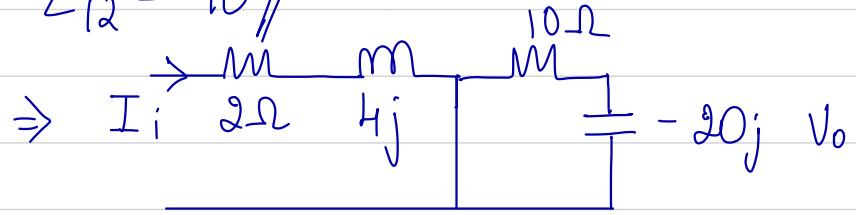

$V_o = 0$ (\because No current flows through $10-20j$)

$$\therefore Z_{21} = 0 \parallel$$

$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 2+4j & 10 \\ 0 & 16-8j \end{bmatrix} \parallel$$

Y parameters

$$\begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned}$$

$$\text{i.e. } \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



$$Y_{11} = \left| \frac{I_1}{V_1} \right| \quad V_2 = 0$$

$$Y_{12} = \left| \frac{I_1}{V_2} \right| \quad V_1 = 0$$

$$Y_{22} = \left| \frac{I_2}{V_2} \right| \quad V_1 = 0$$


$$Y_{21} = \left| \frac{I_2}{V_1} \right| \quad V_2 = 0$$

$y_{11}, y_{22} \rightarrow$ Driving point input, output admittances respectively
 $y_{12} \rightarrow$ Reverse Transadmittance
 $y_{21} \rightarrow$ Forward transadmittance

Ex1: Find out γ -parameters.

Ans


$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

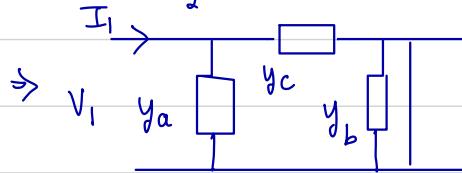

$$\therefore y_{11} = y_a + y_c$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -y_c$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -y_c$$

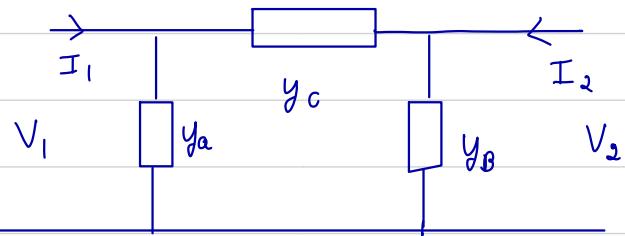

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = y_b + y_c$$

If y_a, y_b, y_c are replaced by R_1, R_2, R_3 (resistors)

$$y_{11} = \frac{1}{R_1} + \frac{1}{R_3}$$


$$y_{12} = y_{21} = -\frac{1}{R_3}$$

$$y_{22} = \frac{1}{R_2} + \frac{1}{R_3}$$

Ex2: Find out γ -parameters

Ans
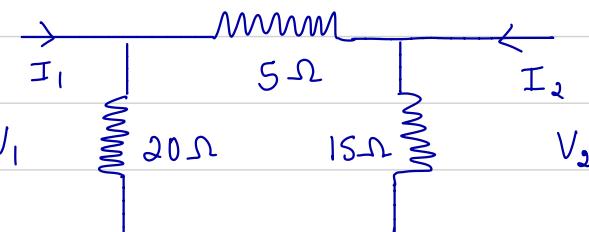
$$y_{11} = \frac{1}{20} + \frac{1}{5} = \frac{5+1}{25} = \frac{1}{5} S_{\parallel}$$



$$y_{12} = y_{21} = -\frac{1}{5} S_{\parallel}$$

$$y_{22} = \frac{1}{5} + \frac{1}{15} = \frac{4}{15} S_{\parallel}$$

3>

Ans

Find Z and y parameters

$$Z_{11} = \frac{V_1}{I_1} \quad \left| \begin{matrix} \\ I_2 = 0 \end{matrix} \right.$$

$$= \frac{5}{6} \Omega_{\parallel}$$

$$Z_{12} = \frac{V_1}{I_2} \quad \left| \begin{matrix} \\ I_1 = 0 \end{matrix} \right.$$

$$V_1 = I_b \times 1$$

$$I_b = \frac{I_2}{2} = V_1$$

$$\therefore Z_{12} = 0.5 \Omega_{\parallel}$$

$$Z_{22} = \frac{V_2}{I_2} \quad \left| \begin{matrix} \\ I_1 = 0 \end{matrix} \right.$$

$$V_2 = I_2 \times 2.5$$

$$\therefore Z_{22} = 2.5 \Omega_{\parallel}$$


$$Z_{21} = \frac{V_2}{I_1} \quad \left| \begin{matrix} \\ I_2 = 0 \end{matrix} \right.$$

$$V_2 = I_d \times 3$$

$$I_d = \frac{1}{6} \times I_1$$


$$\therefore Z_{21} = 0.5 \Omega_{\parallel}$$
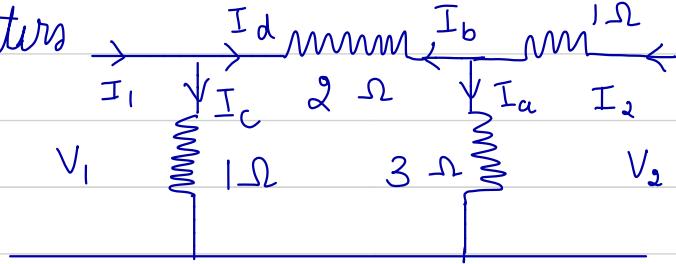
$$Z \text{ parameters} = \left[\begin{matrix} 5/6 & 0.5 \\ 0.5 & 2.5 \end{matrix} \right]_{\parallel}$$



$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

\Rightarrow

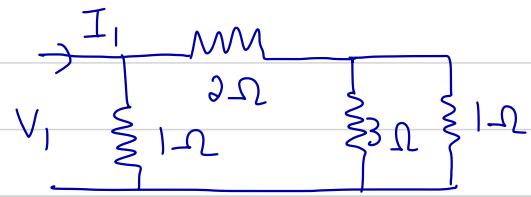


$$1 \parallel (2 + (3 \parallel 1))$$

$$(3 \parallel 1) = \frac{3}{5} \Omega$$

$$1 \parallel \frac{1}{5} = \frac{1}{15} = R$$

$$\therefore Y_{11} = (15 \parallel)_{11} S_{\parallel}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

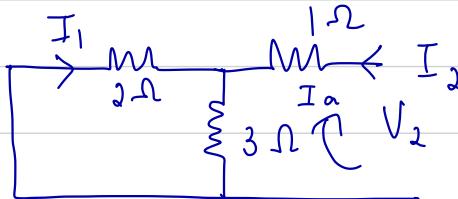

$$-2I_1 - 3(I_1 - I_a) = 0 \Rightarrow 5I_1 = 3I_a$$


$$-3(I_a - I_1) - I_a = V_2 \Rightarrow -4\left(\frac{5}{3}\right)I_1 + 3I_1 = V_2$$

$$V_2 = \frac{-11}{3}I_1 \Rightarrow \frac{V_2}{I_1} = Y_{12} = -\frac{3}{11}S_{\parallel}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$R = (2 \parallel 3) + 1 = \frac{6}{5} + 1 = \frac{11}{5} \quad \therefore Y_{22} = \frac{5}{11} S_{\parallel}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

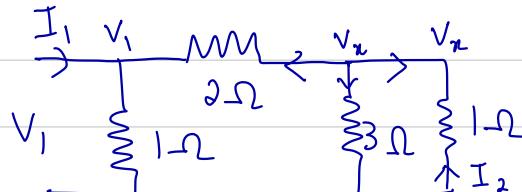

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2}{1} = 0$$

$$\frac{V_2}{2} + \frac{V_2}{1} + \frac{V_2}{3} = \frac{V_1}{2}$$

$$\frac{11}{6} V_2 = \frac{V_1}{2} \Rightarrow V_1 = \frac{11}{3} V_2$$

$$V_2 = -I_2$$

$$V_1 = -\frac{11}{3} I_2$$

$$\therefore Y_{21} = -\frac{3}{11} S$$

$$Y \text{ parameters} = \begin{bmatrix} 15/11 & -3/11 \\ -3/11 & 5/11 \end{bmatrix}$$

Hybrid (h) parameters

$V_1, I_2 \rightarrow$ Dependent variables (responses)

$I_1, V_2 \rightarrow$ Independent variables (excitations)

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

$h_{11} \rightarrow$ Short circuit

circuit

input

impedance

$h_{12} \rightarrow$ Open circuit

voltage

transfer function

$h_{21} \rightarrow$ short circuit

current

transfer function

$h_{22} \rightarrow$ open circuit

output

admittance

Q1> Find h parameters

Ans

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$= \frac{1}{Y_a + Y_c}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$\Rightarrow h_{12} = \frac{Y_c}{Y_a + Y_c}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$\text{But } V_1 = V_2 \times \frac{Y_a}{Y_a + Y_c}$$

$$I_2 = -I_1 \times \frac{Y_a}{Y_a + Y_c}$$


$$\therefore h_{21} = \frac{-Y_c}{Y_a + Y_c}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \left(\frac{1}{Y_a} + \frac{1}{Y_c} \right) \parallel \frac{1}{Y_B}$$

$$\left(\frac{1}{Y_a} + \frac{1}{Y_c} \right) \parallel \frac{1}{Y_B} = \underbrace{\frac{1}{Y_B} \cdot \left(\frac{1}{Y_a} + \frac{1}{Y_c} \right)}_{\frac{1}{Y_a} + \frac{1}{Y_B} + \frac{1}{Y_c}} = \frac{Y_c + Y_a}{Y_a Y_B + Y_B Y_c + Y_c Y_a}$$


$$h_{22} = \frac{Y_a Y_B + Y_B Y_c + Y_c Y_a}{Y_a + Y_c}$$

✓

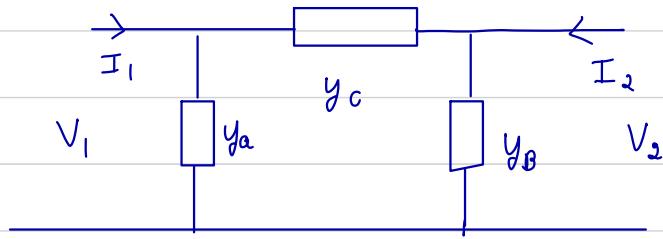

Q2) Find h parameters

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{R_1 R_3}{R_1 + R_3 //}$$

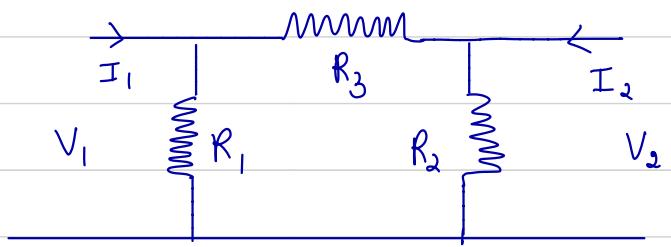

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{R_1}{R_1 + R_3 //}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{-R_1}{R_1 + R_3 //}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{R_2 // (R_1 + R_3)}$$

$$R_2 // (R_1 + R_3) = \frac{R_2 R_1 + R_2 R_3}{R_1 + R_2 + R_3}$$

$$h_{22} = \frac{R_1 + R_2 + R_3}{R_1 R_2 + R_2 R_3}$$

- g parameters

$I_1, V_2 \rightarrow$ Dependent variables

$V_1, I_2 \rightarrow$ Independent variables

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

ABCD parameters (T-parameters)

$V_2, I_2 \rightarrow$ Independent

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$V_1, I_1 \rightarrow$ Dependent

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$A = \frac{V_1}{V_2} \Big|_{\substack{I_2=0}}$$

$$B = \frac{V_1}{-I_2} \Big|_{\substack{V_2=0}}$$


$$C = \frac{I_1}{V_2} \Big|_{\substack{I_2=0}}$$

$$D = \frac{I_1}{-I_2} \Big|_{\substack{V_2=0}}$$

Q1) Find ABCD parameters:

$$A = \frac{V_1}{V_2} \Big|_{\substack{I_2=0}}$$

$$= 6/5 //$$

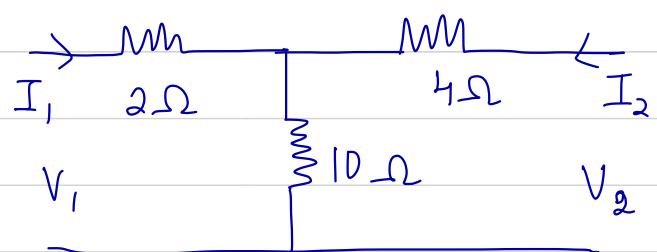


$$C = \frac{I_1}{V_2} \Big|_{\substack{I_2=0}}$$

$$= \frac{1}{10} S //$$

$$D = \frac{I_1}{-I_2} \Big|_{\substack{V_2=0}} = \frac{7}{5} //$$

$$B = \frac{V_1}{I_2} \Big|_{\substack{V_2=0}}$$

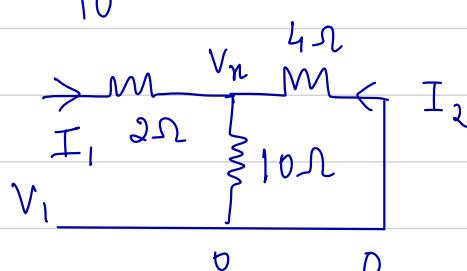

$$\frac{V_1 - V_n}{2} = \frac{V_n}{4} + \frac{V_n}{10}$$

$$V_1 - V_n = \frac{V_n}{5} + \frac{V_n}{2} \Rightarrow V_1 = V_n \left(\frac{3}{2} + \frac{1}{5} \right) = \frac{17}{10} V_n$$

$$V_R = -h I_2$$

$$\therefore V_1 = \frac{-17 \times 4 \times I_2}{10} = \frac{-34 I_2}{5}$$

$$\therefore B = \frac{34}{5} \Omega$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1.2 & 6.8 \\ 0.1 & 1.4 \end{bmatrix}$$

Relationship between ABCD and Z & Y parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$\text{Also } \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{Z_{11}}{Z_{21}}$$

$$\therefore A = \frac{Z_{11}}{Z_{21}}$$

//

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$\text{Also } \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{Z_{21}}$$

$$\therefore C = \frac{1}{Z_{21}}$$

$$Y \text{ parameters: } I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = \frac{-1}{Y_{21}}$$

||| by

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = -\frac{1}{Y_{21}}$$



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} Z_{11} & -\frac{1}{Y_{21}} \\ Z_{21} & Y_{11} \\ \frac{1}{Z_{21}} & -\frac{Y_{11}}{Y_{21}} \end{bmatrix}$$

Condition for Reciprocity

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

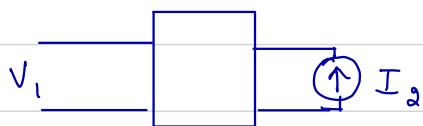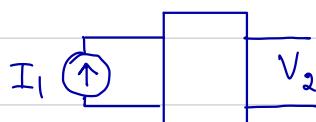

$$\text{For the circuit to be reciprocal, } \left. \frac{V_2}{I_1} \right|_{I_2=0} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$\text{when } I_1 = 0$$

$$CV_2 = DI_2$$

$$\left. \frac{V_2}{I_2} \right|_{I_2=0} = \frac{D}{C}$$

$$V_1 = \left. \frac{AD}{C} I_2 - BI_2 \right|_{I_1=0} \Rightarrow \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{AD}{C} - B$$

$$\therefore \frac{1}{C} = \frac{AD - BC}{C} \quad \therefore AD - BC = 1_f$$


Ex: Find Z & h parameters of CE transistor represented by T circuit model.

Ans

$$V_1 = I_1(r_b + r_e) + I_2 r_e$$

$$V_2 = I_1(r_e) + I_2(r_e + r_c) - r_m I_1$$

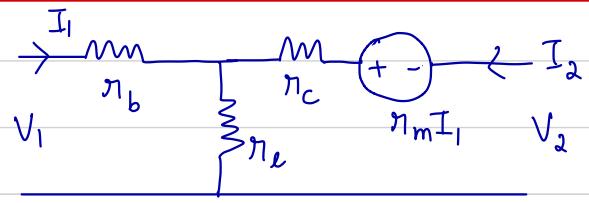
$$V_2 = I_1(r_e - r_m) + I_2(r_e + r_c)$$



$$\therefore Z_{11} = r_b + r_e \quad Z_{12} = r_e$$

$$Z_{21} = (r_e - r_m) \quad Z_{22} = r_e + r_c$$

H parameters: $h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$

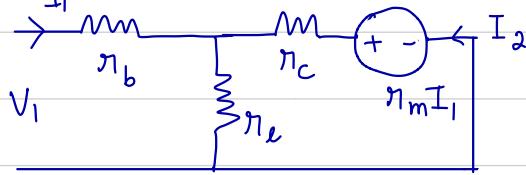


$$V_1 = I_1(r_b + r_e) + I_2 r_e$$

$$0(V_2) = (r_e - r_m) I_1 + I_2 (r_e + r_c)$$

$$\therefore h_{11} = \frac{(r_b + r_e) r_c + r_b r_e + r_e r_m}{r_c + r_e}$$

By we can find other h parameters.

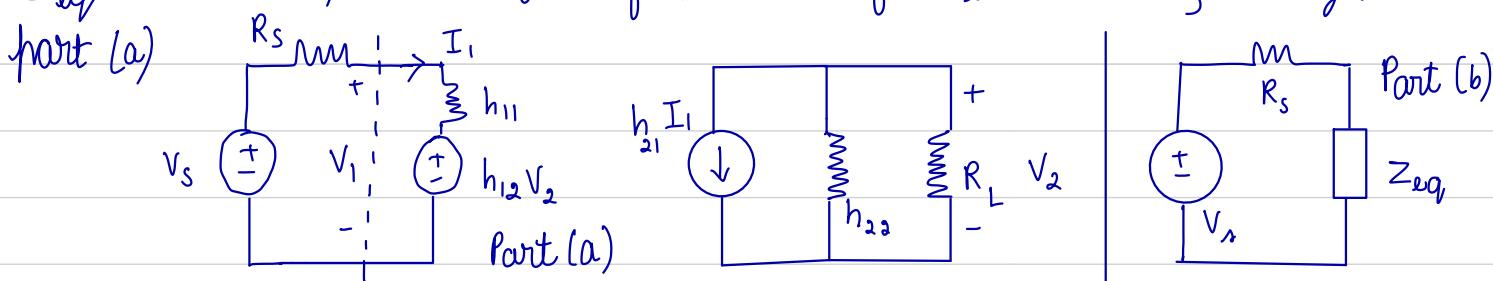Ex2 The circuit in part (a) of figure is to be described by an equivalent input shown in part (b). Determine Z_{eq} in (b) as a function of elements & voltages in part (a)



Ans

$$Z_{eq} = \frac{V_1}{I_1}$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$


$$V_2 = -h_{21} I_1 \times \frac{\frac{1}{h_{22}}}{1 + R_L} = \frac{-h_{21} I_1}{1 + R_L h_{22}}$$

$$V_1 = h_{11} I_1 - \frac{h_{12} h_{21} I_1}{1 + R_L h_{22}}$$


$$\therefore Z_{eq} = \frac{V_1}{I_1} = h_{11} - \frac{h_{12} h_{21}}{1 + R_L h_{22}}$$

HW
Find Z parameters
if $Z_a = Z_d$ & $Z_b = Z_c$
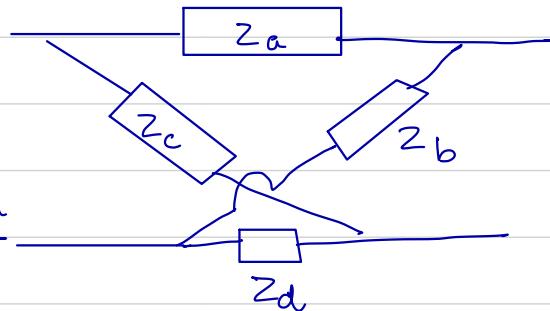
$$Z_{11} = Z_{22} = \frac{Z_a + Z_b}{2} \quad Z_{12} = Z_{21} = \frac{Z_b - Z_a}{2}$$



Interconnection of 2-Port Networks

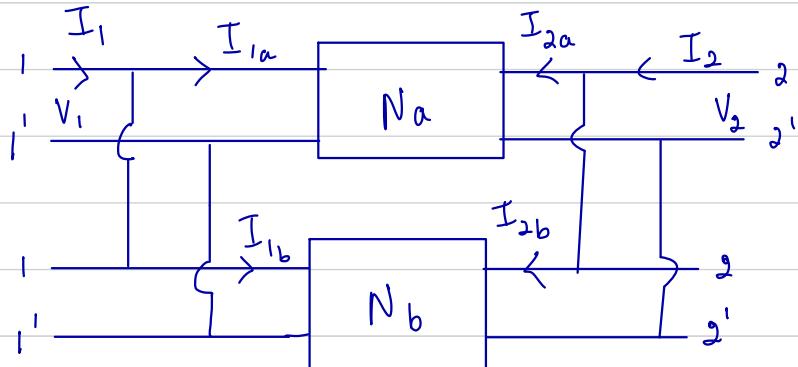

$$V = Z I$$

$$I = Y V$$


$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} Y_{11b} & Y_{12b} \\ Y_{21b} & Y_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11a} + Y_{11b} & Y_{12a} + Y_{12b} \\ Y_{21a} + Y_{21b} & Y_{22a} + Y_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Q1>

Solve :

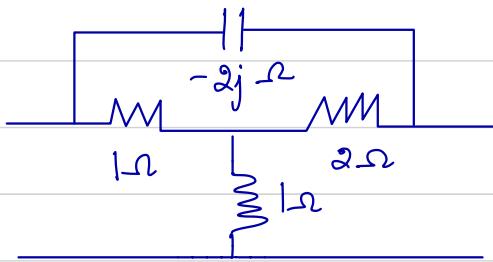

Ans



$$V_1 - V_2 = -2j \times (-I_1)$$

$$= 2j I_1$$

Also $I_1 = -I_2$

$$Y_{11a} = \left| \frac{I_1}{V_1} \right|_{V_2=0} = \frac{j}{2}$$

By

$$\begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} = \begin{bmatrix} j/2 & -j/2 \\ -j/2 & j/2 \end{bmatrix}$$

Also $Z_b = \begin{bmatrix} 2 & 1 \\ 1 & 3 \end{bmatrix}$


NOTE: $[Z]^{-1} = [Y]$

$$\therefore Y_b = \frac{1}{5} \begin{bmatrix} 3 & -1 \\ -1 & 2 \end{bmatrix}$$

$$\therefore Y = Y_a + Y_b$$

$$= \begin{bmatrix} j/2 + 3/5 & -j/2 - 1/5 \\ -j/2 - 1/5 & j/2 + 2/5 \end{bmatrix}$$

Series interconnections

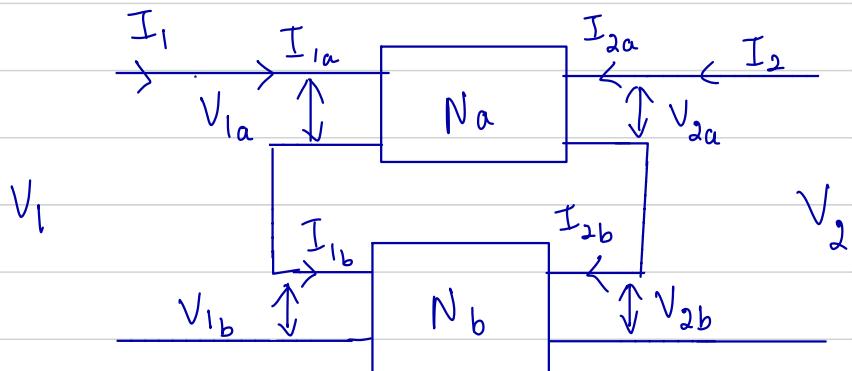

$$V = ZI$$

$$I_1 = I_{1a} = I_{1b}$$

$$V_1 = V_{1a} + V_{1b}$$

$$I_2 = I_{2a} = I_{2b}$$

$$V_2 = V_{2a} + V_{2b}$$

Z parameters


$$\begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} = \begin{bmatrix} Z_{11a} & Z_{12a} \\ Z_{21a} & Z_{22a} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} = \begin{bmatrix} Z_{11b} & Z_{12b} \\ Z_{21b} & Z_{22b} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_{1a} + V_{1b} = V_1 \\ V_{2a} + V_{2b} = V_2 \end{bmatrix} = \begin{bmatrix} Z_{11a} + Z_{11b} & Z_{12a} + Z_{12b} \\ Z_{21a} + Z_{21b} & Z_{22a} + Z_{22b} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Cascade

Interconnections


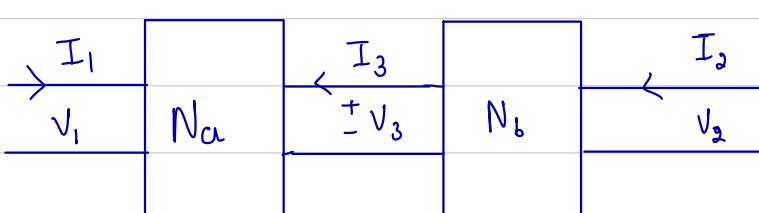


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_3 \\ -I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_3 \\ -I_3 \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$


Q) Find ABCD parameters:

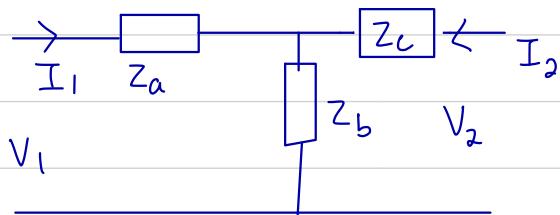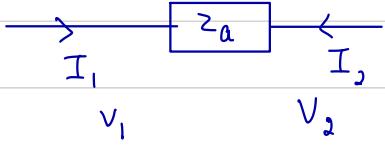

$$V_1 - I_1 z_a = V_2$$

$$\therefore \text{ABCD parameters} = \begin{bmatrix} 1 & z_a \\ 0 & 1 \end{bmatrix}$$

$$\text{But } I_1 = -I_2$$

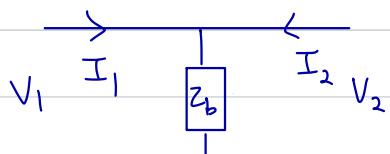


$$V_1 = V_2$$

$$I_1 + I_2 = \frac{V_2}{z_b}$$

$$I_1 = \frac{V_2}{z_b} - I_2$$
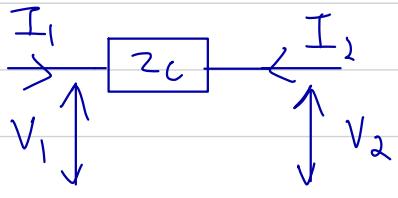
$$\therefore \text{ABCD parameters} = \begin{bmatrix} 1 & 0 \\ 1/z_b & 1 \end{bmatrix}$$




$$\text{ABCD parameters} = \begin{bmatrix} 1 & z_c \\ 0 & 1 \end{bmatrix}$$

$$\therefore \text{Total ABCD parameters: } \begin{bmatrix} 1 & z_a \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{z_b} & 1 \end{bmatrix} \begin{bmatrix} 1 & z_c \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1+z_a/z_b & z_a \\ \frac{1}{z_b} & 1 \end{bmatrix} \begin{bmatrix} 1 & z_c \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1+z_a & z_a + z_c + \frac{z_a z_c}{z_b} \\ z_b & z_b \end{bmatrix}$$

Here $AD - BC = 1$

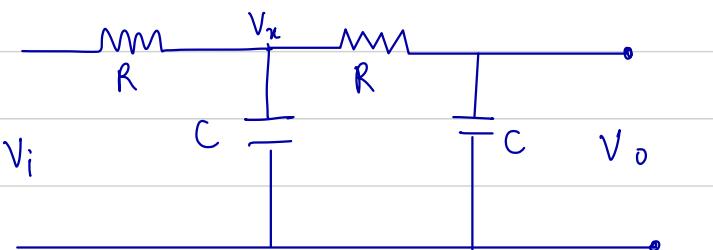

Find the transfer function $\frac{V_o}{V_i}$

Ans

Transfer function:

$$\left(\frac{1}{cs}\right) \parallel \left(R + \frac{1}{cs}\right) \Rightarrow \frac{1}{Z} = cs + \frac{1}{R + \frac{1}{cs}}$$

$$= cs \left(1 + \frac{1}{Rcs + 1}\right)$$

$$= cs \left(\frac{1+Rcs}{1+Rcs}\right)$$

$$\Rightarrow Z = \frac{1+Rcs}{cs(1+Rcs)} \quad \text{Also } V_x = \frac{Vi}{Z}$$

$$V_o = \frac{V_x \times \frac{1}{cs}}{R + \frac{1}{cs}} = \frac{V_x}{1+Rcs}$$


$$\Rightarrow V_o = \frac{Vi}{(Z+R)(1+Rcs)} = \frac{Vi}{(1+Rcs)} \times \frac{(1+Rcs)}{(1+Rcs)cs} \times \frac{1}{\frac{(1+Rcs)}{(1+Rcs)cs} + R}$$

$$\Rightarrow V_o = \cancel{\frac{Vi}{(1+Rcs)}} \times \cancel{\frac{(1+Rcs)}{(1+Rcs)cs}} \times \frac{1}{\frac{(1+Rcs)}{(1+Rcs)cs} + R}$$

$$V_o = \frac{V_i}{1 + RCS + 2RCS + (RCS)^2} = \frac{V_i}{(RCS)^2 + 3RCS + 1}$$

$$\therefore \frac{V_o}{V_i} = \frac{1}{(RCS)^2 + 3RCS + 1}$$

Q5

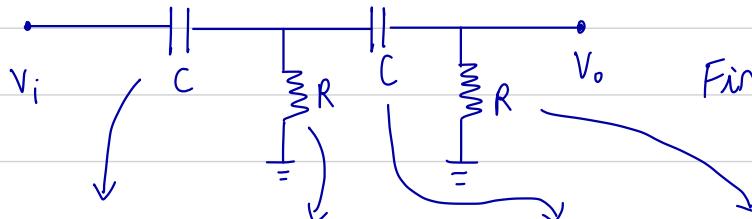

Find Transfer function =

Am

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 1/Cs \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/R & 1 \end{bmatrix} \begin{bmatrix} 1 & 1/Cs \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/R & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{1}{RCS} & \frac{1}{Cs} \\ \frac{1}{R} & 1 \end{bmatrix} \begin{bmatrix} 1 + \frac{1}{RCS} & \frac{1}{Cs} \\ \frac{1}{R} & 1 \end{bmatrix}$$


$$= \begin{bmatrix} 1 + \frac{3}{RCS} + \frac{1}{(RCS)^2} & \frac{2}{Cs} + \frac{1}{Cs^2R} \\ \frac{2}{R} + \frac{1}{R^2Cs} & 1 + \frac{1}{RCS} \end{bmatrix}$$

Transfer function $\frac{V_o}{V_i} = \frac{1}{A}$

$$A = \frac{(RCS)^2 + 3RCS + 1}{(RCS)^2}$$

$$\frac{1}{A} = \frac{(RCS)^2}{(RCS)^2 + 3RCS + 1}$$

Amplifiers

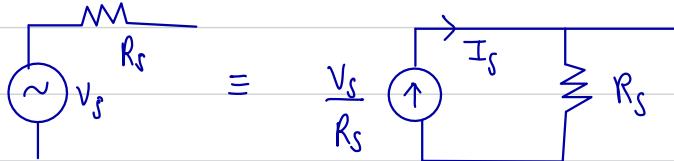

If R_s is very large, it acts as current source.


If R_s is very small, it acts as voltage source.

Type of Amplifiers

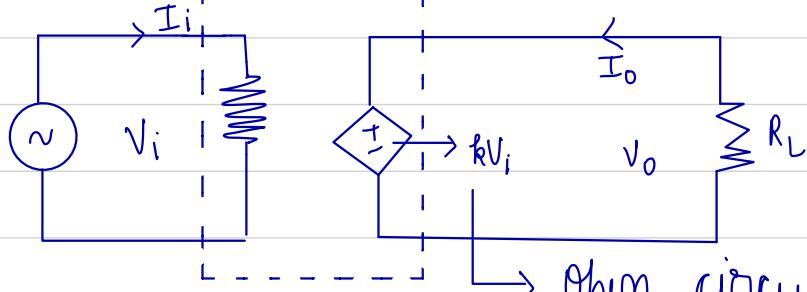- 1) Voltage amplifiers
- 2) Current amplifiers
- 3) Transadmittance amplifiers
- 4) Transimpedance amplifiers
- 5) Transconductance amplifiers


$$\text{Output} = \text{gain} \times \text{Input}$$

where gain is any proportionality constant.



Ideal case
voltage gain

Actual case:

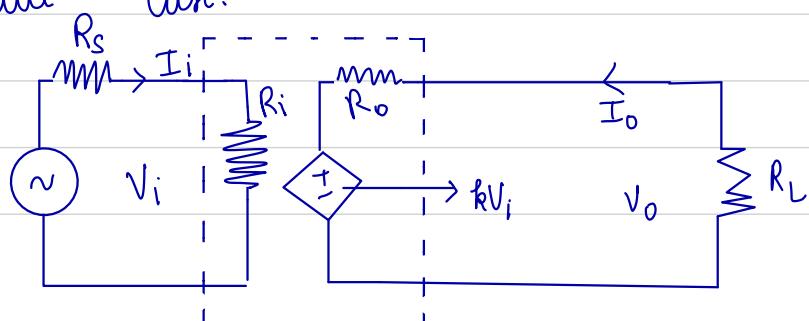

R_i is ideally ∞ . Practically $R_i > R_s$. If $R_i \gg R_s$, amplifier is efficient. $k \rightarrow$ multiplication factor.

$R_o > 0$, $V_o < kV_i$, $\therefore T_0$ minimizes the difference between kV_i & V_o , $R_L \gg R_o$.

Transducer: It converts real world signal to electrical signal. It contains mirrors.

$$V_i = \frac{R_i \times V_s}{R_i + R_s}$$

$$V_o = \frac{A_v V_i \cdot R_L}{R_L + R_o}$$

$$\therefore \frac{V_o}{V_s} = \frac{A_v R_i R_L}{(R_i + R_s)(R_L + R_o)}$$

$$\therefore \frac{V_o}{V_s} = A_v \times \text{loading}$$

$$\text{where loading} = \frac{R_i R_L}{(R_i + R_s)(R_L + R_o)}$$

Here there is no feedback. It is unilateral.

$$\frac{P_o}{P_i} = \frac{V_o I_o}{V_i I_i} \Rightarrow P_{dB} = 10 \log \frac{P_o}{P_i}$$

$$\text{Also } A_{VdB} = 20 \log \frac{V_o}{V_i}$$

$$\underline{\text{Ex}} \quad R_i = 100k\Omega \quad R_o = 1k\Omega \quad R_s = 10k\Omega \quad R_L = 10k\Omega$$

$$A_v = 10^3$$

$$\text{Ans} \quad \frac{V_o}{V_s} = \frac{A_v \times R_i R_L}{(R_i + R_s)(R_L + R_o)} = 10^3 \times \frac{1000 \times 10^6}{(110)(11) \times 10^6}$$

$$= 826.44,$$

$$\text{in dB} = 20 \log 826.44 = 58.34 \text{ dB},$$

$$I_o = \frac{V_o}{R_L}$$

$$I_i = \frac{V_i}{R_i}$$


$$\frac{I_o}{I_i} = \frac{V_o}{V_i} \times \frac{R_i}{R_L} = 9090.9$$

$$P_o = \frac{V_o I_o}{V_i I_i} = 8.26 \times 10^6$$


$$\begin{aligned} P_{dB} &= 10 \log (8.26 \times 10^6) \\ &= 10 (6 + 0.917) \\ &= 69.17 \text{ dB}_{II} \end{aligned}$$

2) Current amplifiers: Current controlled current source.

Ideal: $R_i = 0$ $R_o = \infty$

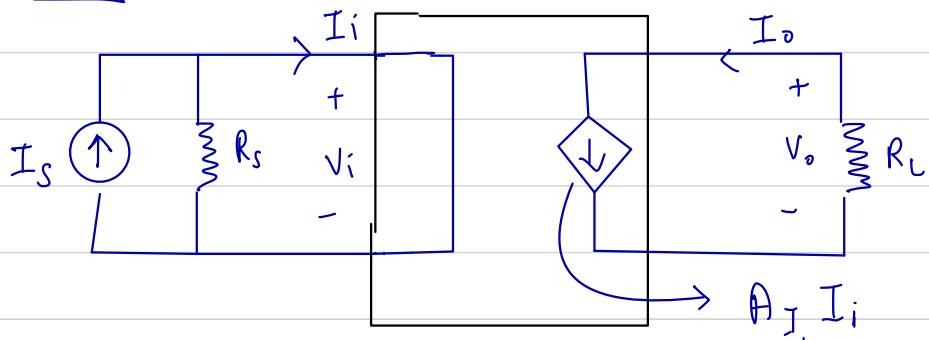

Practical:

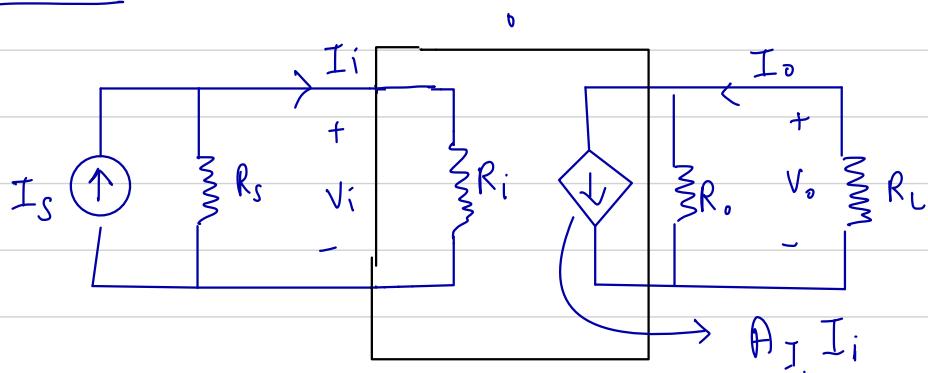

$$R_i \ll R_s$$

$$R_o \gg R_L$$

$$I_i = \frac{R_s I_s}{R_s + R_i}$$

$$I_o = \frac{R_o \times A_I I_i}{R_o + R_L}$$

$$\therefore \frac{I_o}{I_s} = \frac{R_o A_I R_s}{(R_o + R_L)(R_s + R_i)}$$

$$\therefore \frac{I_o}{I_s} = A_i \times \text{loading}$$

Q) An amplifier with R_i of $1\text{k}\Omega$ is fed by independent current source with $R_s = 10\text{k}\Omega$, $A_I = 100$, R_o for dependent \mathcal{I} source is $100\text{k}\Omega$. Determine I_o/I_s when $R_L = 10\text{k}\Omega$, also find the power gain

Ans

$$\frac{I_o}{I_s} = A_I \frac{R_o R_s}{(R_o + R_L)(R_i + R_s)} = 100 \times \frac{100 \times 10 \times 10^6}{(110)(11) \times 10^6}$$

$$= 82.64,$$

$$\therefore \text{im dB} = 20 \log (82.64) = 38.34 \text{ dB},$$


$$\frac{P_o}{P_i} = \frac{V_o I_o}{V_i I_i} = \frac{R_L}{R_i} \left(\frac{I_o}{I_i} \right)^2$$

$$= 10 (82.64)^2 = 68293.7$$

$$P_{\text{gain}} = 10 \log (68293.7) = 48.34 \text{ dB};$$

3)


Transconductance Amplifier

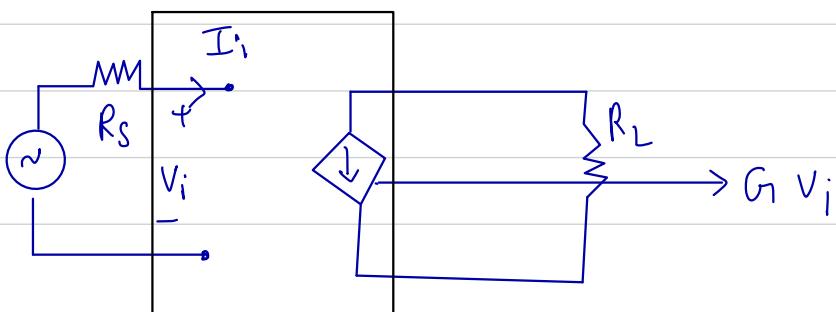

$$R_i = \infty$$

$$R_o = \infty$$

Actual case.

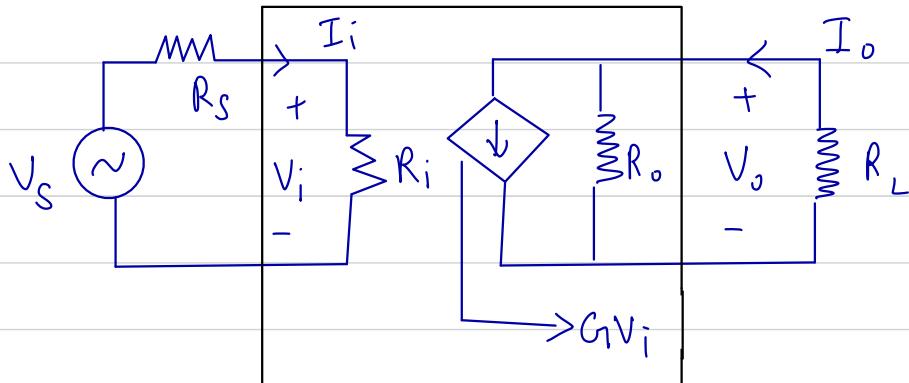


$$R_i \gg R_s$$

$$R_o \gg R_L$$

Actual case

h>


Transresistance amplifier

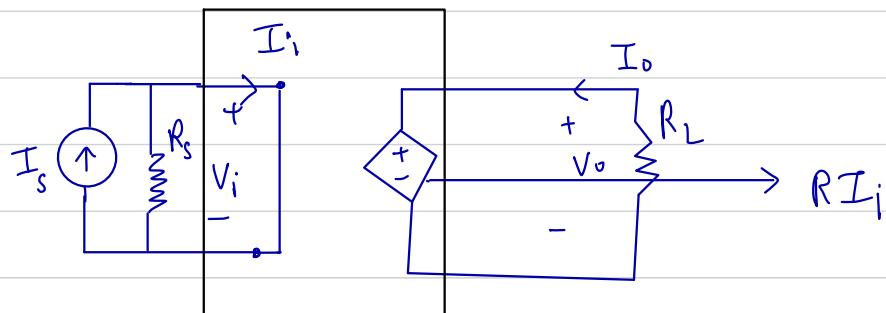

$$R_i = 0$$

$$R_o = 0$$

Ideal case

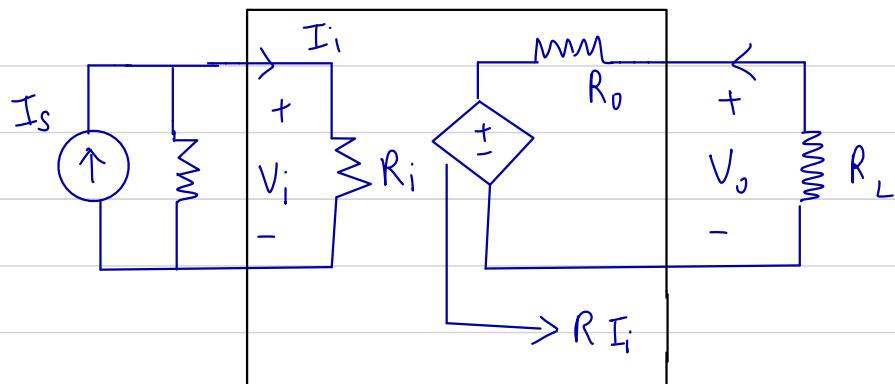

$$R_i \ll R_s$$

$$R_o \ll R_L$$


Amplifier types

Amplifier	R_i		R_o	
	Ideal	Practical	Ideal	Practical
1) voltage Amplifier (VCVS)	∞	$R_i \gg R_s$	0	$R_o \ll R_L$
2) Current Amplifier (CCCS)	0	$R_i \ll R_s$	∞	$R_o \gg R_L$
3) Transconductance amplifier (VCCS)	∞	$R_i \gg R_s$	∞	$R_o \gg R_L$
4) Transresistance amplifier (CCVS)	0	$R_i \ll R_s$	0	$R_o \ll R_L$

Q> A source of $5 \mu\text{A}$ with internal resistance $200 \text{ k}\Omega$ drives a transresistance amplifier with a short circuit current $I_s = 30 \text{ mA}$. Given that amplifier has a transresistance of $2 \text{ k}\Omega$. Find R_i , R_o , R and V_o/I_s .

Ans

$$V_i = 100 \text{ mV}$$

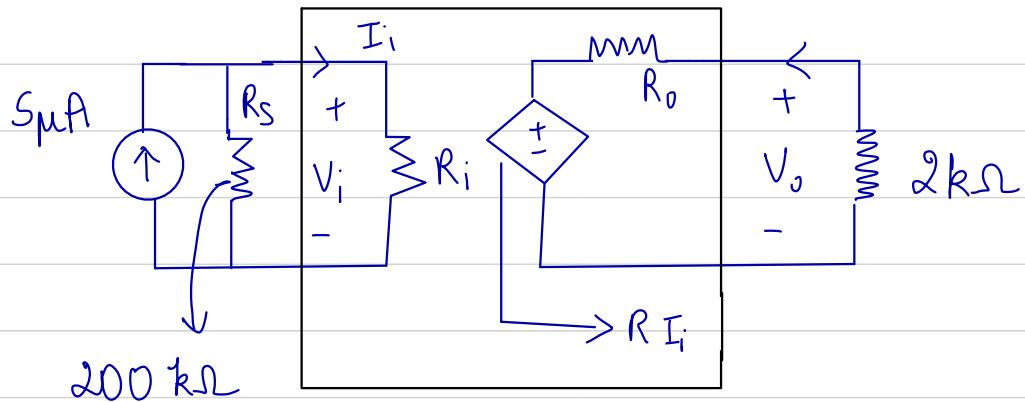

$$V_i = 100 \text{ mV} = I_i R_i = \frac{I_s R_o R_i}{R_i + R_s}$$

$$\therefore R_i = 22.22 \text{ k}\Omega$$

$$30 \text{ mA} = \frac{\text{D.C. voltage}}{R_o} = \frac{R I_i}{R_o}$$

$$R_o = 466.66 \text{ }\Omega$$

$$I_i = \frac{V_i}{R_i} = \frac{100 \text{ mV}}{22.22 \text{ k}\Omega} = 4.5 \mu\text{A}$$

$$I_s = 0.5 \mu\text{A} \quad (5 - I_i)$$

$$R = \frac{14}{I_i} = \frac{14}{4.5} = 3.11 \times 10^6 \text{ V/A}$$

$$V_o = \frac{R_L R I_i}{R_L + R_o}$$

$$I_i = \frac{I_s R_s}{R_s + R_i}$$

$$\frac{V_o}{I_s} = \frac{R_s \times R \times R_L}{(R_s + R_i)(R_L + R_o)} = 2.27 \text{ V/mA}$$

Q> A transresistance amplifier is designed with R_i of $50 \text{ k}\Omega$, $R = 0.5 \text{ V/mA}$ which is decided by the input current I_i and $R_o = 100 \Omega$. If it is driven by a source I_s with parallel internal resistance of $300 \text{ k}\Omega$ and resistance of 500Ω

as what is the transresistance V_o/V_s . Also find Power gain $\frac{P_i}{P_s}$ where P_i is the power absorbed by source ΣP_s is power delivered by the source.

b> what should be the gain of the amplifier if we want to achieve a V_o/I_s of 1 V/mA . find what is the power gain in this case

Ans $R_s = 300 \text{ k}\Omega$


$R_i = 50 \text{ k}\Omega$

$R_o = 100 \Omega$

$$V_o = \frac{R_L R I_i}{R_L + R_o}$$

$$\frac{V_o}{I_s} = \frac{R_L \cdot R \cdot R_s}{(R_L + R_o)(R_i + R_s)}$$

$$= 0.357 \text{ V/mA}$$

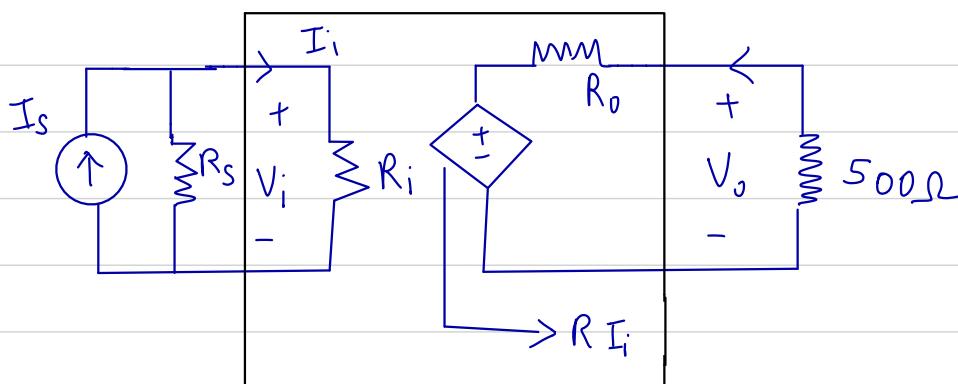

$$P_s = I_s^2 (R_s \parallel R_i) = I_s^2 \frac{R_s R_i}{R_i + R_s} = 42.857 \text{ k}\Omega \times I_s^2$$

$$P_L = \frac{V_o^2}{R_L} = \frac{V_o^2}{500}$$

$$\frac{P_L}{P_s} = \frac{V_o^2}{500 \times 42.857 \text{ k} \times I_s^2} = 5.9 \text{ mW/W}$$

b>


$$\frac{V_o}{I_s} = 1 \text{ V/mA}_i$$

$$\frac{V_o}{I_s} = \frac{R_L \times R \times R_s}{(R_L + R_s)(R_i + R_s)}$$


$$\therefore R = 1.4 \text{ V/mA}_i$$

$$\text{Also } \frac{P_L}{P_s} = 46.6 \text{ mW/W}$$

Cascading of amplifiers

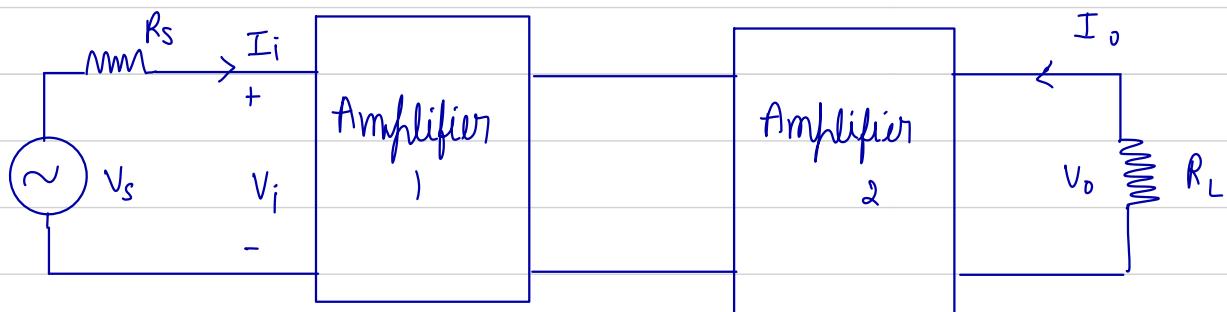

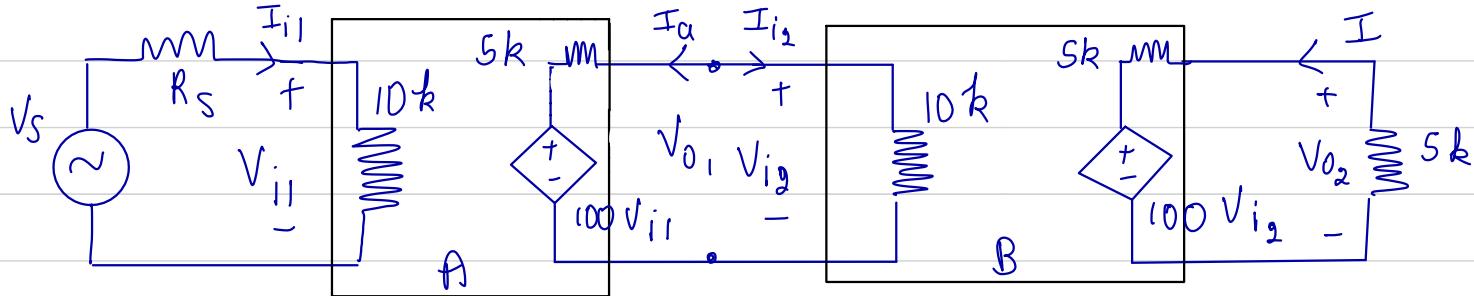Q> An amplifier A with R_i of $10 \text{ k}\Omega$ & $R_o = 5 \text{ k}\Omega$ has open loop gain 100. It is cascaded with another identical amplifier B. The source has resistance of $4 \text{ k}\Omega$. The load resistance for amplifier B is $5 \text{ k}\Omega$. Determine the overall voltage gain, current gain, power gain.



$$\text{Ans} \quad \frac{V_{i1}}{V_s} = \frac{10}{15}; \quad \frac{V_{o1}}{V_{i1}} \Rightarrow \frac{100 V_{i1} \times 10}{15} = V_{o1} = V_{i2}$$

$$\frac{V_{o1}}{V_{i1}} = \frac{100 \times 10}{15} = \frac{V_{i2}}{V_{i1}}$$

$$\frac{100 V_{i2} \times 5}{10} = V_{o2}$$

$$\frac{V_{o2}}{V_{i2}} = \frac{100 \times 5}{10} = 50$$

$$\frac{V_{o2}}{V_{i1}} = \frac{V_{o2}}{V_{i2}} \times \frac{V_{i2}}{V_{i1}} = 50 \times \frac{1000}{15} = 3333.33 //$$


$$\text{i) } V_{o2} = \frac{V_{o2}}{V_{i1}} \times \frac{V_{i1}}{V_s} = 3333.33 \times \frac{5}{7} = 2380.95 //$$

$$\text{ii) } V_{i1} = I_{i1} \times 10k \quad V_{o2} = -I_{o2} \times 5k \\ \therefore \frac{I_{o2}}{I_{i1}} = -\frac{V_{o2}}{5k} \times \frac{10k}{I_{i1}} = -2 \times 3333.33 = -6666.66$$

$$\text{iii) power gain} = \left| \frac{V_{o2} \cdot I_{o2}}{V_{i1} \times I_{i1}} \right| = (3333.33) \cdot (6666.66) \\ = 22.22 \times 10^6$$

$$P_{dB} = 10 \log (22.22 \times 10^6) = 10(6 + 1.346) = \underline{\underline{73.46 \text{ dB}}}$$

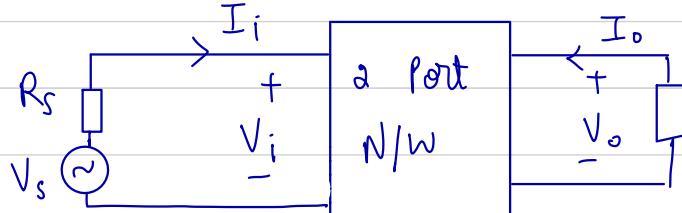Link between 2 port parameters and amplifiers



Z parameters

$$V_i = Z_i I_i + Z_{\pi} I_o \Rightarrow [Z] = \begin{bmatrix} Z_i & Z_{\pi} \\ Z_f & Z_o \end{bmatrix}$$

$$V_o = Z_f I_i + Z_o I_o$$

For ideal amplifier, $Z_{\pi} = 0$

If Z_i, Z_o are also zeroes then it becomes ideal CCVS (transresistance) amplifier.

Y parameters

$$I_i = Y_i V_i + Y_{\pi} V_o$$

$$I_o = Y_f V_i + Y_o V_o$$

$$[Y] = \begin{bmatrix} Y_i & Y_{\pi} \\ Y_f & Y_o \end{bmatrix}$$

If $Y_i, Y_{\pi}, Y_o = 0$ then we get ideal VCCS (transconductance) amplifier.



$$\text{current gain} = Z_f^i \cdot y_f$$

Similarly



VCVS

$$\text{voltage gain} = Z_f^i y_f$$

h parameters

$$V_i = h_i I_i + h_n V_o$$

$$I_o = h_f I_i + h_o V_o$$

$$[h] = \begin{bmatrix} h_i & h_n \\ h_f & h_o \end{bmatrix}$$

If $h_i, h_n, h_o = 0$ then we get ideal CCCS amplifier
i.e. current amplifiers.

-g parameters

$$I_i = g_i V_i + g_n I_o$$

$$V_o = g_f V_i + g_o I_o$$

$$[g] = \begin{bmatrix} g_i & g_n \\ g_f & g_o \end{bmatrix}$$


If $g_i, g_n, g_o = 0$ then we get ideal VCVS amplifier
i.e. voltage amplifiers.

Equivalent circuit


Z parameters

$$V_i = Z_i I_i + Z_n I_o$$

$$V_o = Z_f I_i + Z_o I_o$$

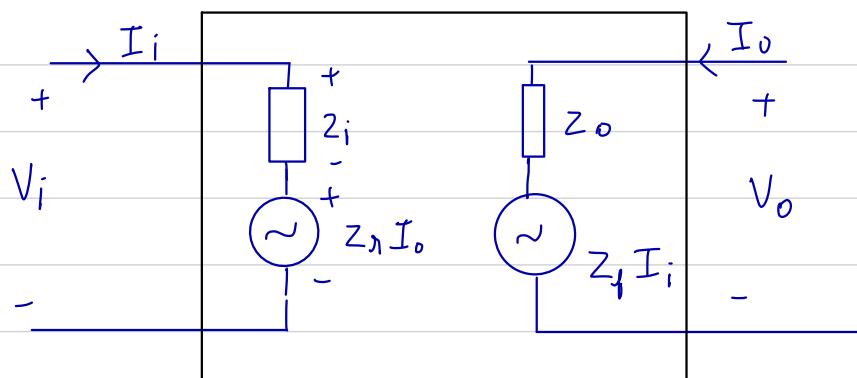

y - parameters

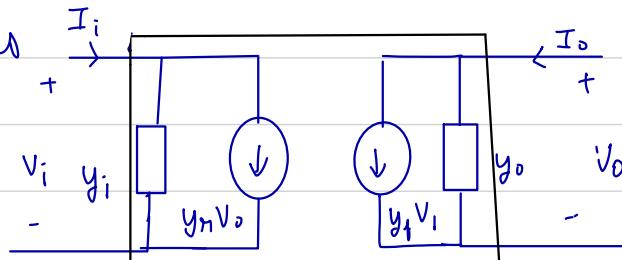


$$I_i = y_i V_i + y_n V_o$$

$$I_o = y_f V_i + y_o V_o$$

h parameters :

$$V_i = h_f I_i + h_o V_o$$


$$I_o = h_f I_i + h_o V_o$$

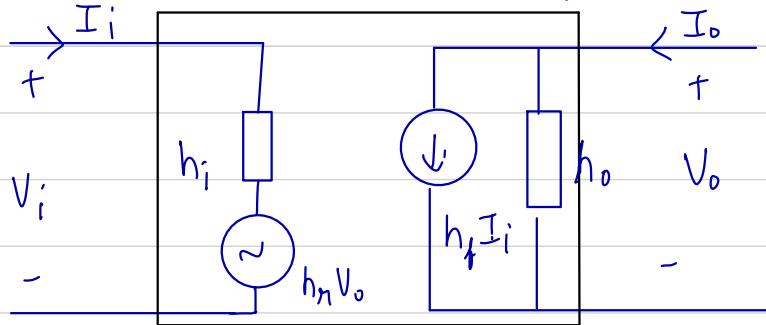

g parameter :

$$I_i = g_f V_i + g_o I_o$$


$$V_o = g_f V_i + g_o I_o$$

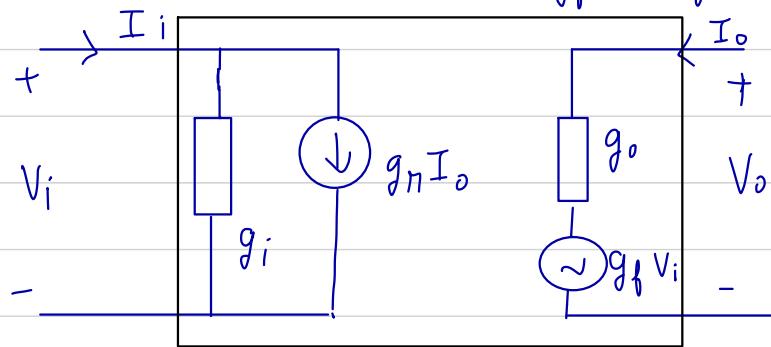

y parameters : (Actual amplifier)

$$I_i = y_i V_i + y_n V_o$$

$$I_o = y_f V_i + y_o V_o$$

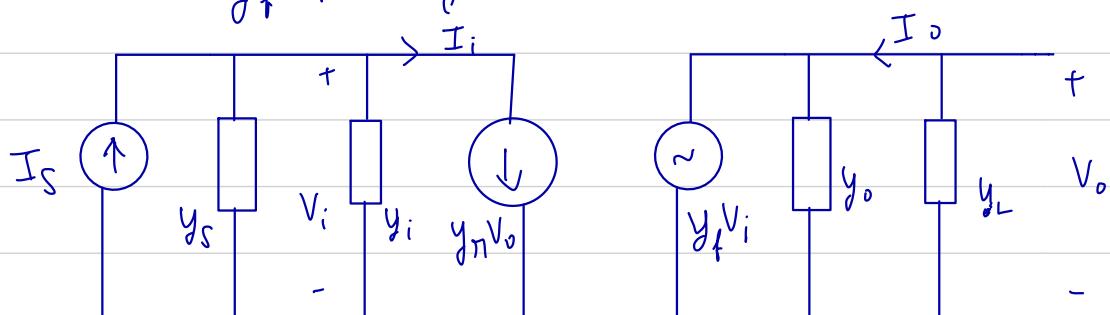

$$y_i = \frac{I_i}{V_i} \text{ (ideal)} \quad V_o = -y_f V_i \times \frac{1}{y_o + y_L} = -\frac{y_f V_i}{y_o + y_L}$$

$$I_i = y_i V_i - \frac{y_n y_f V_i}{y_o + y_L}$$

$$\therefore \frac{I_i}{V_i} = y_i - \frac{y_n y_f}{y_o + y_L} = y_{in}$$

voltage gain $\frac{V_o}{V_i} = -\frac{y_f}{y_o + y_L}$

$$V_o = -\frac{I_o}{y_L}$$

$$V_i = \frac{I_i}{y_{in}}$$

$$\therefore \frac{V_o}{V_i} = -\frac{I_o y_{in}}{I_i y_L}$$

\therefore Current gain =

$$\frac{I_o}{I_i} = -\frac{V_o y_L}{V_i y_{in}}$$



Make $I_o = 0$.

Then, $V_i = -\frac{y_n V_o}{y_n + y_i}$

$$I_o = y_f V_i + y_o V_o$$

$$I_o = \left(-\frac{y_f y_n}{y_f + y_i} + y_o \right) V_o$$
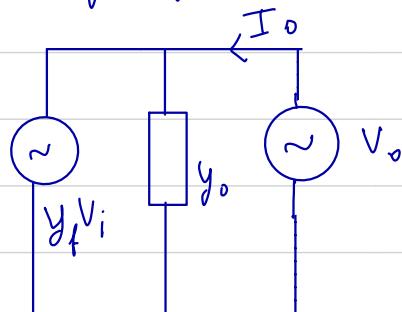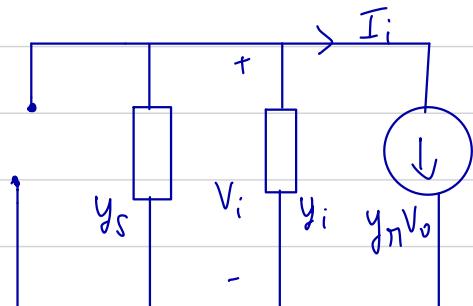
$$\therefore \frac{I_o}{V_o} = Y_{out} = y_o - \frac{y_n y_f}{y_n + y_i}$$




$$\text{Power gain} \quad \left| \frac{P_o}{P_i} \right| = \left| \frac{V_o I_o}{V_i I_i} \right|$$

$$\text{Impedance: } Z_{in} = Z_i - \frac{Z_s Z_f}{Z_o + Z_L}$$

$$Z_{out} = Z_o - \frac{Z_s Z_f}{Z_s + Z_i}$$

$$\text{Immittance: } b_{in} = p_i - \frac{h_r h_f}{h_o + h_L} \quad b_{out} = p_o - \frac{h_r h_f}{h_s + h_i}$$

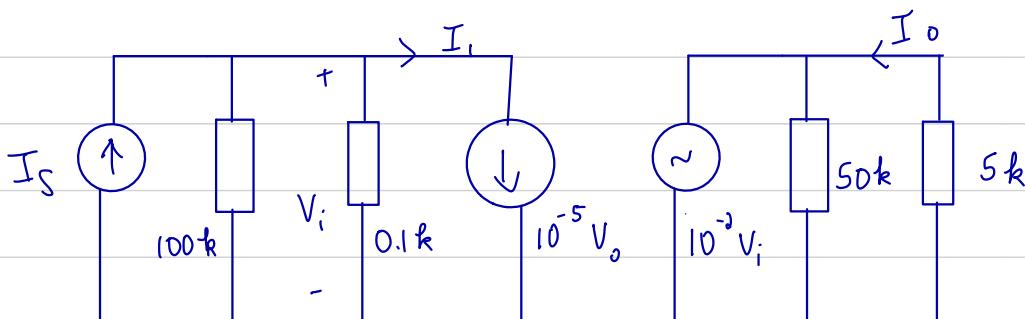Q3 For the 2 port network shown, determine $\frac{V_o}{V_i}$, $\frac{I_o}{I_i}$, R_{in} , R_{out} , $\frac{P_o}{P_i}$



$$\begin{bmatrix} y_i & y_n \\ y_f & y_o \end{bmatrix} = \begin{bmatrix} 10^{-2} & 10^{-5} \\ 10^{-2} & 2 \times 10^{-5} \end{bmatrix}$$

$$\frac{V_o}{V_i} = \frac{-y_f}{y_o + y_L} = \frac{-10^{-2}}{2 \times 10^{-5} + 20 \times 10^{-5}} = -10^3 \times \frac{1}{22} = -45.45 \parallel$$

$$y_{in} = y_i - \frac{y_n y_f}{y_o + y_L} = 10^{-2} + 10^{-5} (-45.45) \\ = 9.54 \times 10^{-3} \parallel$$

$$R_{in} = \frac{1}{y_{in}} = 104.8 \parallel$$

$$\frac{I_o}{I_i} = -\frac{V_o}{V_i} \frac{R_{in}}{R_L}$$

$$= 45.45 \times \frac{104.82}{5 \times 10^3} = 0.952$$


$$\frac{P_o}{P_i} = \left| \frac{V_o I_o}{V_i I_i} \right| = 45.45 \times 0.952 = 43.03$$

$$Y_{out} = Y_o - \frac{Y_s Y_f}{Y_s + Y_i} = 2 \times 10^{-5} - \frac{10^{-5} \times 10^{-2}}{10^{-5} + 10^{-2}} = 10^{-5}$$

$$R_{out} = 100 \text{ k}\Omega$$

Feedback concept

Negative feedback :

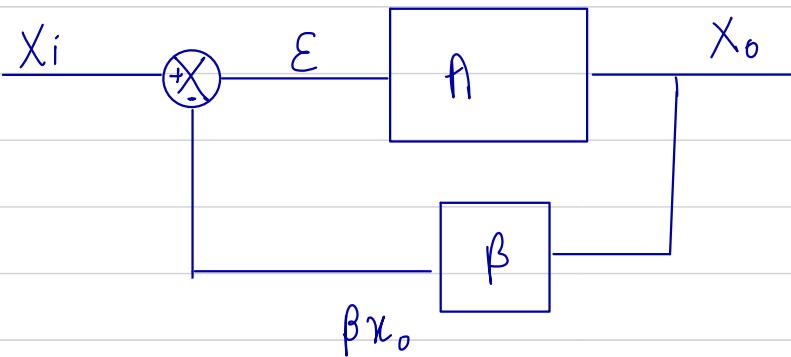

$$E = X_i - \beta X_o$$

$$X_o = A(X_i - \beta X_o)$$

$$\Rightarrow X_o (1 + A\beta) = Ax_i$$

$$X_o = \left(\frac{A}{1 + A\beta} \right) X_i$$

$$\therefore A \rightarrow \underline{A}$$

$$1 + A\beta$$

\therefore gain reduces.

If $A\beta$ is very large, $\frac{A}{1 + A\beta} \approx \frac{A}{A\beta} = \frac{1}{\beta}$

$$\frac{A}{1 + A\beta} = A_f$$

Advantages of negative feedback

1) Sensitivity or Reduction in active parameter sensitivity.

$$S_A^{Af} = \frac{\partial A_f / A_f}{\partial A / A} = \left(\frac{\partial A_f}{\partial A} \right) \cdot \frac{A}{A_f} = \frac{1}{(1 + A\beta)^2} \cdot \frac{A}{A} (1 + A\beta)$$

$$= \frac{1}{1 + A\beta} \approx \frac{1}{A\beta} (\because A\beta \gg 1)$$

2) Linearity Improvement:

- A non linear circuit will have

$$V_{out} = V_{offset} + Av_i + k_1 v_i^2 + k_2 v_i^3 + \dots$$

For negative feedback:

$$V_{out} = V_{offset} + A(v_i - \beta V_o) + N \quad \text{where } N = k_1 v_i^2 + k_2 v_i^3 + \dots$$

$$V_{out}[1 + A\beta] = V_{offset} + Av_i + N$$

$$\therefore V_{out} = \frac{V_{offset}}{1 + A\beta} + \frac{Av_i}{1 + A\beta} + \frac{N}{1 + A\beta}$$

$$\Rightarrow \frac{V_{out}}{v_i} \approx \frac{1}{\beta}$$

3) Bandwidth Improvement

$$\text{Def} \quad A = \frac{A_o}{1 + \frac{s}{\omega_o}} \quad (\text{forward gain})$$

$$A_f = \frac{A}{1+A\beta} = \frac{A_0}{1+\frac{A_0}{1+\frac{S/\omega_0}{1+\frac{\beta A_0}{1+S/\omega_0}}}} = \frac{A_0}{1+\frac{S}{\omega_0} + A_0\beta} = \frac{A_0}{1+\frac{S}{\omega_0(1+A_0\beta)}}$$

So $A_0 \rightarrow \frac{A_0}{1+A_0\beta}$ and $\omega_0 \rightarrow \omega_0(1+A_0\beta)$

Hence bandwidth increases.

$$\text{But } A_{\text{initial}} \cdot \omega_{\text{initial}} = A_{\text{final}} \cdot \omega_{\text{final}}$$

Q3 A feedback amplifier consists of 2 Amplifier blocks in series. Each has a gain of 100. a) If overall gain is 100, then calculate the gain of feedback circuit.

b) If gain of each block reduces by 50%, then calculate the overall gain of feedback.

Ans as Total gain = $A_1 A_2 = 10^4$

$$A_f = \frac{A}{1+A\beta} = 100$$

$$\Rightarrow \frac{10^4}{1+\beta \cdot 10^4} = 100 \quad \therefore \beta = 0.0099,$$

b) Total gain = $A'_1 A'_2 = 2500$

$$A_f = \frac{2500}{1+0.0099 \times 2500} = 97.08,$$

Q3 An amplifier with open loop gain of $A = 2000 \pm 150$ is available. It is necessary to have an amplifier whose gain varies not more than 0.2%. Compute A_f & β .

Aus

$$\frac{dA_f}{A_f} = 0.2\%$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \times \frac{1}{1+A\beta}$$


$$\frac{0.2}{100} = \frac{150}{2000} \quad \frac{1}{1+2000\beta}$$

$$1+2000\beta = 37.5$$

$$2000\beta = 36.5$$

$$A_f = \frac{A}{1+A\beta} = \frac{2000}{37.5} = 53.33$$

positive feedback

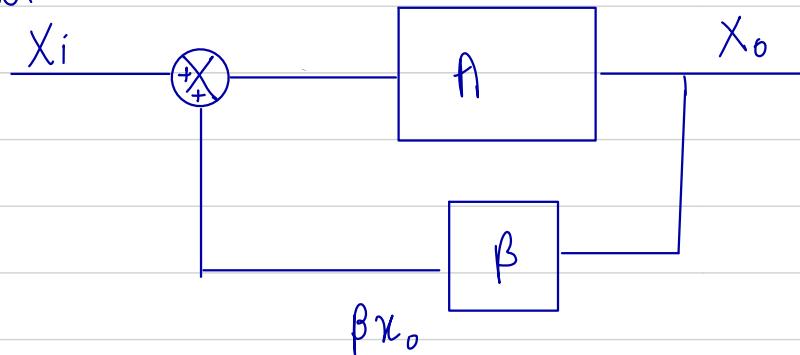

$$A_f = \frac{A}{1-A\beta} \quad \text{i.e. } A_f > A$$

$$S_A^{\frac{A_f}{A}} = \frac{1}{1-A\beta}$$

Oscillation criterion

Barkhausen oscillation criterion:


$$A\beta = 1$$

i.e. $|A\beta| = 1$


$$|A\beta| = 0^\circ \text{ or } 360^\circ$$

$$L(s) = A(s) B(s)$$

$$L(j\omega) = A(j\omega) B(j\omega)$$

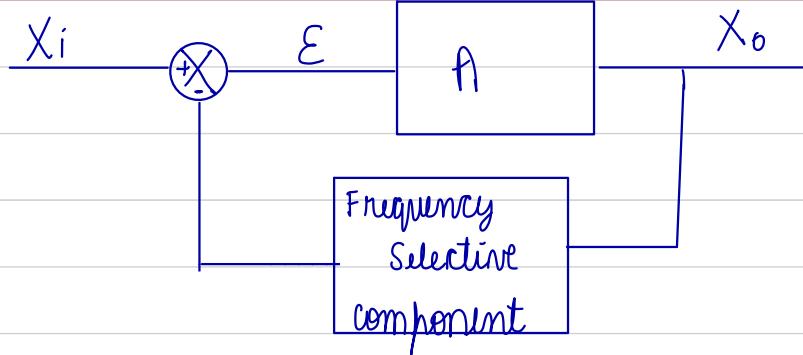

VCVS with -ve feedback

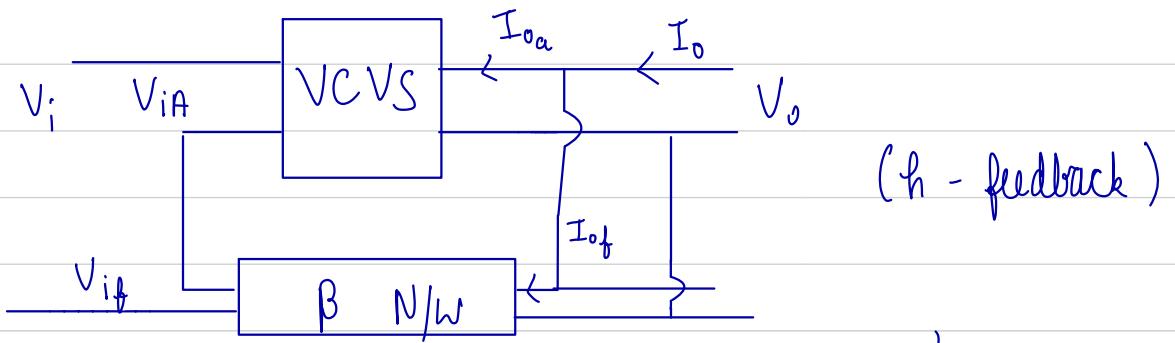

$$[h] = \begin{bmatrix} h_{ia} + h_{if} & h_{ra} + h_{rf} \\ h_{fa} + h_{ff} & h_{oa} + h_{of} \end{bmatrix} \quad [g] = [h]^{-1}$$

$$i.e \quad g_i = \frac{h_{oa} + h_{of}}{\Delta h} \quad g_n = \frac{-(h_{ra} + h_{rf})}{\Delta h}$$

$$g_o = \frac{-(h_{ia} + h_{if})}{\Delta h} \quad g_f = \frac{-(h_{fa} + h_{ff})}{\Delta h}$$

$$\begin{aligned} \Delta h &= (h_{ia} + h_{if}) \cdot (h_{oa} + h_{of}) - (h_{ra} + h_{rf}) \cdot (h_{fa} + h_{ff}) \\ &= \left[1 - \frac{h_r h_f}{h_i h_o} \right] h_i h_o \quad \text{but } \frac{h_r h_f}{h_i h_o} = A\beta \\ &= (1 - A\beta) h_i h_o \end{aligned}$$

If $A\beta$ is -ve it is negative feedback. If $A\beta$ is +ve it is positive feedback.

$$g_i = \frac{h_o}{(1 - A\beta) h_i h_o} = \frac{1}{(1 - A\beta) h_i} \Rightarrow g_i \rightarrow 0$$


$$g_f = \frac{-h_f}{(h_i h_o - h_n h_f) h_i h_o} \approx \frac{1}{h_n} = \frac{1}{h_{n_a} + h_{n_f}} \approx \frac{1}{h_{n_f}}$$

$$g_n = \frac{-h_n}{\left(1 - \frac{h_n h_f}{h_i h_o}\right) h_i h_o} \approx \frac{1}{h_f} \Rightarrow g_n \downarrow$$

$$g_o = \frac{h_i}{(1 - A\beta) h_i h_o} = \frac{1}{(1 - A\beta) h_o} \Rightarrow g_o \rightarrow 0$$


CCCS: ideal = $\begin{bmatrix} 0 & 0 \\ h_f & 0 \end{bmatrix}$
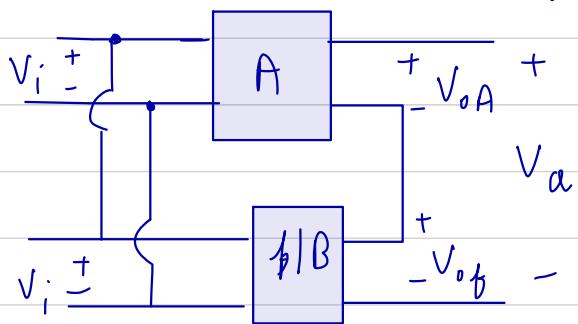
$$\begin{aligned} j_i &= g_i v_i + g_n I_o \\ v_o &= g_f v_i + g_o I_o \end{aligned}$$



improve h parameters
using g parameters

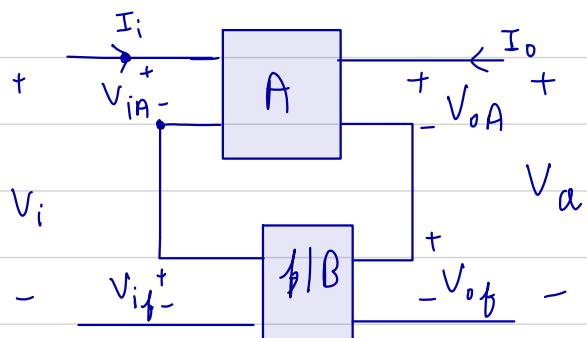VCCS: ideal = input impedance = ∞
output impedance = ∞




improve Y parameters
using Z parameters

$$V_i = Z_i j_i + Z_n I_o$$

$$V_o = Z_f I_i + Z_o I_o$$

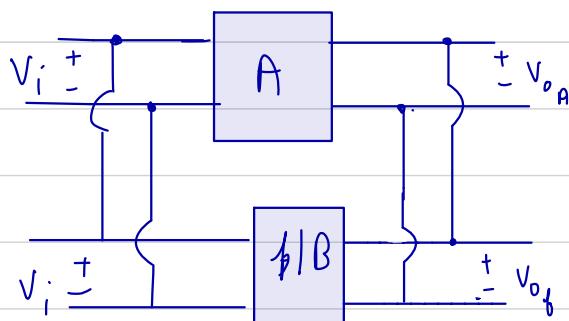CCVS: Ideal \rightarrow input impedance = 0
output impedance = 0




Improve Z parameters using Y parameters

- In general $A_B = \frac{P_o P_f}{P_i P_d}$ (immittance)


Effect of -ve feedback on gain and I/p, o/p impedances

VCVS:

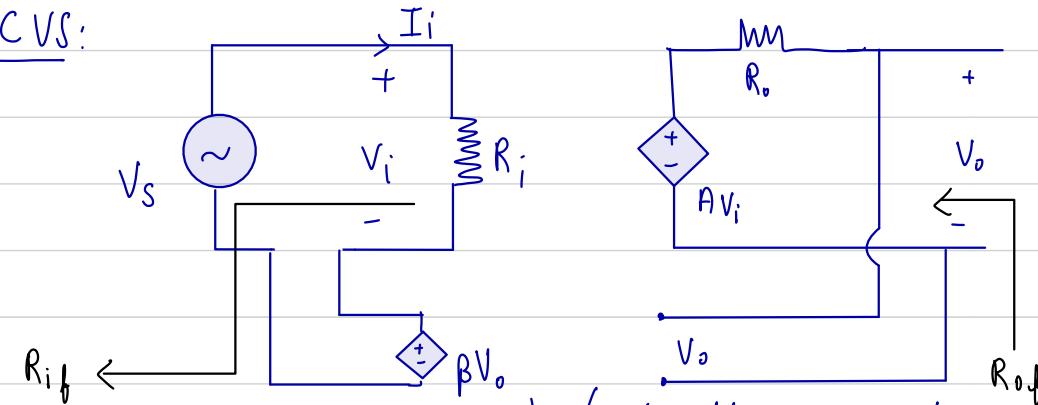

(series-shunt feedback) / (voltage-voltage feedback)
o/p i/p

Equivalent circuit:

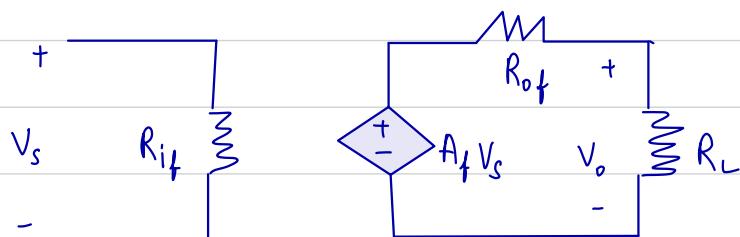


$$\text{Gain: } A_f \rightarrow \frac{A}{1 + A\beta}$$

$$\begin{aligned}
 V_o &= AV_i \\
 &= A(V_s - V_f) \\
 &= A(V_s - \beta V_o) \\
 V_o(1 + A\beta) &= AV_s \\
 \frac{V_o}{V_s} &= \frac{A}{1 + A\beta}
 \end{aligned}$$

Input impedance, $R_{if} = \frac{V_s}{I_i} = \frac{V_s}{V_i/R_i} = \frac{V_s}{V_i} R_i$

$$R_{if} = \frac{R_i(V_i + V_f)}{V_i} = \frac{R_i(V_i + \beta V_o)}{V_i} = \frac{R_i(V_i + A\beta V_i)}{V_i} = R_i(1 + A\beta)$$

Output impedance:

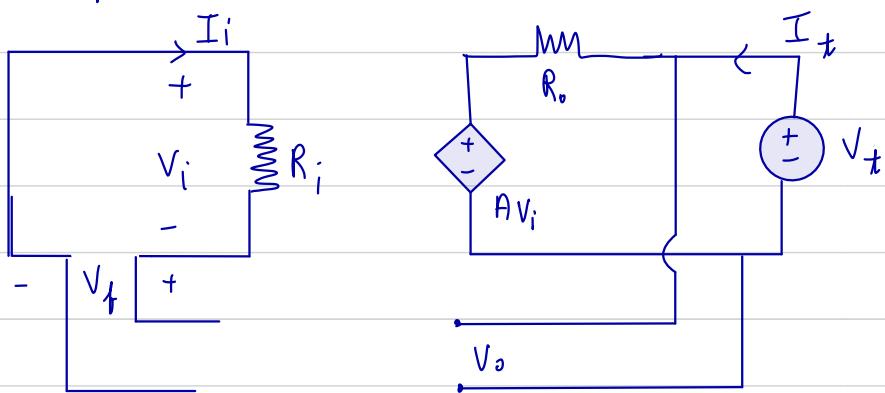


$$R_{of} = \frac{V_t}{I_t} \quad I_t = \frac{V_t - AV_i}{R_o}$$

$$\begin{aligned}
 V_s &= 0 & V_i &= -V_f = -\beta V_o = -\beta V_t \\
 I_t &= \frac{V_t + A\beta V_t}{R_o} &
 \end{aligned}$$

$$\frac{V_t}{I_t} = R_{of} = \frac{R_o}{1 + A\beta}$$

VCCS:

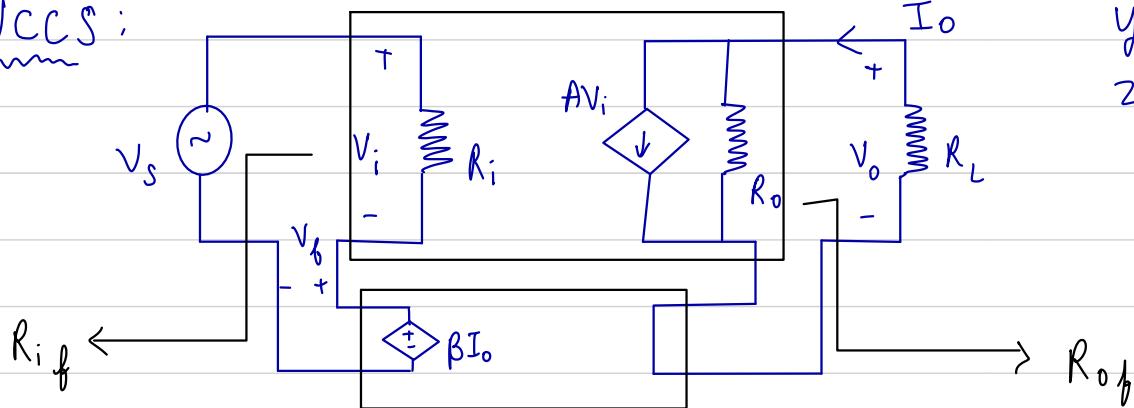

$y \text{ N/w}$
 $z \text{ f B}$

i/p o/p
Series - Series Feedback
current - series feedback
o/p i/p

($V_s - V_f$ are in series)
current - voltage feedback
o/p i/p

$$\text{Gain: } A_f = \frac{I_o}{V_s}$$

$$I_o = AV_i = A(V_s - V_f)$$


$$I_o = A(V_s - \beta I_o) \Rightarrow I_o(1 + A\beta) = V_s A$$

$$\therefore A_f = \frac{A}{1 + A\beta}$$

$$\text{Input impedance: } R_{if} = \frac{V_s}{I_i} = \frac{V_i + V_f}{I_i} = \frac{V_i + \beta I_o}{I_i} = \frac{V_i + A\beta V_i}{I_i}$$

$$R_{if} = R_i(1 + A\beta)_{\parallel}$$

Output impedance:

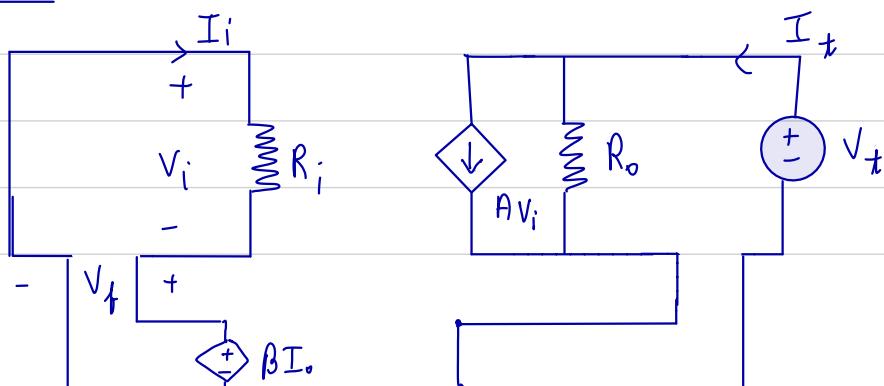

$$R_{of} = \frac{V_t}{I_t}$$


$$V_i = -V_f = -\beta I_o = -\beta I_t$$

$$V_t = (I_t - A V_i) R_o$$

$$V_t = (I_t + A \beta I_t) R_o$$

$$\therefore \frac{V_t}{I_t} = R_{of} = R_o (1 + A \beta)$$

CCVS:

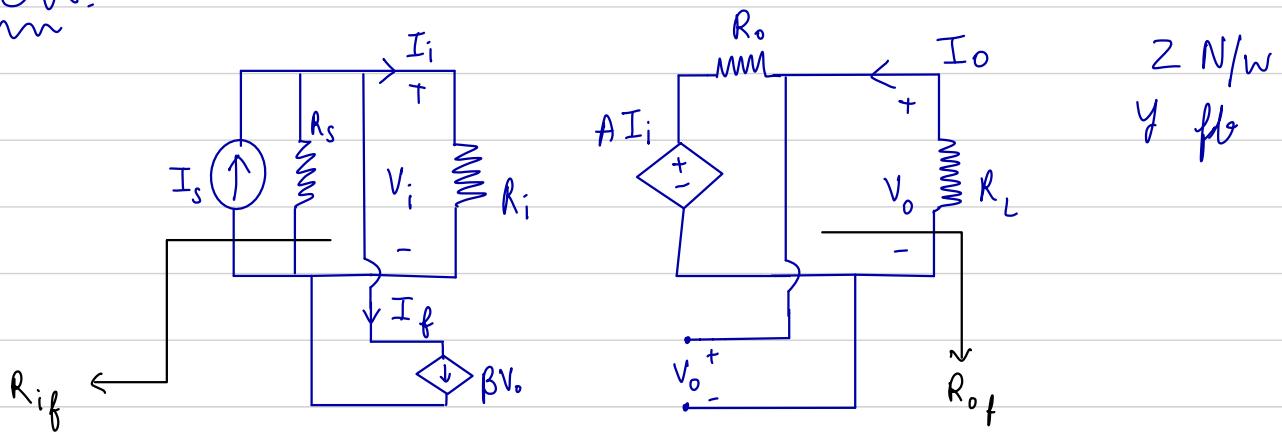



$$\text{Gain: } A_f = \frac{V_o}{I_s} = \frac{V_o}{I_i + I_f} = \frac{V_o}{I_i + \beta V_o} = \frac{V_o}{I_i + A \beta I_i}$$

$$A_f = \frac{A}{1 + A \beta}$$

$$\text{Input impedance: } R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_f + I_i} = \frac{V_i}{I_i + \beta V_o} = \frac{V_i}{I_i (1 + A \beta)}$$

$$R_{if} = \frac{R_i}{1 + A \beta}$$

Output impedance:

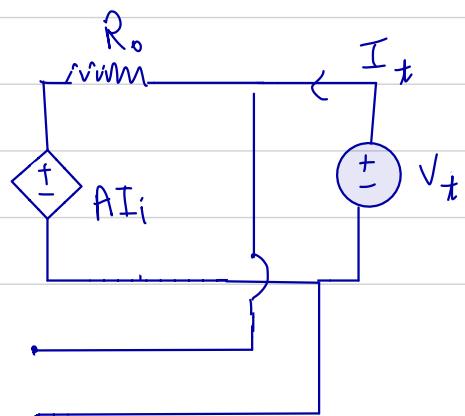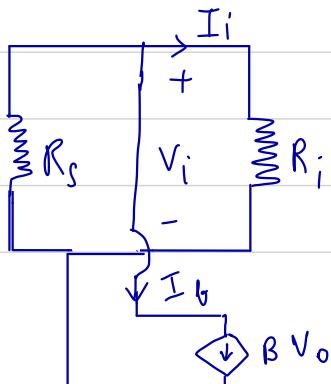

$$R_{o_f} = \frac{V_o}{I_o}$$

$$I_o = \frac{V_o - A I_i}{R_o}$$


$$I_s = 0 \Rightarrow I_i + I_f = 0 \Rightarrow I_i = -I_f \Rightarrow I_i = -\beta V_o = -\beta V_t$$

$$I_o = \frac{V_o (1 + A\beta)}{R_o}$$

$$\therefore R_{o_f} = \frac{R_o}{1 + A\beta}$$

Q VC VS of a stable gain of 2 should be designed.
Design a suitable feedback amplifier if VC VS
is represented by following matrix.
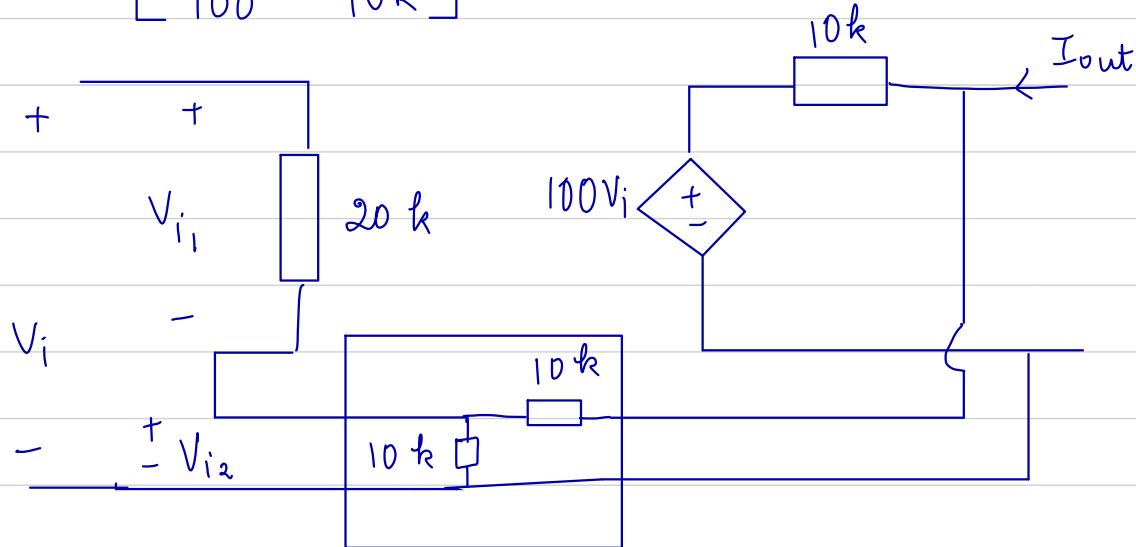
$$g = \begin{bmatrix} 1 & 0 \\ \frac{1}{20k} & 0 \\ 100 & 10k \end{bmatrix}$$



Feedback network

$$\frac{A}{1 + A\beta} \approx \frac{1}{\beta} = 2 \quad \beta = 0.5$$

$$h_i = \left| \frac{V_i}{I_i} \right| = 20k + (10k \parallel 10k) = 25k \Omega_{\parallel}$$

$$V_o = 0$$

$$h_f = \left| \frac{I_{out}}{I_i} \right| \quad V_o = 0$$

$$I_{out} = \frac{100V_i}{10k} + \frac{V_i/25k}{2}$$

$$I_i = \frac{V_i}{25k}$$

$$\frac{I_{out}}{I_i} = -250 \cdot 5_{\parallel} = h_f \parallel$$

$$h_n = \left| \frac{V_o}{V_i} \right|_{I_i=0} = \frac{1}{2} = 0.5 \parallel$$

$$h_o = \left| \frac{I_o}{V_o} \right|_{I_i=0} = \frac{1}{20 \parallel 10} = 1.5 \times 10^{-4} S_{\parallel}$$

$$[jh] = \begin{bmatrix} 25k & 0.5 \\ -250.5 & 1.5 \times 10^{-4} \end{bmatrix}$$

$\frac{h_n h_f}{h_i h_o}$ should be -ve for negative feedback.

$$\frac{h_n h_f}{h_i h_o} = -33.4 \parallel$$

$$h_i h_o$$

composite g parameters $[g] = [h]^{-1}$


$$g = \begin{bmatrix} \frac{1.5 \times 10^{-4}}{129} & \frac{-0.5}{129} \\ \frac{250.5}{129} & \frac{25k}{129} \end{bmatrix}$$

$$\text{I/p impedance} = R_{if} = \frac{129}{1.5 \times 10^{-4}} = 860 \text{ k}\Omega$$




$$\text{o/p impedance} = R_{of} = \frac{25k}{129} = 193.8 \Omega_{\parallel}$$

$$g_f = 1.94 \parallel$$

OPERATIONAL AMPLIFIERS

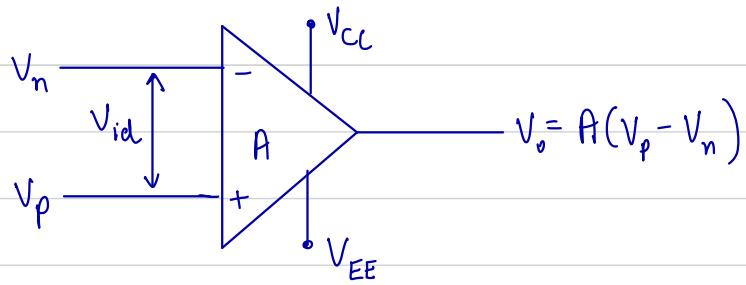

Equivalent circuit

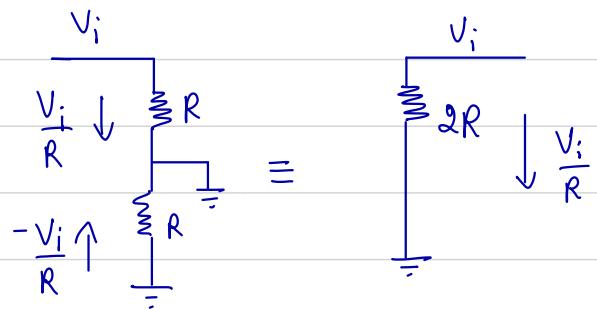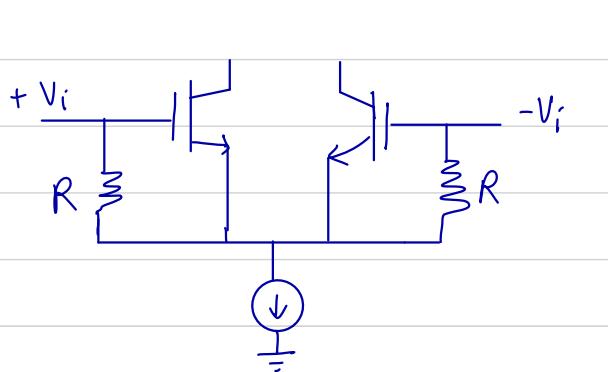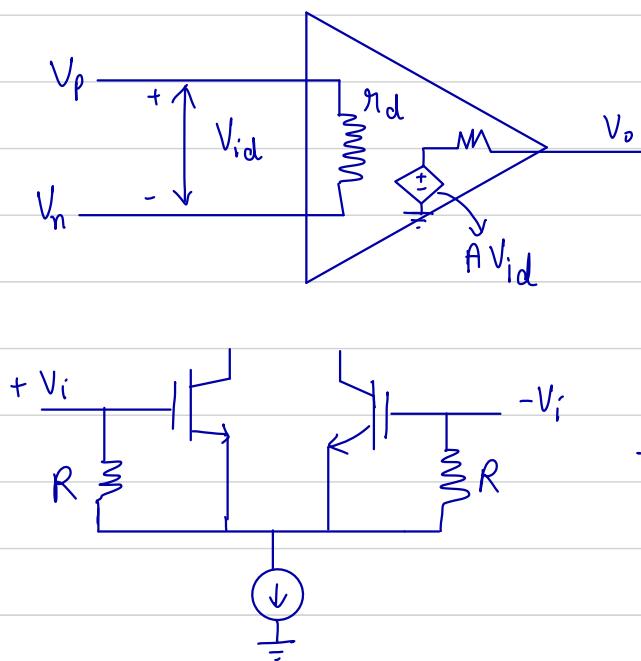


$$\text{Generally } r_d = R_i = 2M\Omega$$

$$A = 200 \text{ V/mV}$$

$$r_o \approx 75 \Omega$$

$$I_L = \pm 25 \text{ mA}$$

Ideal opamp model

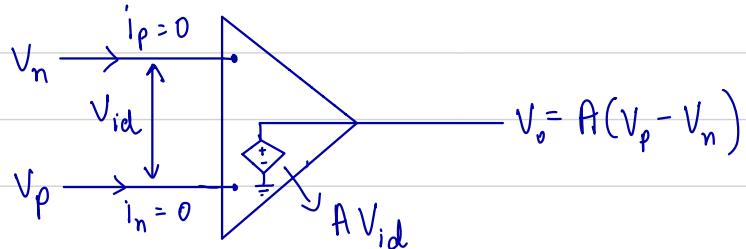

Basic architecture of Op-Amp



or
Emitter follower
Source follower
Push-pull Amp

Requirement of OP-Amp

1> Infinite open loop gain ($10^5 - 10^6$)

2> Infinite input impedance

3> Zero output impedance

4> Infinite bandwidth

5> Zero offset voltage

6> Zero bias & offset currents

Input offset current, $I_{io} = |I_{Bp} - I_{Bn}|$

I_B (Bias current) = $\frac{I_{Bp} + I_{Bn}}{2}$

7> Slew rate must be ∞

$$\text{Slew rate} = \frac{dV_{out}}{dt}$$

(For IC741, SR = 0.5 V/ μ s)

8> Common mode rejection ratio (CMRR) must be very high

$$V_{out} = A(V_p - V_n) + A_{cm} V_{cm}$$

Q) Determine the output voltage of an opamp for input voltages, $V_{i1} = 300 \mu V$, $V_{i2} = 240 \mu V$. Amplifier has differential gain of 5000. Value of CMRR are: a) 100 b) 10^5

Ans

$$CMRR = \frac{A_{dm}}{A_{cm}}$$

$$V_{dm} = V_{i1} - V_{i2}$$

$$V_{dm} = 60 \mu V$$

$$V_{cm} = \frac{V_{i1} + V_{i2}}{2}$$

$$V_{cm} = 270 \mu V$$


$$a) A_{cm} = \frac{A_{dm}}{CMRR} = 50$$

$$\begin{aligned} V_o &= V_{dm} A_{dm} + V_{cm} A_{cm} \\ &= 0.316 V \end{aligned}$$

$$b) A_{cm} = 0.5$$


$$\begin{aligned} V_o &= V_{dm} A_{dm} + V_{cm} A_{cm} \\ &= 0.3 V \end{aligned}$$

Transfer characteristic of OPAMP

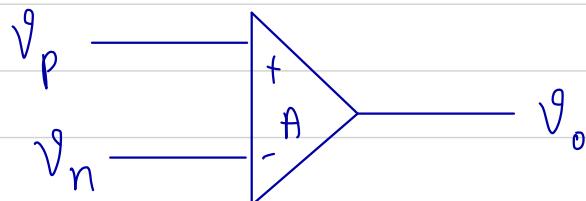

$$\begin{aligned} V_o &= A(V_p - V_n) \\ &= A V_{dm} \end{aligned}$$

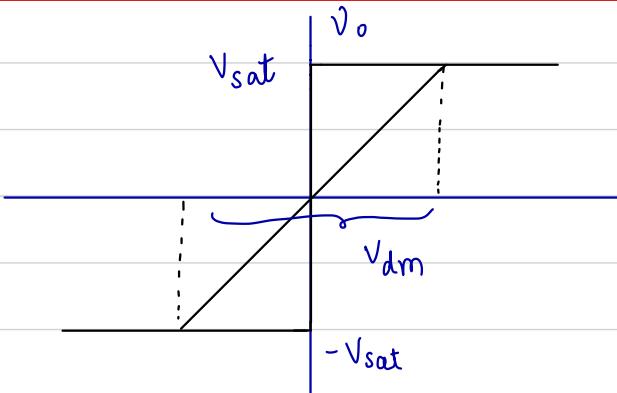
as $A \rightarrow \infty$, V_o is finite $\therefore V_p - V_n = 0$ i.e. $V_{dm} = 0$



It means when V_o is finite & A is infinite V_{dm} is zero $\Rightarrow V_p = V_n$. $\therefore V_p$ & V_n are virtually short.

V_o can be finite only in negative feedback.


In negative feedback: (voltage follower)

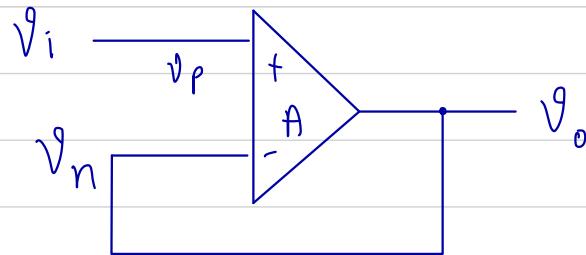

$$V_o = A (V_p - V_n)$$


$$V_o = A (V_i - V_o)$$
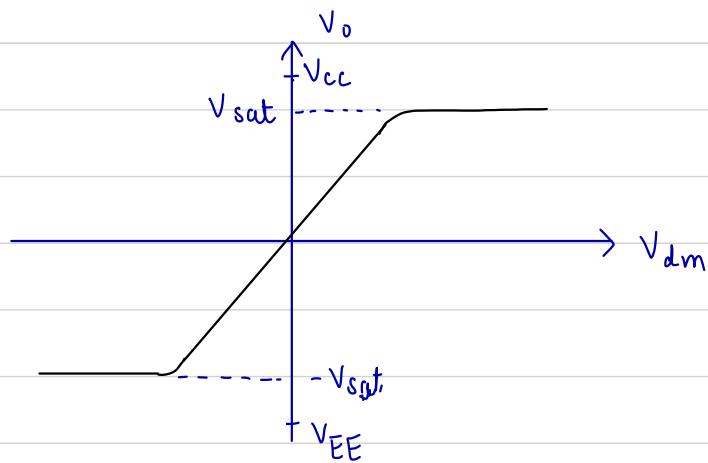
$$\frac{V_o}{V_i} = \frac{A}{1+A} \approx 1$$




It acts as a buffer


Voltage crossover detector:

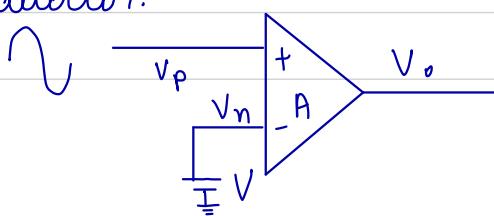
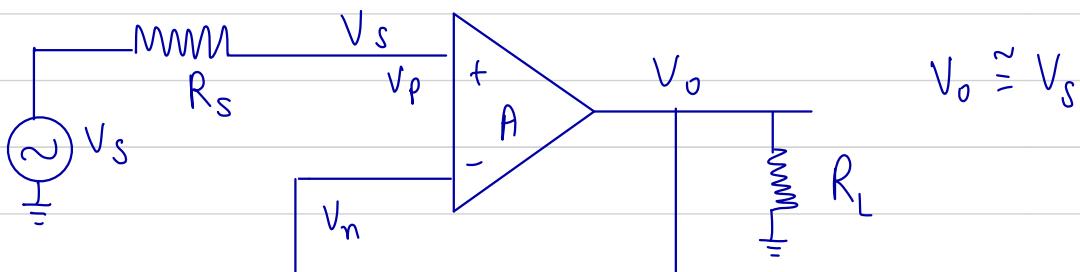
$$V_o = \begin{cases} V_{sat}, & V_p > V \\ -V_{sat}, & V_p < V \end{cases}$$



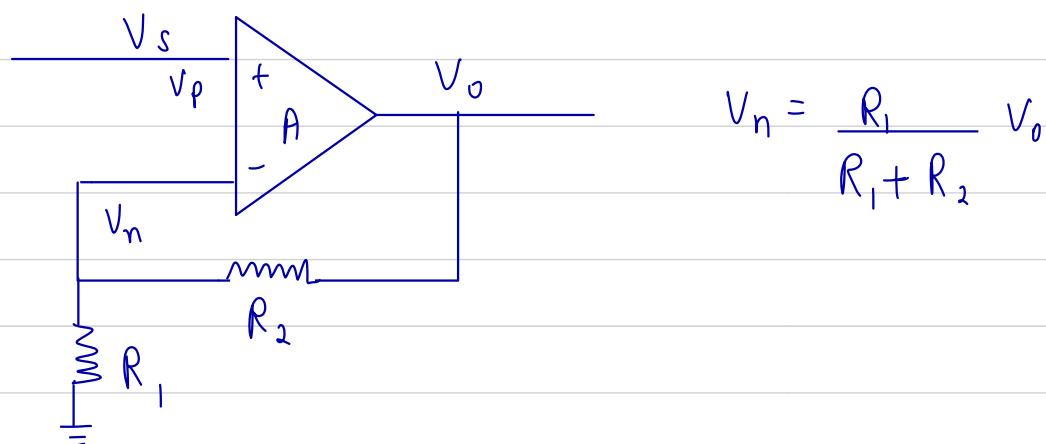- If V_o is +ve then OPAMP is current source with max current = $\pm 25 \text{ mA}$
- If V_o is -ve then OPAMP absorbs current with max current = $\pm 25 \text{ mA}$.
- $V_o = \frac{R_L}{R_s + R_L} V_s$




$$V_o = A[V_p - V_n] \Rightarrow V_o = A \left[V_i - \frac{R_1}{R_1 + R_2} V_o \right]$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{A}{1 + \frac{A R_1}{R_1 + R_2}}$$


If $V_p = V_n \Rightarrow V_i = V_o \frac{R_1}{R_1 + R_2}$ then $\frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$
i.e. ($A \rightarrow \infty$)

The name circuit can be written as:

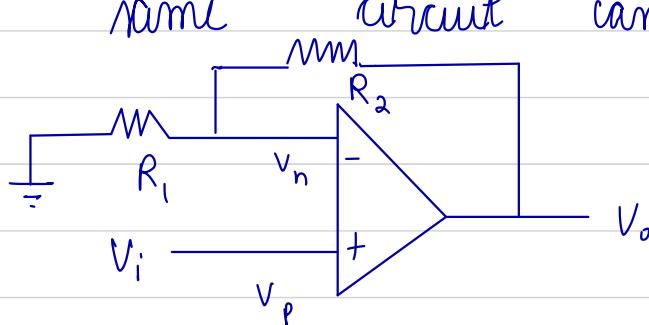

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$

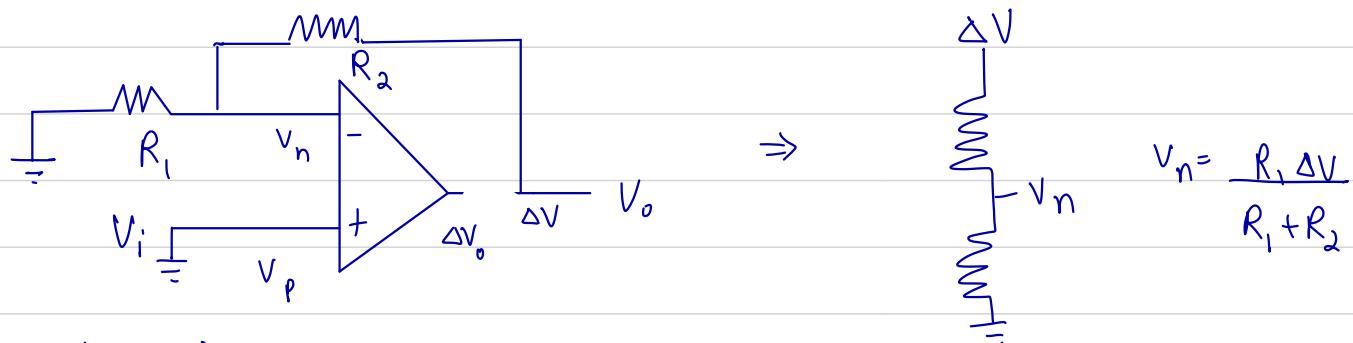
How To check if we have negative feedback



$$\Delta V_o = A(V_o - V_n)$$


So as $\Delta V \uparrow$ $\Delta V_o \downarrow$ in negative feedback
In positive feedback as $\Delta V \uparrow$, ΔV_o also increases.

equivalent circuit

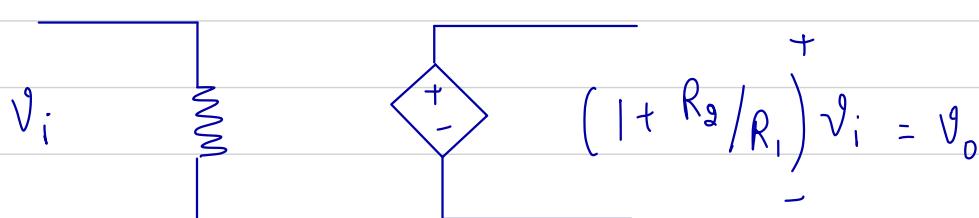

Frequency response : $|H|_{dB}$ \uparrow ω_u \leftarrow open loop

$$20 \log(10^5) = 100 \text{ dB}$$

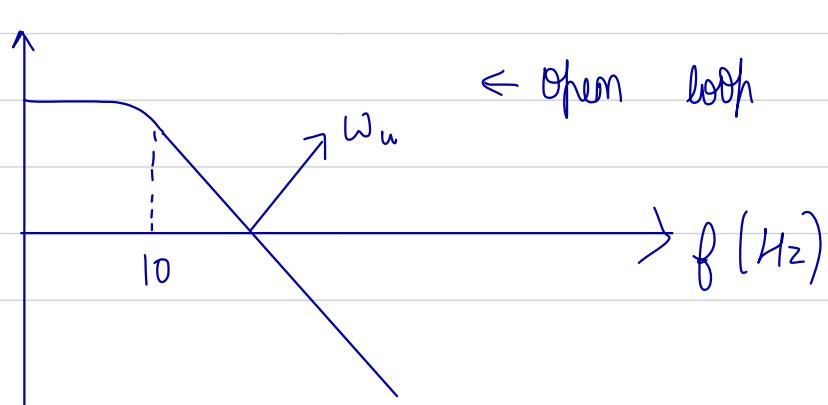


$$\frac{A_0}{1 + \frac{j\omega}{\omega_0}} = H$$

$$|H| = 1 \Rightarrow \frac{A_0^2}{1 + \left(\frac{\omega}{\omega_0}\right)^2} = 1$$

$$A_0^2 - 1 = \left(\frac{\omega}{\omega_0}\right)^2 \Rightarrow \omega = \omega_0 \sqrt{A_0^2 - 1}$$

$$\omega_u \text{ (unit gain frequency)} \approx A\omega_0 /$$

For negative feedback:

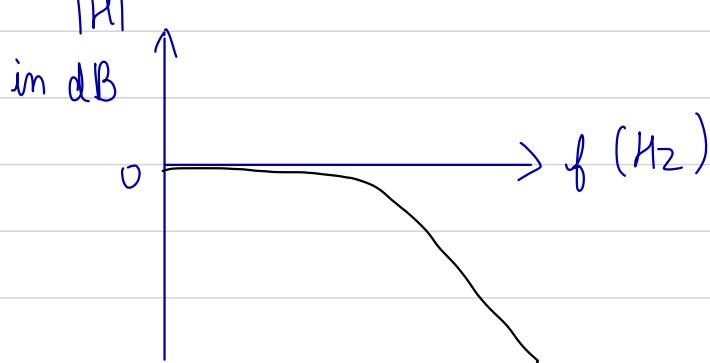

$$A_f = \frac{A_0}{1 + \frac{1}{\omega_0}} = \frac{A_0}{1 + \frac{A_0 \beta}{1 + \frac{1}{\omega_0}}} = \frac{A_0}{1 + A_0 \beta + \frac{A_0}{\omega_0}} = \frac{A_0}{1 + \frac{A_0}{\omega_0(1 + A_0 \beta)}}$$

$$\therefore A_0 \rightarrow \frac{A_0}{1 + A_0 \beta}; \quad \omega_0 \rightarrow \omega_0 (1 + A_0 \beta)$$

Q> What is bandwidth / Draw frequency response for an non-inverting amplifier of gain 5 & bandwidth 10 Hz.


Ans

$$\text{Gain} = 5 = A'$$


$$\beta = \frac{1}{5}$$

$$\omega' A' = \omega_0 A_0$$

$$\omega' = \frac{10^6}{5} = 200 \text{ kHz},$$

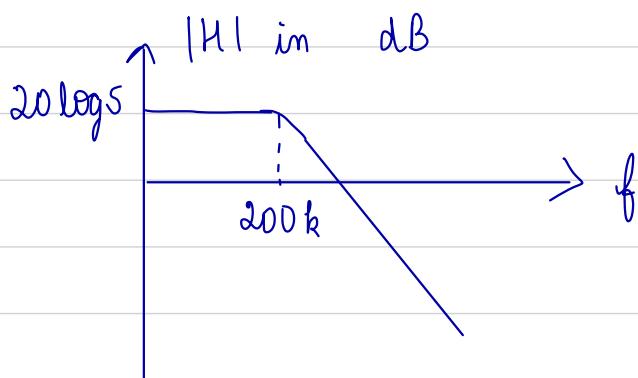

Expt 6

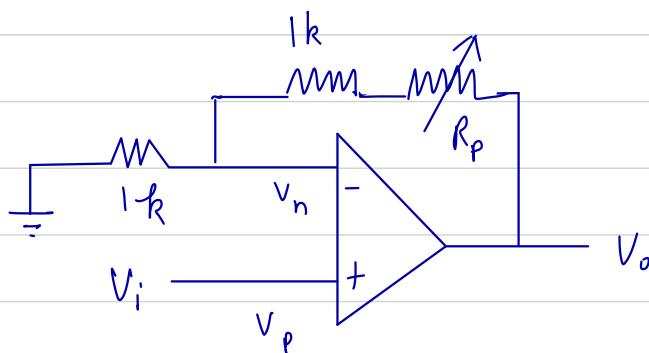


$$A = \left(1 + \frac{1+R_p}{1} \right) = 2+R_p$$


$$\text{Gain} \Rightarrow 2 \text{ to } 10 \Rightarrow 2 < A < 10$$

when gain = 2	$R_p = 0$
= 6	$R_p = 4 \text{ k}\Omega$
= 10	$R_p = 8 \text{ k}\Omega$

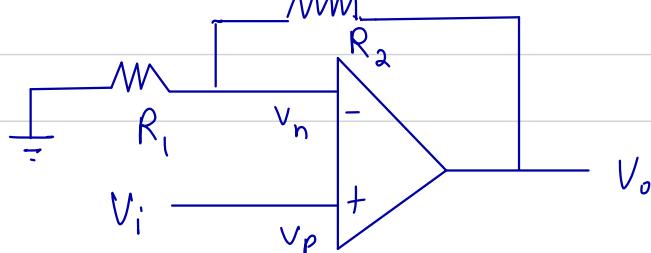Bias current into 741 opamp input $\approx 80 \text{ nA}$


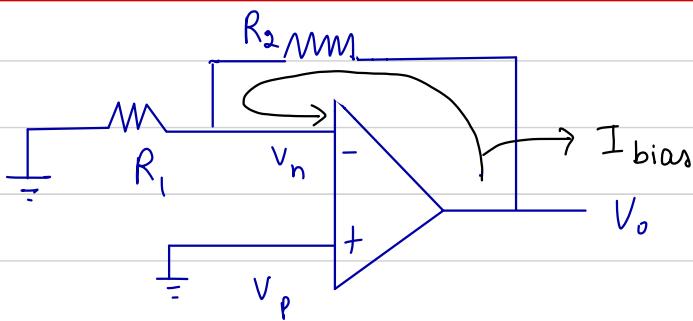
$$V_o = \left(1 + \frac{R_2}{R_1} \right) V_i + I_{\text{Bias}} R_2$$



To observe effect of I_{bias} we connect V_p to ground.


$$\rightarrow V_n \text{ becomes virtually ground} \Rightarrow V_n = 0$$

Observe DC shift for $R_2 = 10 k\Omega, 1M\Omega, 10 M\Omega$

$$\therefore I_{bias} = \frac{\text{DC shift}}{10 M\Omega} \approx 80 \text{nA}$$

$$= \frac{\text{DC shift} - 2 \times (\text{DC of } V_{in})}{10 M\Omega} \approx 80 \text{nA}$$

To remove the effect of I_{bias} :

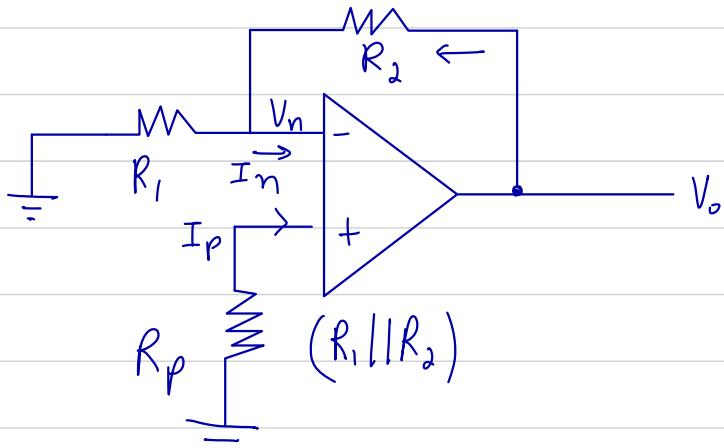

$$\frac{O - V_p}{R_p} = I_p$$

$$V_p = -I_p R_p$$

$$\frac{O - V_p}{R_1} + \frac{E_o - V_p}{R_2} = I_n$$

where E_o is the voltage due to bias current

$$E_o = I_n R_2 + \frac{V_n R_2}{R_1} + V_n$$


$$E_o = I_n R_2 - I_p \frac{R_p R_2}{R_1} - I_p R_p$$

$$\begin{aligned}
 &= I_n R_2 + \left(1 + \frac{R_2}{R_1}\right) (-I_p R_p) \\
 &= \left(1 + \frac{R_2}{R_1}\right) \left(-I_p R_p + \frac{I_n R_2 R_1}{R_1 + R_2}\right) \\
 &= \left(1 + \frac{R_2}{R_1}\right) \left(-I_p R_p + I_n (R_1 || R_2)\right) \\
 \Rightarrow R_p &= R_1 || R_2
 \end{aligned}$$

Slew rate limitation

$$\text{Slew rate} = \frac{dV_o}{dt} \Big|_{\text{max}}$$

For voltage buffer

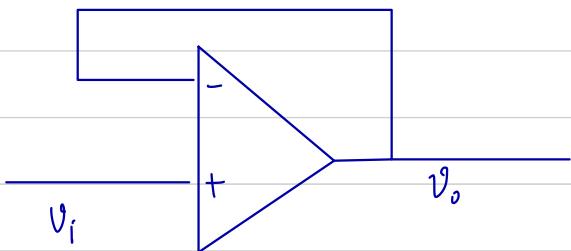

$$\begin{aligned}
 V_i &= V_m \sin \omega t & V_o &= V_m \sin \omega t \\
 \frac{dV_o}{dt} &= V_m \omega \cos \omega t & \frac{dV_o}{dt} \Big|_{\text{max}} &= V_m \omega
 \end{aligned}$$

$$\text{Slew rate} = 2\pi f V_m \text{ V/}\mu\text{s} = \frac{2\pi f V_m}{10^6} \text{ V/}\mu\text{s}$$

Q> An amplifier is to be designed for a gain of 5 using opamp. Input has an amplitude of 200 mV and bandwidth of 20 kHz. Find slew rate required for the opamp

$$\text{Ans } SR = \frac{2\pi f \cdot V_m}{10^6}$$

$$V_m = 5 \times 200 \text{ mV} = 1 \text{ V}$$

$$\Rightarrow SR = \frac{2\pi \times 20 \text{ kHz} \times 1}{10^6} = 0.1256 \text{ V/}\mu\text{s}$$

Q> A voltage buffer is to be designed using opamp. It is expected to operate for frequencies in the range 10 kHz to 100 kHz. The swing in voltage is in the range of 1V pk-pk to 20V pk-pk. The error between i/p & o/p in amplification / buffering has to be less than 0.01%. what are the op-amp specifications required to get desired performance (Find A_o , ω_o , ω_u , SR)

$$\text{Ans } \frac{|V_o - V_{in}|}{V_{in}} \leq \frac{0.01}{100}$$

$$\frac{|V_{in} - V_o|}{V_{in}} = 1 - \frac{|V_o|}{V_{in}} = 1 - \frac{A_o}{1 + A_o} = \frac{1}{1 + A_o} \leq \frac{0.01}{100}$$


$$100 \leq 0.01 + 0.01 A_o$$

$$\Rightarrow A_o \geq 10^4 - 1,$$

$$\omega_u > (2\pi \times 100 \text{ kHz}) \text{ rad/sec}$$

$$\omega_o > \frac{\omega_u}{A_o} \Rightarrow \omega_o > \frac{2\pi \times 100 \text{ kHz}}{10^4 - 1} = 62.8 \text{ rad/sec}$$

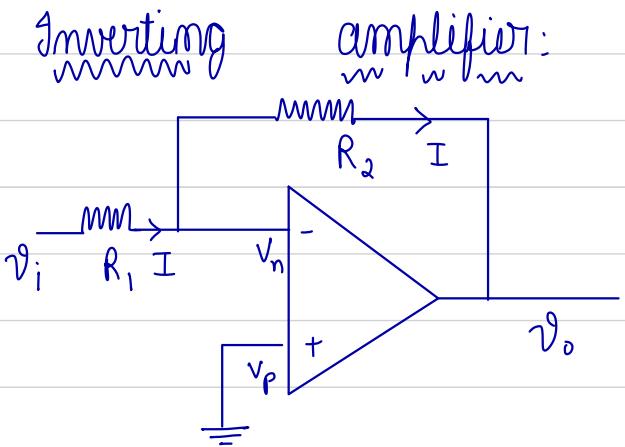
$$SR > \frac{2\pi f V_m}{10^6} = \frac{2\pi \times 100 \text{ kHz} \times 10}{10^6} = 2\pi \text{ V/}\mu\text{s}$$




$$\frac{v_i - v_n}{R_1} = \frac{v_n - v_o}{R_2} \quad v_n \approx 0$$

$$\Rightarrow \frac{v_i}{R_1} = -\frac{v_o}{R_2} \quad \Rightarrow \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

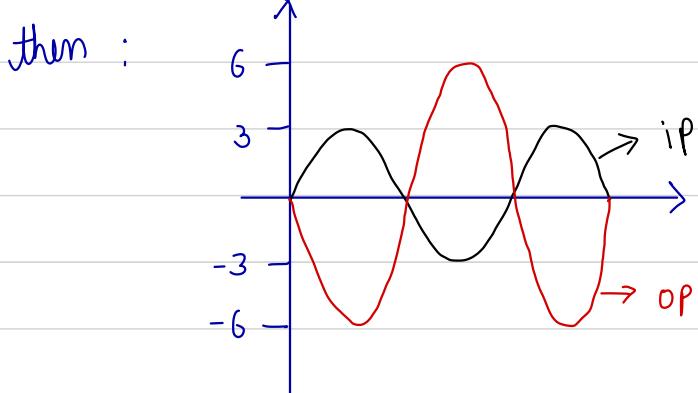
If $v_i = 6 \text{ V p-p}$ and $\frac{R_2}{R_1} = 2$



Equivalent circuit

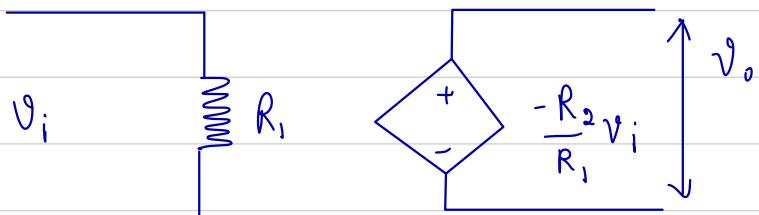

Miller's theorem

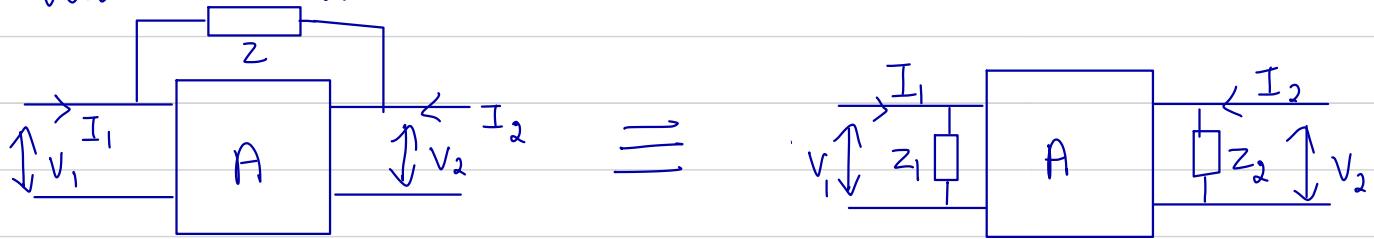

$$\text{i) } \frac{V_1 - V_2}{Z} = I_1 = \frac{V_1}{Z_1}$$

$$\frac{V_1}{Z} \left[1 - \frac{V_2}{V_1} \right] = \frac{V_1}{Z_1}$$

$$\frac{1}{Z} [1 - A] = \frac{1}{Z_1} \Rightarrow$$

$$Z_1 = \frac{Z}{1 - A}$$



$$\text{ii) } \frac{V_2 - V_1}{Z} = I_2 = \frac{V_2}{Z_2}$$

$$\frac{V_2}{Z} \left[1 - \frac{V_1}{V_2} \right] = \frac{V_2}{Z_2}$$

$$\frac{1}{Z} \left[1 - \frac{1}{A} \right] = \frac{1}{Z_2} \Rightarrow$$

$$Z_2 = \frac{A_2}{A - 1}$$


In inverting amplifiers:

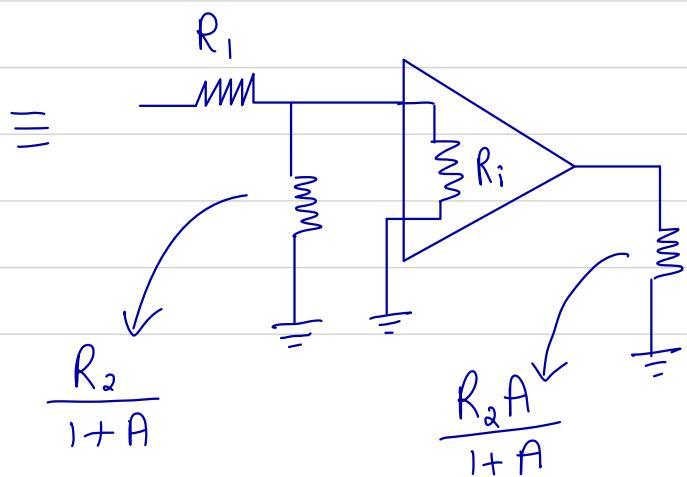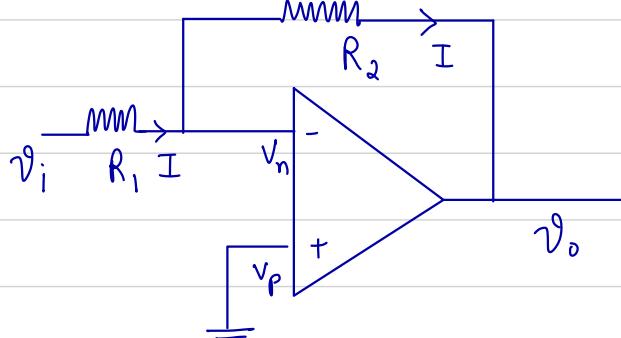

$$R_{if} = R_i + \left(\frac{R_2}{1+A} \parallel R_i \right)$$

$$R_{if} \approx R_i$$

Summing Amplifiers (Inverting adder)

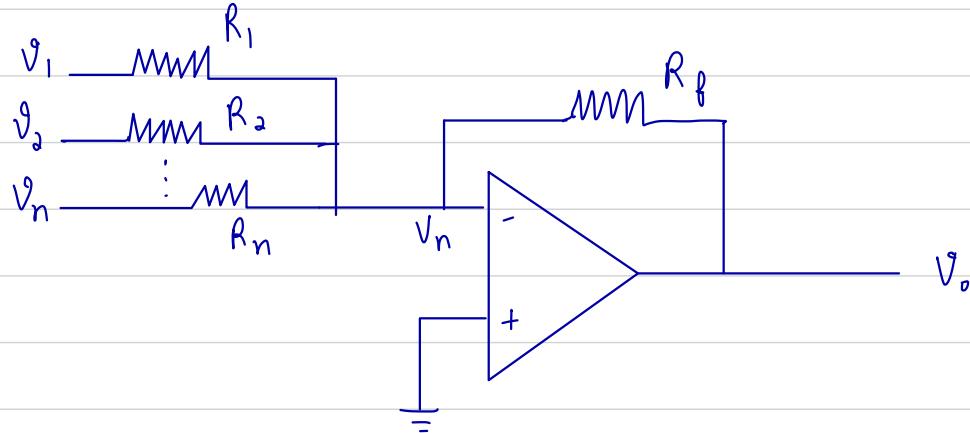

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} = -\frac{V_o}{R_f}$$


$$V_o = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots + \frac{V_n}{R_n} \right]$$

$$\text{If } R_1 = R_2 = \dots = R_n = R$$

$$V_o = -\frac{R_f}{R} [V_1 + V_2 + \dots + V_n]$$

To make it positive pass V_o to another inverting amplifier.

Ex: Find V_o

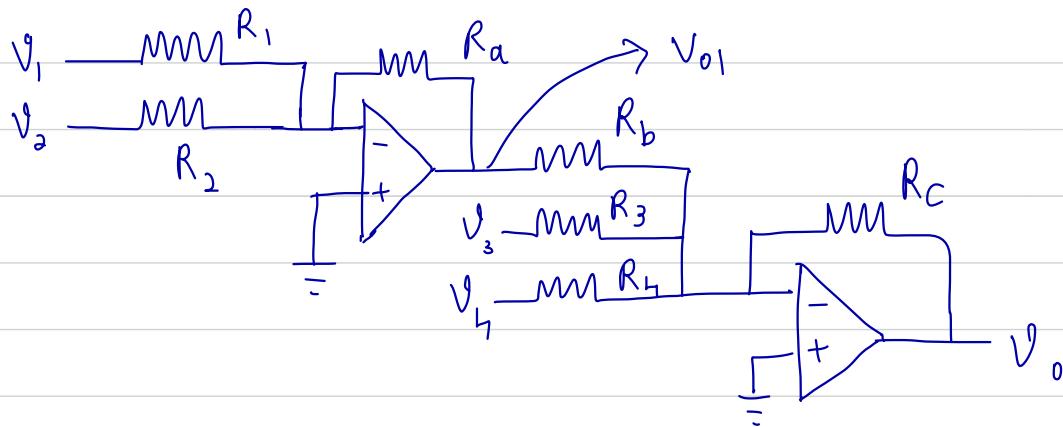

Ans

$$V_{01} = -R_a \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} \right]$$

$$V_0 = -R_c \left[-\frac{R_a}{R_b} \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} \right] + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right]$$


$$V_0 = V_1 \left(\frac{R_a}{R_1} \right) \left(\frac{R_c}{R_b} \right) + V_2 \left(\frac{R_a}{R_2} \right) \left(\frac{R_c}{R_b} \right) - V_3 \left(\frac{R_c}{R_3} \right) - V_4 \left(\frac{R_c}{R_4} \right)$$

Ex2 Design an opamp band circuit to implement the following function:


$$V_0 = 6V_1 + 3V_2 - V_3 - 2V_4.$$

Ans Assume that only $10\text{ k}\Omega$ resistors are available.

Let $R = 10\text{ k}\Omega$

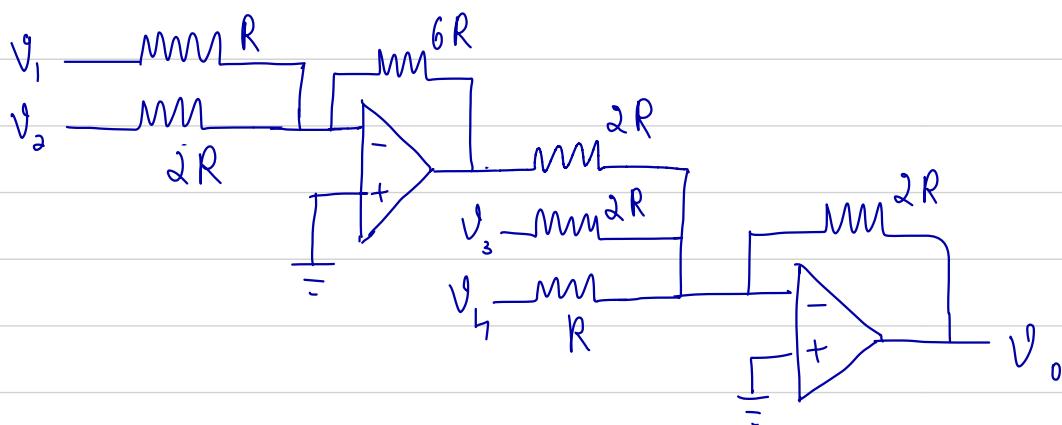

3>

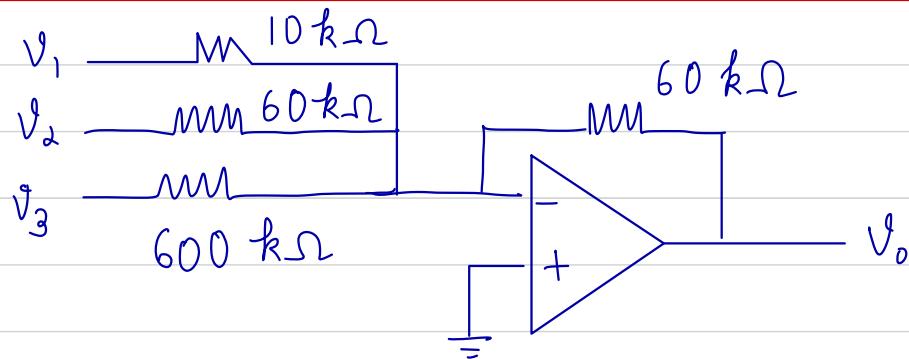


$$V_1 = \sin \omega t \quad V_2 = 5V \quad V_3 = -10V. \text{ Find } V_o.$$

Ans


$$V_{o1} = \frac{-60}{10} \sin \omega t = -6 \sin \omega t$$

$$V_{o2} = -5V$$

$$V_{o3} = 1V$$

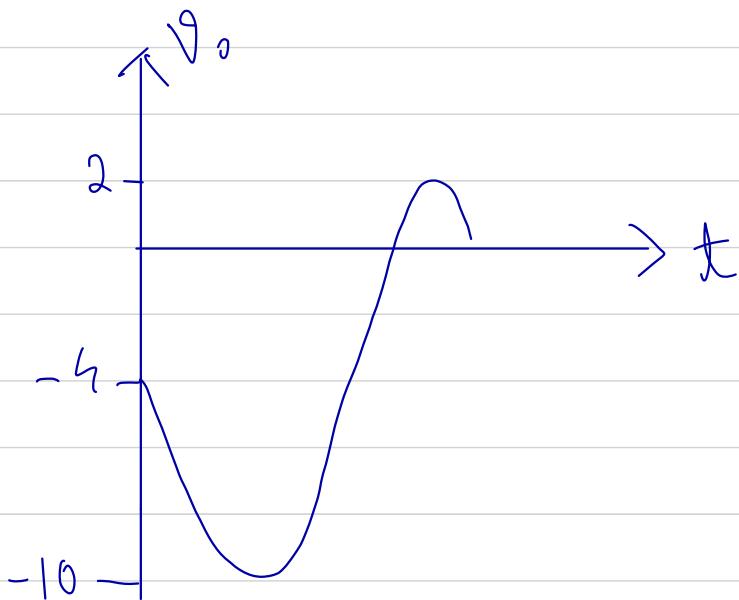


Digital to analog convertor (DAC)

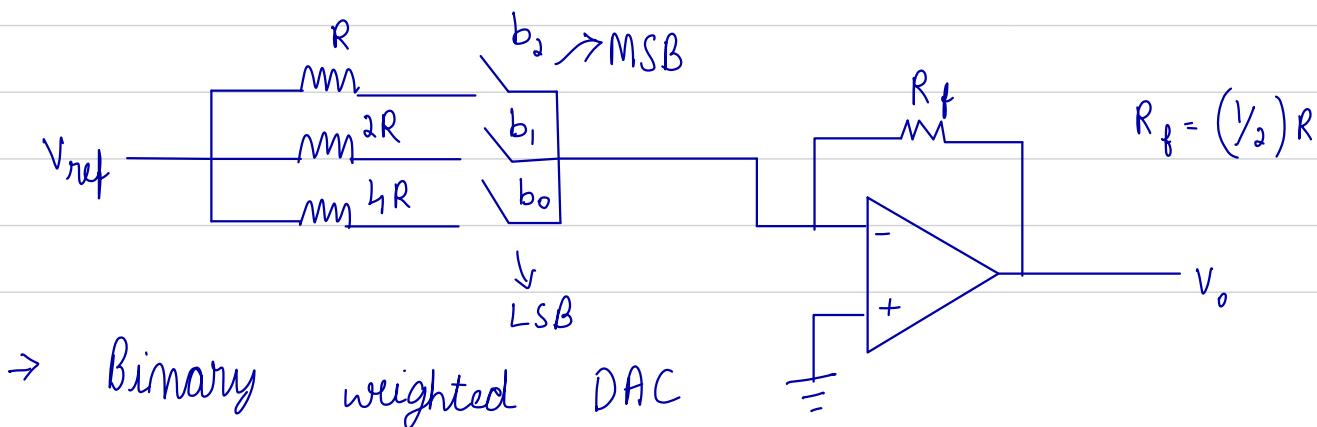

$$V_o = -R_f V_{ref} \left(\frac{b_2}{R} + \frac{b_1}{2R} + \frac{b_0}{4R} \right) = -V_{ref} \frac{R_f}{R} \left(\frac{b_2}{1} + \frac{b_1}{2} + \frac{b_0}{4} \right)$$


b_2	b_1	b_0	$V_o (V)$
0	0	0	0
0	0	1	$(1/8) \cdot V_{ref}$
0	1	0	$(2/8) \cdot V_{ref}$
0	1	1	$(3/8) \cdot V_{ref}$
1	0	0	$(4/8) \cdot V_{ref}$
1	0	1	$(5/8) \cdot V_{ref}$
1	1	0	$(6/8) \cdot V_{ref}$
1	1	1	$(7/8) \cdot V_{ref}$

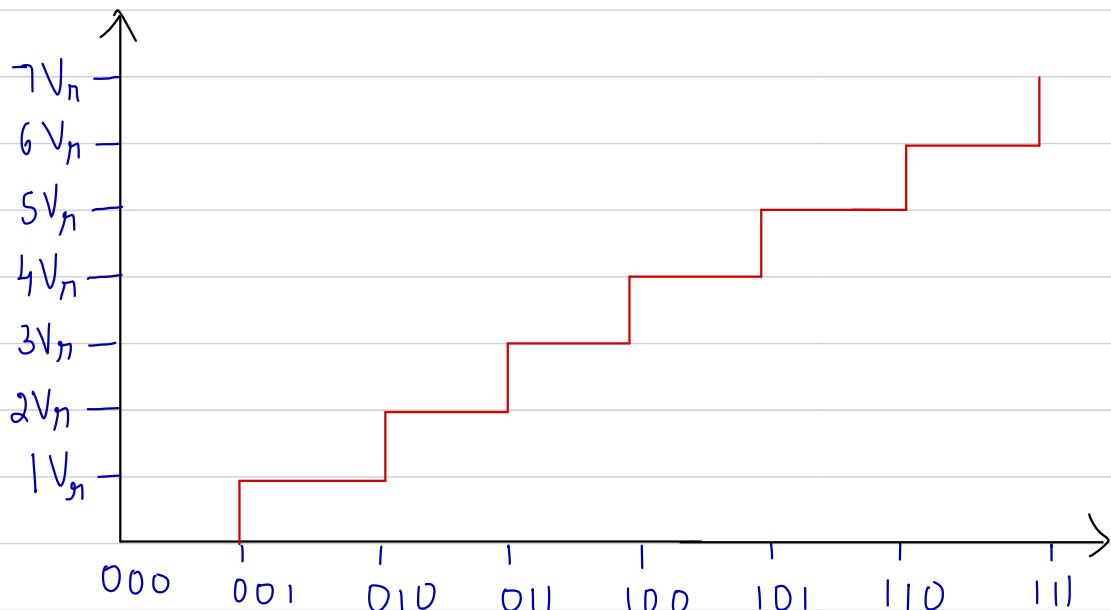

where $V_n = \frac{V_{ref}}{8}$


Max voltage = $V_{ref} \left(1 - \frac{1}{2^n} \right)$

Experiment 7 - Inverting adder

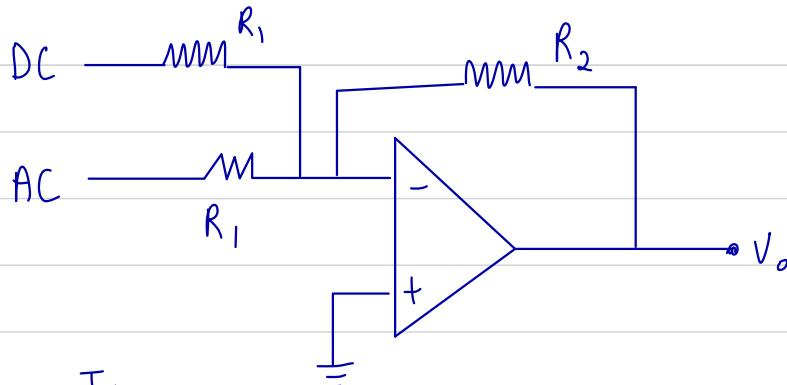

$$R_1 = R_2 = 10 \text{ k}\Omega$$

i>

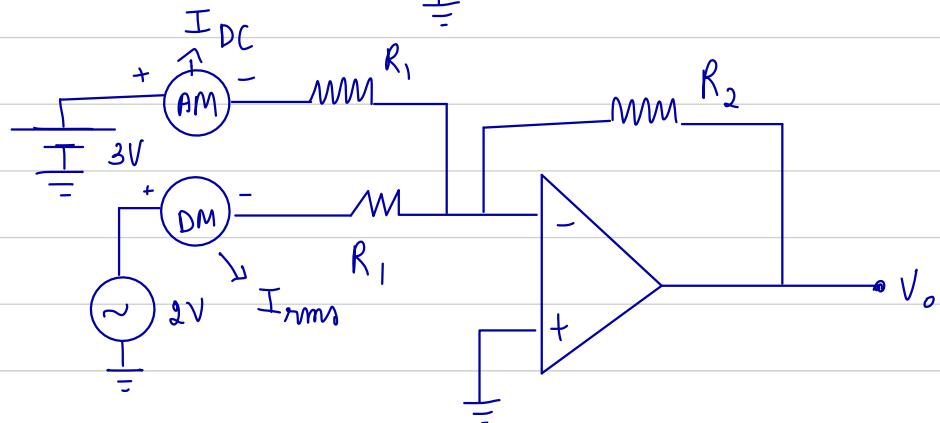


AM - Analog multimeter
DM - Digital multimeter


$$V_{rms} = \frac{2}{\sqrt{2}} = \sqrt{2} \text{ V}$$

Impedance sum = $\frac{\text{Voltage supplied to source}}{\text{current drawn from source}}$
(measured by multimeter)


ii>

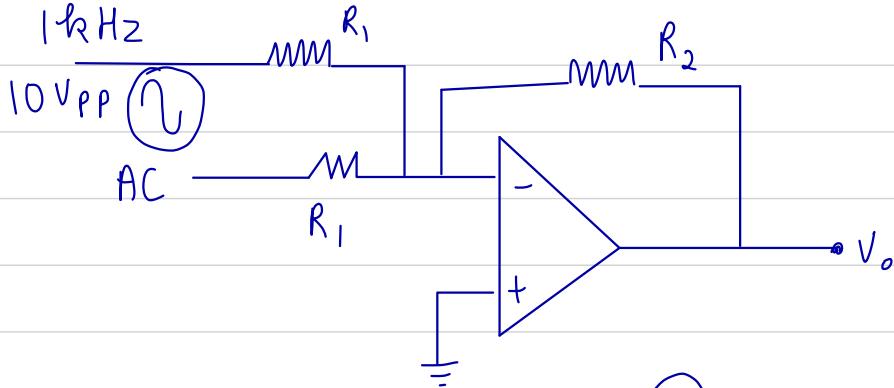

graph :

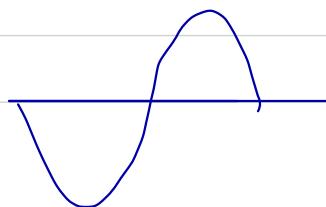

as frequency increases

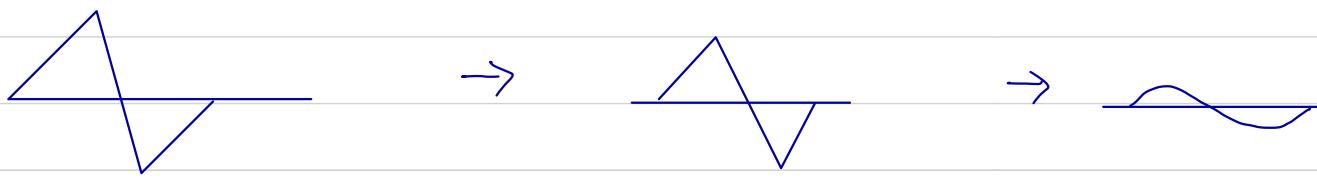


Slow rate limitation

$$0.5 \text{ V/}\mu\text{s} = \left(\frac{2\pi f V_o}{10^6} \right) \quad \text{find } f$$

Both system f & V_o contribute to o/p of distortionless

iii>

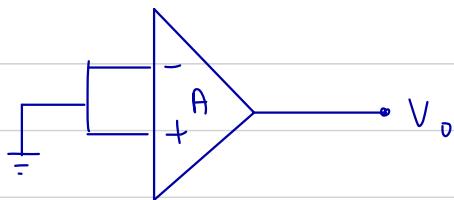


Sdually $V_o = 0$

$$\text{i.e. } A(V_+ - V_-) = 0$$


But $V_o = \pm V_{sat}$ due to small differences in V_+ & V_-

Non inverting adder

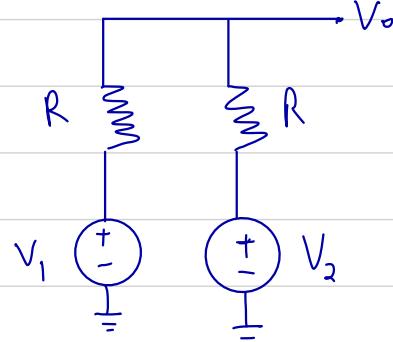


$$V_o = V_1 \frac{R}{R+R} + V_2 \frac{R}{R+R}$$

$$= \frac{V_1 + V_2}{2}$$

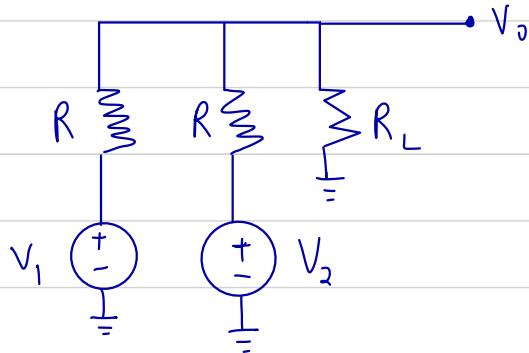

$$V_0 = \left(\frac{R_1 + R_L}{R_1 + (R_1 + R_L)} \right) V_1 + \left(\frac{R_2 + R_L}{R_2 + (R_1 + R_L)} \right) V_2$$

Using opamp:

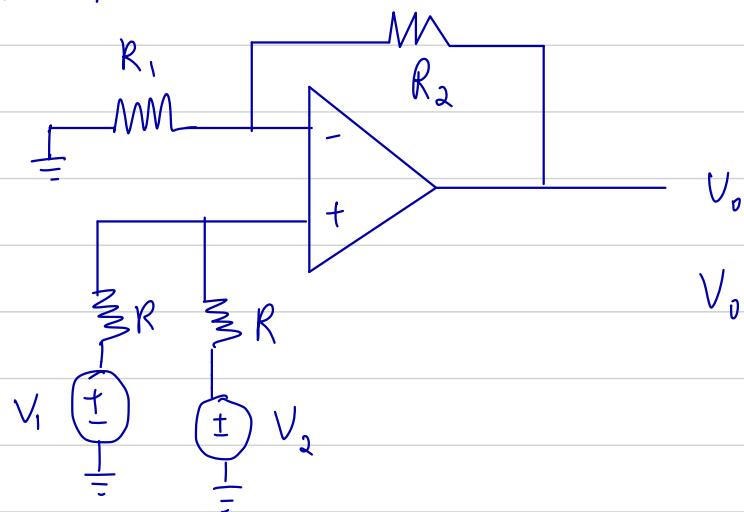

$$\begin{aligned} V_0 &= \left(1 + \frac{R_2}{R_1} \right) V_p \\ &= \left(1 + \frac{R_1}{R_1} \right) \left(\frac{V_1 + V_2}{2} \right) \end{aligned}$$

Q) For 741 opamp, calculate typical result from a 80 mV common input voltage

Ans

$$A_d = 2 \times 10^5 \quad SR = 0.5 \text{ V/}\mu\text{s} \quad CMRR = 90 \text{ dB}$$

$$V_{icm} = 80 \text{ mV} \quad V_{o,cm} = ?$$

$$CMRR = \frac{A_d}{A_{cm}} = \frac{A_d}{\left(\frac{V_{ocm}}{V_{icm}} \right)} = \frac{2 \times 10^5}{V_{ocm}}$$

$$\therefore 90 = 20 \log \left(\frac{16 \times 10^3}{V_o} \right) \quad V_o = \frac{16 \times 10^3}{10^{h.s}} = 0.5059 \text{ V}$$

Q> An opamp has $A = 10^5 \text{ V/V}$ $R_i \approx \infty$ $R_o \approx \infty$

Find the following:

a) V_o if $V_1 = 870 \mu\text{V}$, $V_2 = 975.2 \mu\text{V}$

b) V_1 if $V_2 = V_o = 6\text{V}$

c) V_2 if $V_1 = 0\text{V}$, $V_o = -7\text{V}$

d) V_2 if $V_1 = -V_o = 2\text{V}$

Ans

$$A(V_1 - V_2) = V_o$$

a) $V_o = 10^5(870 - 975.2) \times 10^{-6} = -10.52 \text{ V}_o$

b) $6 = 10^5(V_1 - 6)$

$$\Rightarrow V_1 - 6 = 6 \times 10^{-5}$$

$$\therefore V_1 = 6 + 6 \times 10^{-5} = 6.00006 \text{ V}_1$$

c) $-7 = 10^5(0 - V_2)$

$$V_2 = 7 \times 10^{-5} = 70 \mu\text{V}_2$$

d) $-2 = 10^5(2 - V_2)$

$$V_2 - 2 = 2 \times 10^{-5}$$


$$V_2 = 2 + 2 \times 10^{-5} = 2.00002 \text{ V}_2$$

Q> An opamp with open loop gain 2×10^5 , R_i of $1 \text{ M}\Omega$, and R_o of $75 \text{ }\Omega$, drives load resistance of $2.5 \text{ k}\Omega$. Write the equivalent circuit indicating all these values. Also find the current through & voltage across R_i & R_o .

If: i) $V_1 = 1\text{V}$ $V_o = 5\text{V}$

ii) $V_1 = 5\text{mV}$ $V_o = 6\text{V}$

each case.

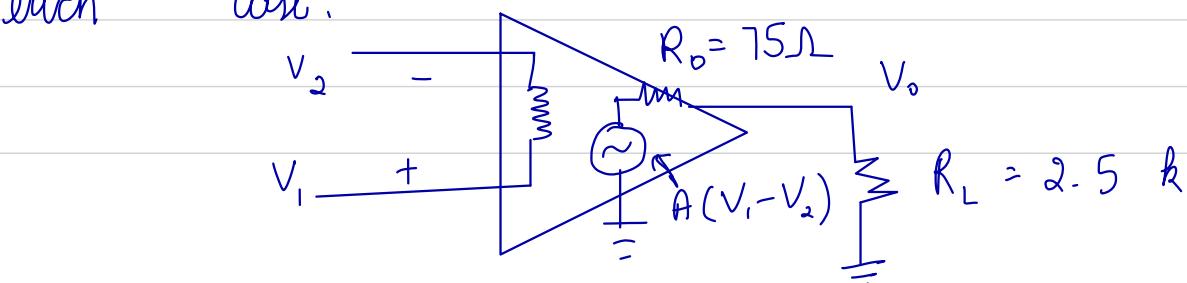

Ans

$$i_{R_o} = \frac{V_o}{R_L} = \frac{5}{2.5 k} = 2 \text{ mA}$$

$$V_{R_o} = 75 \times 2 \text{ m} = 150 \text{ mV}$$

$$A(V_1 - V_2) = 5 + 150 \text{ mV} = 5.15 \text{ V}_\mu$$

$$V_{R_i} = V_1 - V_2 = \frac{5.15}{2 \times 10^5} = 25.75 \mu\text{V}$$

$$i_{R_i} = \frac{V_{R_i}}{R_i} = 25.75 \mu\text{V}$$

$$V_2 = V_1 - V_{R_i} = 1 - 25.75 \mu\text{V} = 0.9997 \text{ V}_\mu$$

Eq2: $R_i = 1 \text{ k}\Omega$ $R_f = 9 \text{ k}\Omega$ $V_{in} = 1 \text{ V}$ $V_o = ?$ if
 a) $A = 10^2$ b) 10^4 c) $A = 10^6$

Ans: $1 + \frac{R_f}{R_i} = 1 + \frac{9}{1} = 10$

$$\beta = \frac{1}{10}$$

$$V_{oA} = \left(\frac{A}{1 + A\beta} \right) \times V_{in} = \frac{100}{1 + 10} = 9.0909 \text{ V}$$

$$V_{oB} = \left(\frac{A}{1 + A\beta} \right) \times V_{in} = \frac{10^5}{1 + 10^3} = 9.9900 \text{ V}$$


$$V_{oC} = \left(\frac{A}{1 + A\beta} \right) \times V_{in} = \frac{10^6}{1 + 10^6} = 9.9999 \text{ V}_\mu$$

→ Better the open loop gain better is the performance.

Q A non inverting amplifier is fed by voltage source of $V_s = 8V$. Divider is implemented by R_a of 100Ω & R_b of $20k\Omega$. The voltage across R_b is fed to amplifier. Amplifier gain of 6 to input him. Let $R_f = 10k\Omega$. Sketch the output circuit & find above for an inverting amplifier.

Amy


a)

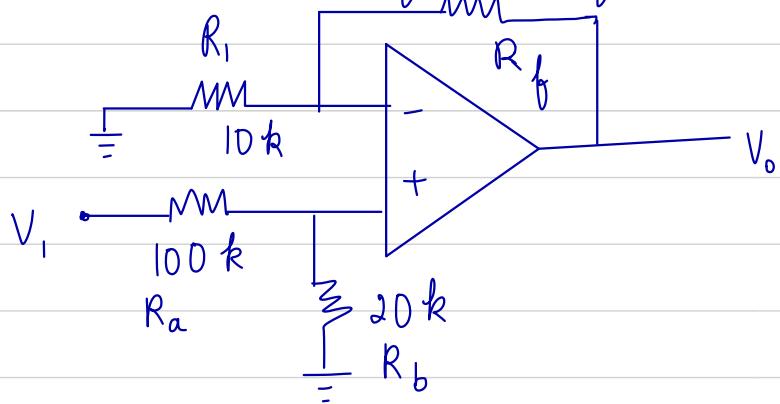

$$R_f = 50k\Omega$$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) \frac{R_b V_i}{R_a + R_b} = 8V_o$$

b)

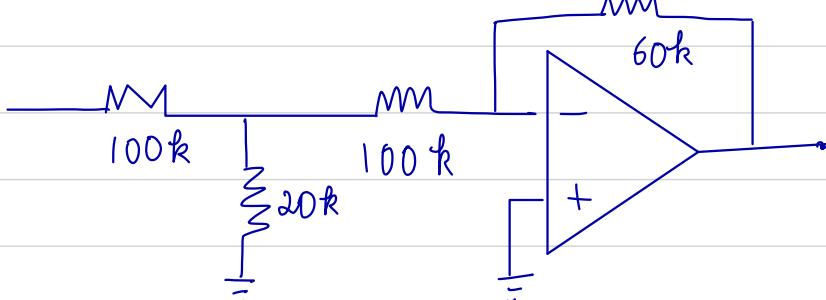

$$V_o = \frac{(20 // 10) V_i}{(20 // 10) + 100} = 0.5 V_i$$

$$V_o = \left(-\frac{60}{10} \right) 0.5 = -3V_f$$

Q) The gain of an opamp has a magnitude of 90 dB at 10 Hz. It exhibits a phase angle of -50° at 300 Hz. Estimate A , f_0 , VGB

A_m

$$A_{oL}(f) = \frac{A_0}{1 + j\frac{f}{f_0}}$$

$$-\tan^{-1} \frac{f}{f_0} = -50^\circ \quad \text{at} \quad f = 300 \text{ Hz}$$


$$\tan 50^\circ = \frac{f}{f_0} \Rightarrow f_0 = \frac{300}{\tan 50^\circ} = 251.72 \text{ Hz}$$

$$f_0 \ggg 10 \text{ Hz}$$

$$90 \text{ dB} = 20 \log A_0$$

$$A_0 = 31.622 \text{ kV/V}$$
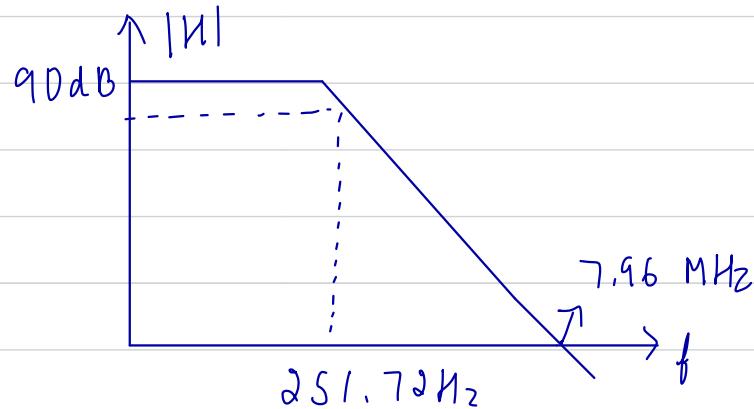
$$VGB = A \times f_0 \\ = 7.96 \text{ MHz}$$



Q) A 741 opamp with $\pm 15 \text{ V}$ power supply is used to build non-inverting amplifier with closed loop gain of 8. Find:

- Max frequency before the output distorts in the AC amplitude is 1 V.
- Max AC input amplitude before the input

distorts if the input frequency is 12 kHz.
 c) Useful frequency range of operation if man AC input amplitude is 20 mV.
 d) Input amplitude range if frequency is 5 kHz.

$$\text{Ans} \quad \text{Slew rate} = 0.5 \text{ V/}\mu\text{s}$$

$$0.5 \text{ V}/\mu\text{s} = \frac{2\pi f V_o}{10^6}$$

$$V_{o,\max} = 8 V_{i,\max} = 8 \text{ V}$$

$$a) f_{\max} = \frac{SR}{2\pi V_{o,\max}} = \frac{0.5 \times 10^6}{2\pi \times 8} = 9.952 \text{ kHz,}$$

$$b) V_{i,\max} = \frac{SR}{2\pi f} = \frac{0.5 \times 10^6}{2\pi \times 12 \times 10^3} = 6.63 \text{ V,}$$

$$V_{i,\max} = \frac{V_{o,\max}}{f} = \frac{6.63}{8} = 0.829 \text{ V,}$$

$$c) V_{i,\max} = 20 \text{ mV}$$

$$V_{o,\max} = 8 \times 20 \text{ mV} = 160 \text{ mV}$$

$$f_{\max} = \frac{SR}{2\pi V_{o,\max}} = \frac{0.5 \times 10^6}{2\pi \times 160 \times 10^{-3}} = 497.3 \text{ kHz,}$$

$$UGB = \frac{10^6}{8} = 125 \text{ kHz,}$$

$$\therefore UGB < f_{\max}$$

$$\therefore \text{Useful frequency range} = 125 \text{ kHz,}$$

$$d) V_{o,\max} = \frac{SR}{2\pi f} = \frac{0.5 \times 10^6}{2\pi \times 5 \text{ kHz}} = 15.923 \text{ V} > 15 \text{ V}_{\text{sat}} = \pm 15 \text{ V}$$

$$V_{i,\max} = \frac{15}{8} = 1.625 \text{ V,} \quad \leftarrow \text{Useful input}$$

output offset voltage (V_{o_0})

Due to :


→ Input offset voltage V_{io}

→ Bias current $\rightarrow I_B \rightarrow \left(\frac{I_{Bp} + I_{Bn}}{2} \right)$

→ Input offset current $\rightarrow I_{io} \rightarrow (|I_{Op} - I_{Bn}|)$

To nullify the o/p voltage we need V_{io} (opposite to o/p) & this is the i/p offset voltage.

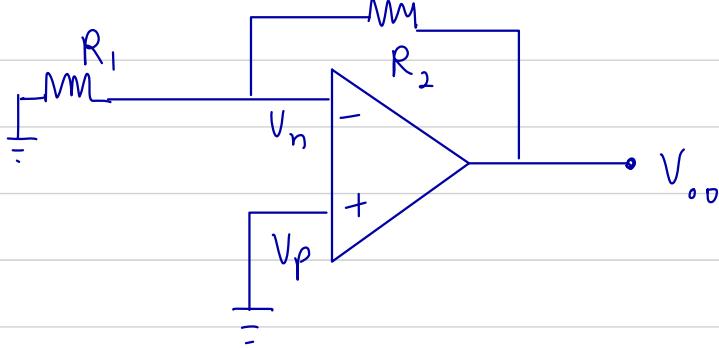• V_{io} need not be only due to I_{bias} but it can be because of V_{cm}



$$V_{io} = |V_p - V_n|$$

$$V_p = 0$$

$$V_n = \frac{R_1}{R_1 + R_2} V_{o_0}$$


$$V_{io} = |0 - V_n| = V_n$$

$$\Rightarrow V_{o_0} = \left(1 + \frac{R_2}{R_1}\right) V_n = \left(1 + \frac{R_2}{R_1}\right) V_{io},$$


• For both configurations (inverting & non inverting) the V_{o_0} & V_{io} relation is same.

$$\begin{aligned}
 V_{o0} &= \left(1 + \frac{R_2}{R_1}\right) V_p \\
 &= \left(1 + \frac{R_2}{R_1}\right) R_p I_{Bp} \\
 &= \left(1 + \frac{R_2}{R_1}\right) \frac{R_2 R_1}{R_1 + R_1} \times I_{BP}
 \end{aligned}$$


$$\Rightarrow V_{o0} = R_2 I_{BP}$$

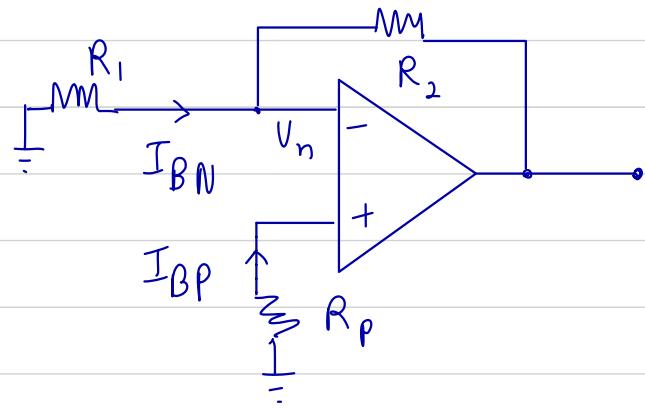

$$V_{o0} = R_2 |I_{Bp} - I_{BN}| = R_2 I_{io}$$

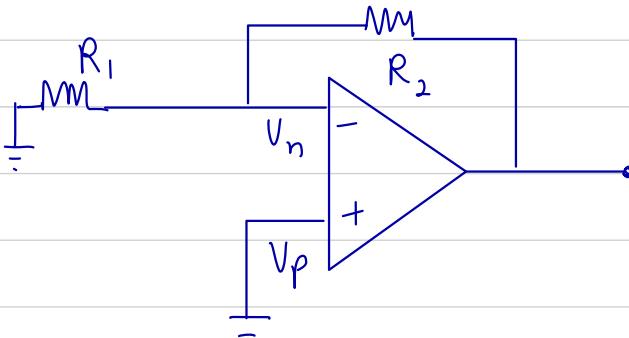
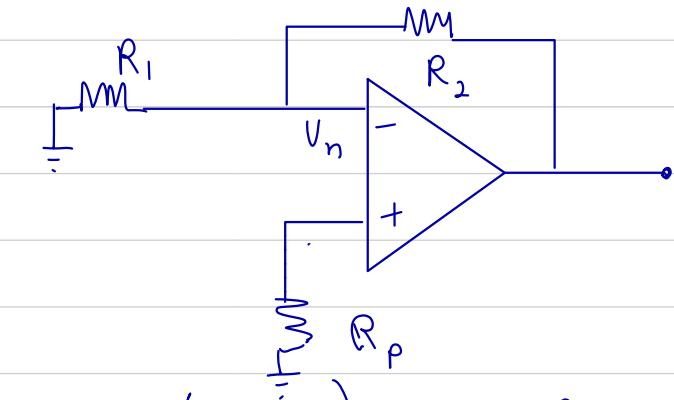
$$V_{o0} = \left(1 + \frac{R_2}{R_1}\right) V_{io} + R_2 I_B$$



$$V_{o0} = \left(1 + \frac{R_2}{R_1}\right) V_{io} + R_2 I_{io}$$

contribution due to i/p offset voltage is much more than $I_B R_2$.

- Q> Compute the max o/p offset voltage in the amplifier
 a> without R_p &
 b> with R_p . The opamp has following specifications:
 $V_{io} = 7.5 \text{ mV max}$

$$I_{i0} = 50 \text{ nA max}$$

at 25°C

let $R_1 = 10 \text{ k}\Omega$ $\therefore R_2 = 1 \text{ k}\Omega$

Am

a) without R_p

$$V_{o0} = \left(1 + \frac{R_2}{R_1}\right) V_{i0} + I_B R_2$$

$$= (1+10) 7.5 + 250 \times 10^{-9} \times 10 \times 10^3$$

$$= 82.5 + 2.5 = 85 \text{ mV}_y$$

b) with R_p :

$$V_{o0} = \left(1 + \frac{R_2}{R_1}\right) V_{i0} + I_{i0} \times R_2$$

$$= 82.5 + 50 \times 10^{-9} \times 10 \times 10^3$$

$$= 82.5 + 0.5 = 83 \text{ mV}_y$$

Power voltage supply rejection ratio (PSRR) or Supply rejection ratio (SVRR)

It is defined by, change in ip offset voltage / change in power supply i.e.

$$SVRR = \frac{dV_{i0}}{dV_{cc}}$$

- It should be as low as possible i.e. as low as $30 \mu\text{V/V}$

$$20 \log \frac{dV_{cc}}{dV_{i0}} = 90 \text{ dB}$$

reciprocal of PSRR.


Q> Consider the circuit given below, showing the input offset voltage due to changes in the power supply. The opamp used is μA741, let R_1 be $100\ \Omega$, R_2 be $100\ k\Omega$. Determine the maximum ripple at the output for a power supply of $0.15\ V_{pp}$ at $120\ Hz$.

$$20 \log \frac{\Delta V_{CC}}{\Delta V_{IO}} = 90 \text{ dB}$$


$$\Delta V_{IO} = \frac{0.15}{31622.77} = 4.74 \mu V$$

$$V_{O0} = \left(1 + \frac{R_2}{R_1}\right) V_{IO} = \left(1 + 10^3\right) 4.74 \mu V = 4.74 mV_{//}$$

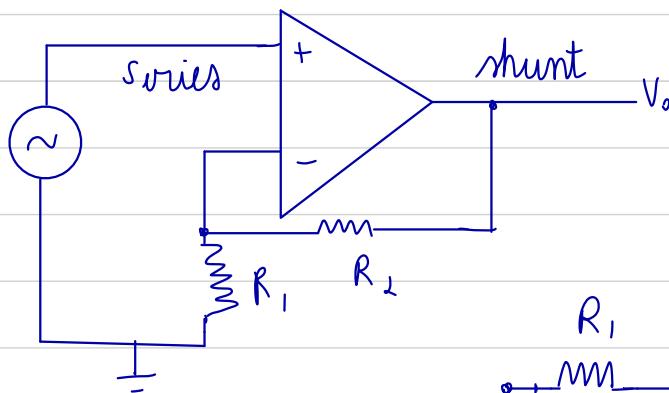Non-idealities in inverting amplifier gain with non-




h - feedback

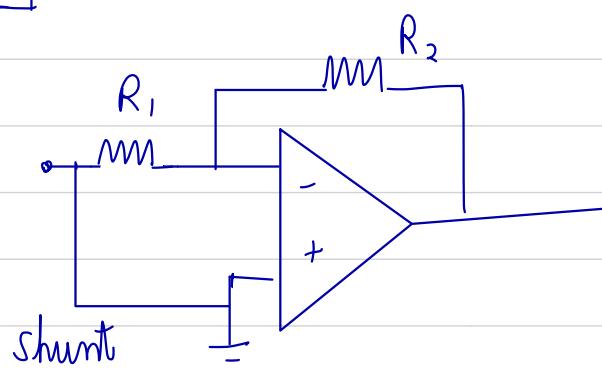

y - feedback

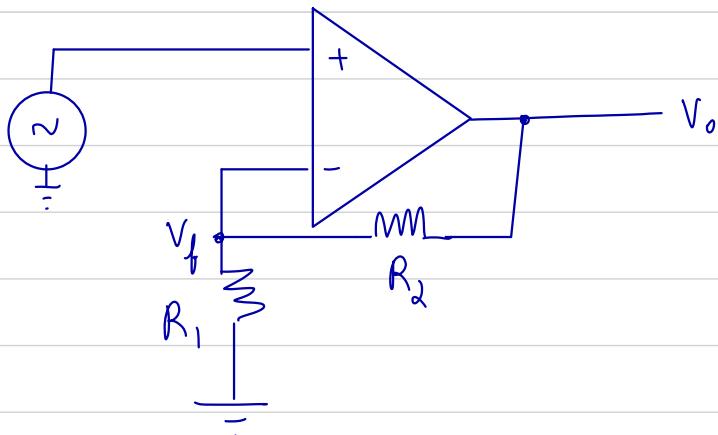Non-inverting amplifier (voltage-series feedback)



$$CL \text{ gain} : A_f = \frac{V_o}{V_{in}}$$

$$OL \text{ gain} : A = \frac{V_o}{V_{id}}$$

$$\text{gain of feedback circuit} : \frac{V_f}{V_o}$$

$$V_o = A V_{id}$$

$$V_o = A \left(V_{in} - \frac{R_1 V_o}{R_1 + R_2} \right)$$

$$\therefore V_o \left(1 + \frac{A R_1}{R_1 + R_2} \right) = A V_{in}$$


$$\therefore A_f = \frac{A}{1 + \frac{A R_1}{R_1 + R_2}}$$

$$A_f = 1 + \frac{R_1}{R_2} \rightarrow \text{ideal}$$

$$\beta = \frac{R_1}{R_1 + R_2} \Rightarrow A_f = \frac{1}{\beta} \rightarrow \text{ideal}$$

$$\begin{aligned}
 A_f &= \frac{A \left(\frac{R_1 R_2}{R_1 + R_2} \right)}{\frac{R_1 + R_2}{R_1 + R_2} + \frac{A R_1}{R_1 + R_2}} = \frac{A}{1 + \frac{A R_1}{R_1 + R_2}} \\
 &= \frac{A}{\frac{A R_1}{R_1 + R_2} \left(1 + \frac{R_1 + R_2}{A R_1} \right)} = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{\left(1 + \frac{1}{A \beta} \right)} \\
 &\approx \left(1 + \frac{R_2}{R_1} \right) \left(1 - \frac{1}{A \beta} \right) \quad \left[\because \frac{1}{A \beta} \ll 1 \right]
 \end{aligned}$$

Input impedance

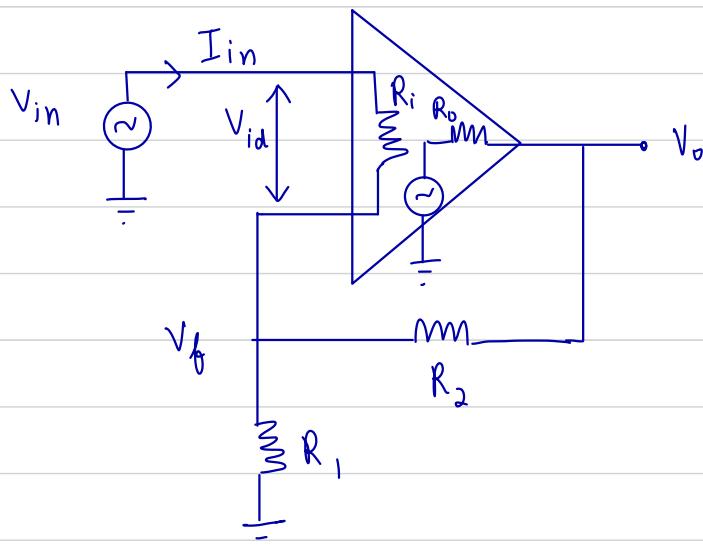

$$\begin{aligned}
 R_{if} &= \frac{V_{in}}{I_{in}} \\
 &= \frac{V_{in}}{V_{id} / R_i} \\
 &= V_{id} / R_i
 \end{aligned}$$


$$V_{id} = \frac{V_o}{A}$$

$$V_o = \frac{A}{1 + A\beta} V_{in}$$

$$R_{if} = \frac{V_{in}}{\frac{V_{in}}{(1 + A\beta) R_i}}$$

$$R_{if} = R_i (1 + A\beta)$$

Output impedance:

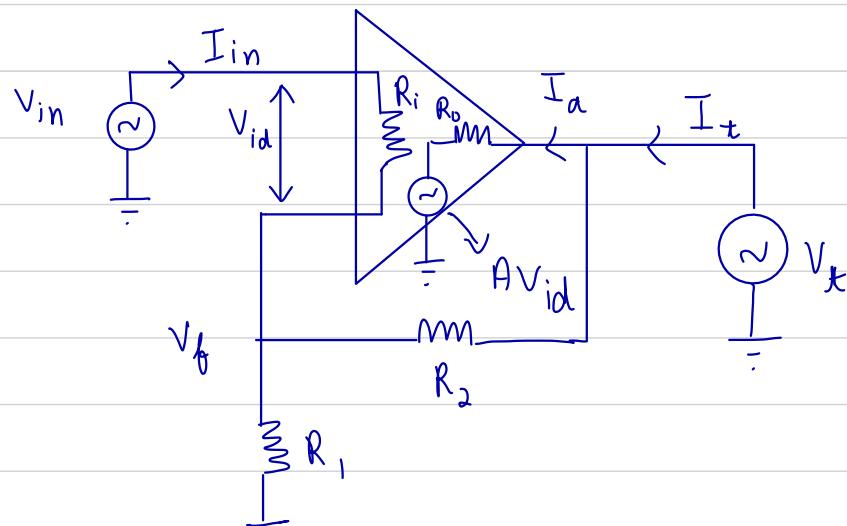

$$R_2 + (R_1 \parallel R_2) \gg R_o$$

$$\therefore I_t = \frac{V_t - A V_{id}}{R_o}$$

$$V_n = \frac{V_t R_1}{R_1 + R_2}$$

$$V_{id} = 0 - V_n$$

$$= -\frac{V_t R_1}{R_1 + R_2}$$

$$I_t \approx I_a$$


$$V_{id} = -\frac{V_t R_1}{R_1 + R_2}$$

$$I_t = \left(V_t + \frac{A V_t R_1}{R_1 + R_2} \right) R_o^{-1}$$

$$\frac{R_o}{1 + A\beta} = \frac{V_t}{I_t}$$

$$\therefore R_{of} = \frac{R_o}{1 + A\beta}$$

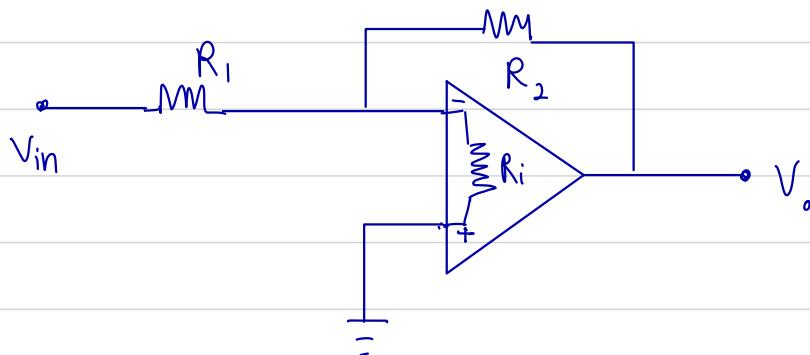Inverting amplifier (voltage - shunt feedback)



$$R_{if} = R_1 + \left(\frac{R_2}{1 + A} \parallel R_i \right) \approx R_1$$

op impedance with feedback:

- Same model & analysis as that of non-inverting case.

C.L gain:

$$V_o = A(0 - V_n) = -AV_n$$

$$V_n = \frac{V_o R_1}{R_1 + R_2} + \frac{V_{in} R_2}{R_1 + R_2} \quad (\text{superposition principle})$$


$$V_o = -\frac{A}{R_1 + R_2} (V_o R_1 + V_{in} R_2)$$

$$\therefore V_o \left(1 + \frac{AR_1}{R_1 + R_2}\right) = -\frac{AV_{in}R_2}{R_1 + R_2}$$

$$\begin{aligned} \therefore \frac{V_o}{V_{in}} &= -\frac{\frac{A}{R_2}}{\frac{R_1 + R_2}{1 + \frac{AR_1}{R_1 + R_2}}} = -\frac{AR_2}{R_1 + R_2} \cdot \frac{1 + \frac{AR_1}{R_1 + R_2}}{AR_1} \\ &= -\frac{R_2}{R_1 \left(1 + \frac{1}{AB}\right)} = -\frac{R_2}{R_1} \left(1 - \frac{1}{AB}\right) \quad \because AB \ll 1 \end{aligned}$$

Now take, $k = \frac{R_2}{R_1 + R_2} \quad k < 1$
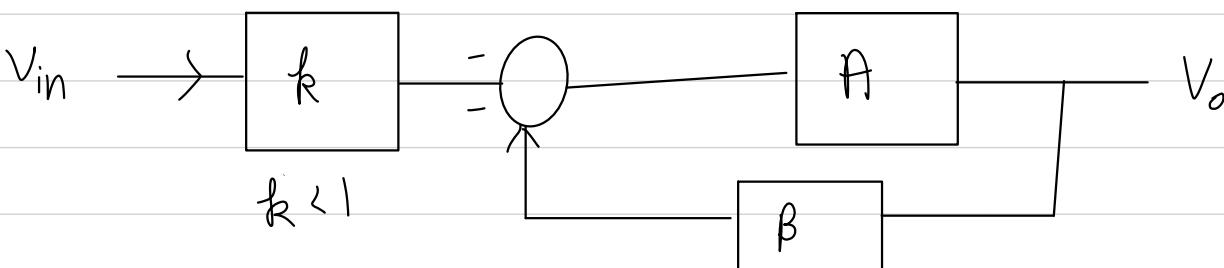
$$A_f = \frac{V_o}{V_{in}} = \frac{-Ak}{1+AB} \approx \frac{k}{B}$$



- Q> Find the minimum value of A for an opamp
- a) The gain of voltage follower built using it does not deviate more than 0.02%.
- b) The gain of the inverting amplifier with $R_1 = R_2$ does not deviate more than 0.02%.
- Ans as gain = $\frac{A}{1+A} = \frac{1}{1+\frac{1}{A}} \approx 1 - \frac{1}{A}$
- $$\frac{1}{A} \leq \frac{0.02}{100} \quad \therefore A \geq \frac{10^4}{2}$$
- $$\therefore A \geq 5000, \quad \therefore A_{\min} = 5000$$
- b) gain = $\frac{-Ak}{1+A\beta}$ $k = 0.5$ $\beta = 0.5$
- $$= \frac{-A/2}{1+A/2} = \frac{-1}{1+\frac{2}{A}} \approx -1 \left(1 - \frac{2}{A}\right)$$
- $$= \frac{2}{A} - 1$$
- $$\therefore \frac{2}{A} \leq \frac{0.02}{100} \quad \therefore A \geq 10^4 \quad \therefore A_{\min} = 10^4$$


Difference amplifier :

$$V_o = (V_2 - V_1) \times \text{non inv gain}$$

$$= (V_2 - V_1) \frac{R_2}{R_1}$$

(This can be done using 2 opamps easily but then it occupies more silicon area. So we need to construct a single opamp for this purpose)


Using 2 opamps:

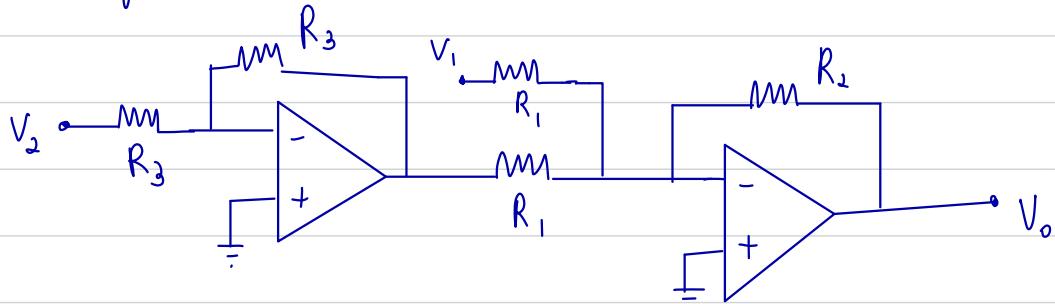

$$\frac{V_1 - V_2}{R_1} = \frac{V_1 - V_0}{R_2}$$

$$\Rightarrow \frac{V_0}{R_2} = \frac{V_2}{R_2} + \frac{V_2}{R_1} - \frac{V_1}{R_1}$$

Using single opamp:

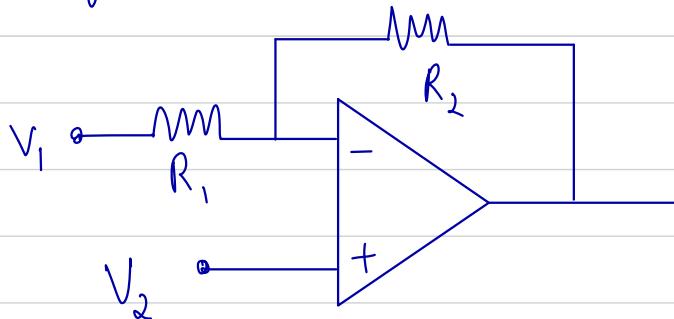

$$\text{Using KCL : } \frac{V_1 - V_2}{R_1} = \frac{V_2 - V_0}{R_2}$$

$$\therefore \frac{V_0}{R_2} = V_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_1}{R_1}$$


$$V_o = V_2 \left(1 + \frac{R_2}{R_1} \right) - V_1 \frac{R_2}{R_1}$$

$$\therefore V_o = \frac{R_2}{R_1} (V_2 - V_1) + V_2$$


Superposition:

$$V_o = \left(1 + \frac{R_2}{R_1} \right) V_2 - \frac{R_2 V_1}{R_1} = \frac{R_2}{R_1} (V_2 - V_1) + V_2$$

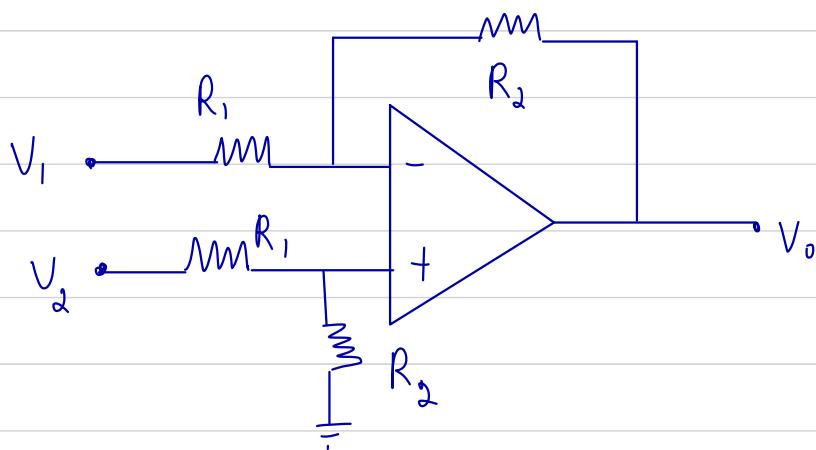if $V_2 = \frac{V_2}{\left(1 + \frac{R_2}{R_1} \right)} \frac{R_2}{R_1}$ then $V_o = \frac{R_2}{R_1} (V_2 - V_1)$



$$V_p = \frac{V_2 R_2}{R_1 + R_2}$$

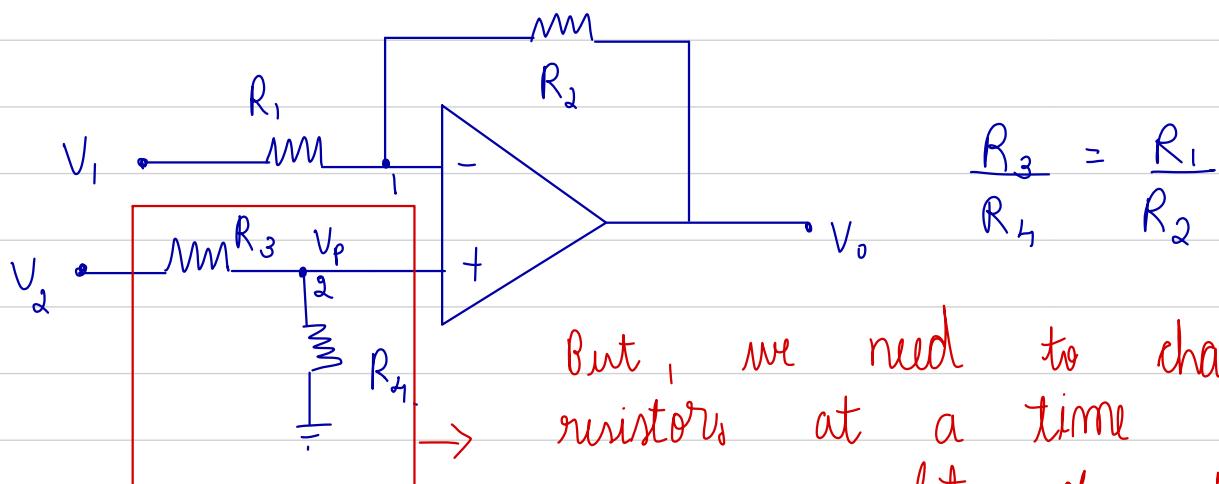

But, we need to change 2 resistors at a time hence, this causes a lot of problem.

Applying KCL:

Node 1:


$$V_p = \frac{R_4}{R_3 + R_4} V_2 = \frac{V_2}{1 + \frac{R_3}{R_4}} = \frac{V_2}{1 + \frac{R_3}{R_4}} = \frac{V_2 (R_2 / R_1)}{1 + \frac{R_2}{R_1}}$$

Node 2:

$$\frac{V_1 - V_p}{R_1} = \frac{V_p - V_o}{R_2}$$

$$\therefore V_o = -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} V_2$$

With common mode signal:

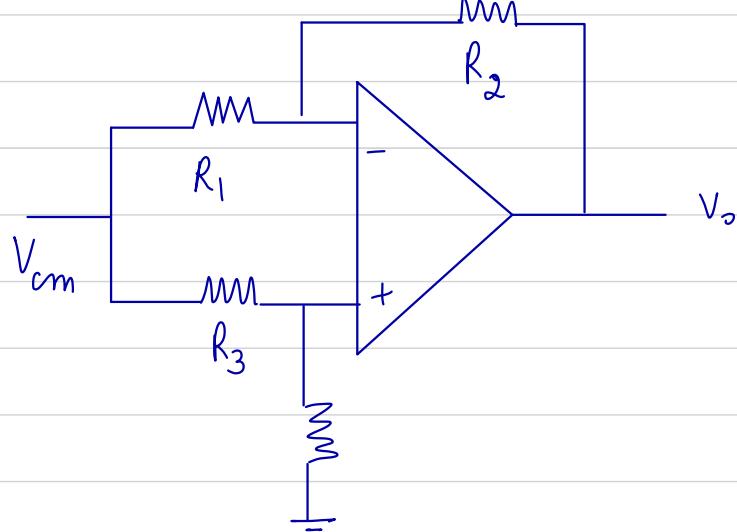

$$\frac{R_3}{R_4} = \frac{R_1}{R_2}$$

$$V_o = (V_2 - V_1) \frac{R_2}{R_1}$$

= 0 (ideally)

$$\frac{V_{cm} - \frac{R_4}{R_3 + R_4} V_{cm}}{\frac{R_1}{R_2}} = \frac{\frac{R_1}{R_2} V_{cm} - V_o}{\frac{R_3 + R_4}{R_2}}$$

$$V_1 = V_{cm} - \frac{V_{dm}}{2}$$

$$V_2 = V_{cm} + \frac{V_{dm}}{2}$$

$$\Rightarrow V_{dm} = V_1 - V_2$$



$$V_{cm} = \frac{V_1 + V_2}{2}$$

$$\frac{V_o}{V_{cm}} = A_{cm} = 0_{II}$$

CMRR = ∞ (ideally)

Experiment 8

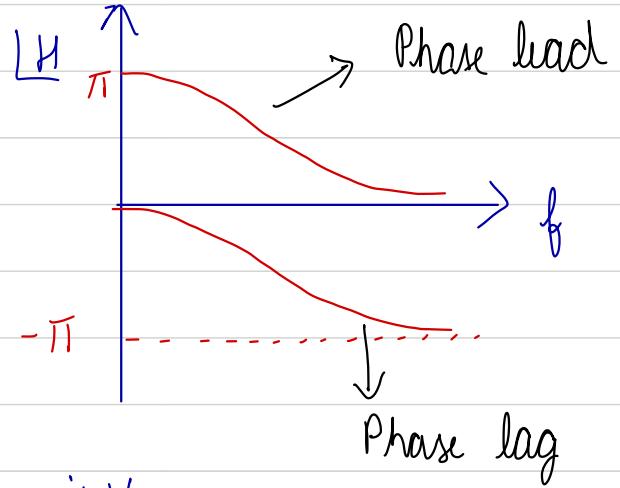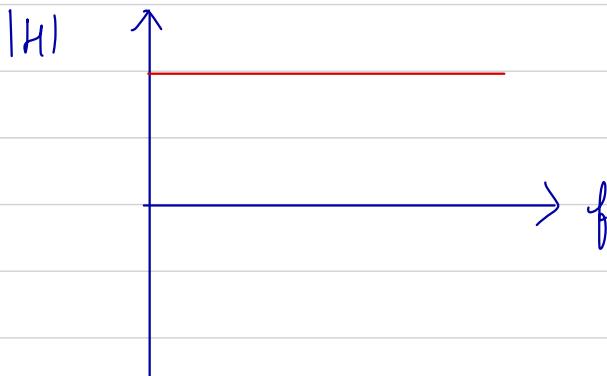All pass filter: (Phase shift) or (Delay equalizer)




$$H(s) = \frac{s - \omega_0}{s + \omega_0}$$

$$H(j\omega) = \frac{j\omega/\omega_0 - 1}{j\omega/\omega_0 + 1}$$

$$\Rightarrow |H| = 1$$



$$\angle H = \tan^{-1} \left(\frac{\omega/\omega_0}{-1} \right) - \tan^{-1} \left(\frac{\omega/\omega_0}{1} \right) = -2 \tan^{-1} \frac{\omega}{\omega_0}$$
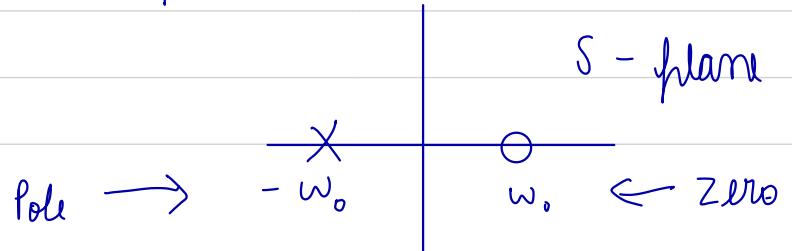
$$= 180 - 2 \tan^{-1} \frac{\omega}{\omega_0}$$



$$H(s) = \frac{s/w_o}{s/w_o + 1} - \frac{1}{s/w_o + 1}$$

HPF LPF

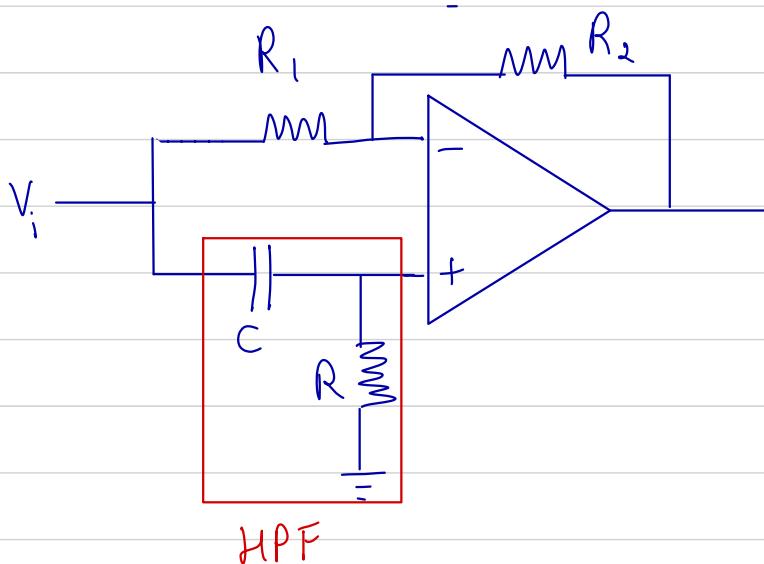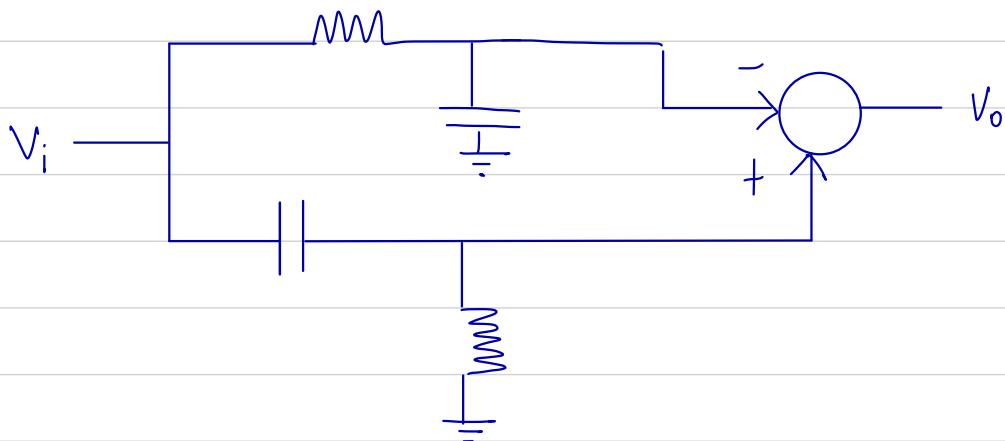

→ All pass filter with phase lead configuration.

$$V_0 = \left(1 + \frac{R_2}{R_1}\right) \frac{s/w_o}{(s/w_o) + 1} V_i$$

$$V_0 = \frac{(s/w_o)V_i}{\left(\frac{s}{w_o} + 1\right)} + \frac{(s/w_o) \frac{R_2}{R_1} V_i}{\frac{s}{w_o} + 1} - \frac{R_2}{R_1} V_i$$

$$= \frac{(s/\omega_0) V_i}{\frac{s}{\omega_0} + 1} + V_i \frac{R_2}{R_1} \left[\frac{\frac{s}{\omega_0}}{\frac{s}{\omega_0} + 1} - 1 \right]$$

Now choose $R_1 = R_2$

$$V_o = \frac{(s/\omega_0) V_i}{\frac{s}{\omega_0} + 1} - \frac{V_i}{\frac{s}{\omega_0} + 1}$$

• For phase lag interchange position of R & C.

$$H(j\omega) = \frac{j\omega - 1}{\frac{\omega_0}{j\omega + 1}} = \frac{j\omega RC - 1}{j\omega RC + 1}$$


$$|H| = \sqrt{1 + (\omega RC)^2} = 1,$$

$$\angle H = 180^\circ - 2\tan^{-1} \omega RC$$

$$\text{At } \omega = 0, \angle H = 180^\circ$$

$$\omega = \infty, \angle H = 0^\circ$$

All pass filter with lagging phase:

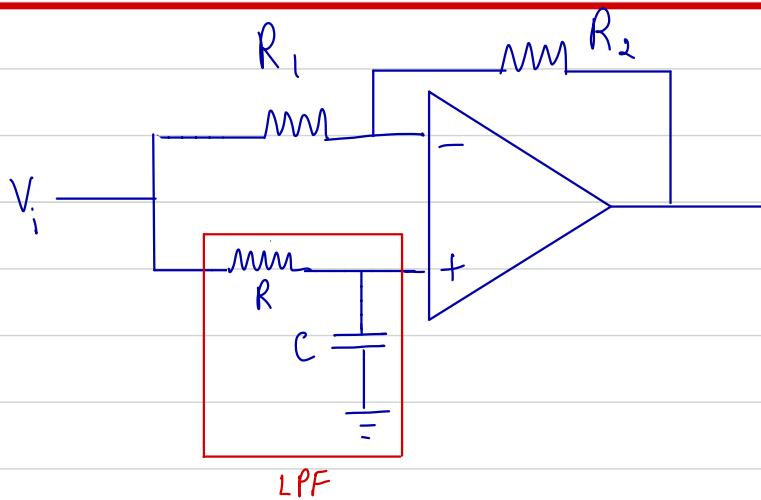

$$V_o = -\frac{R_2}{R_1} V_i + \left(1 + \frac{R_2}{R_1}\right) \frac{V_i}{1 + RCS}$$

Take $R_1 = R_2$

$$\begin{aligned} V_o &= -V_i + \frac{2V_i}{RCS+1} \\ &= \frac{V_i}{1+RCS} + V_i \left(\frac{1}{1+RCS} - 1 \right) \end{aligned}$$

$$H(j\omega) = \frac{1-j\omega RC}{1+j\omega RC}$$

$$|H(j\omega)| = 1 \quad H = -2\tan^{-1} \omega RC,$$


Q) Design a phase shifter that offers phase lag of 45° for an input of 500 Hz . Plot the time domain response of the system and compare with that of a graph of input $-45^\circ = 2\tan^{-1}(2\pi \times 500) RC$.

Ans

$$RC = 1.319 \times 10^{-4}$$



$$\text{let } C = 0.01 \mu\text{F}$$

$$R_1 = R_2 = 10 \text{ k}\Omega$$

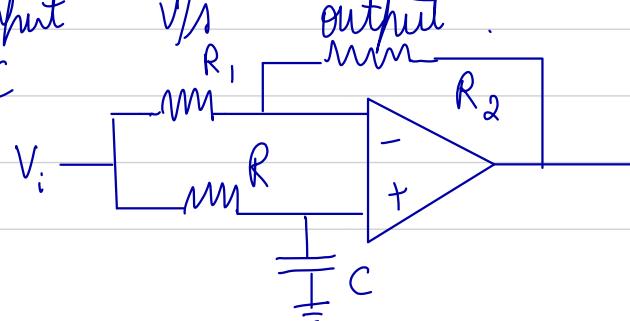

$$R = 13.19 \text{ k}\Omega$$

Input	Output
0.7	0
1	0.7
0.7	1
0	0.7
-0.7	0
-1	-0.7
-0.7	1
0	-0.7

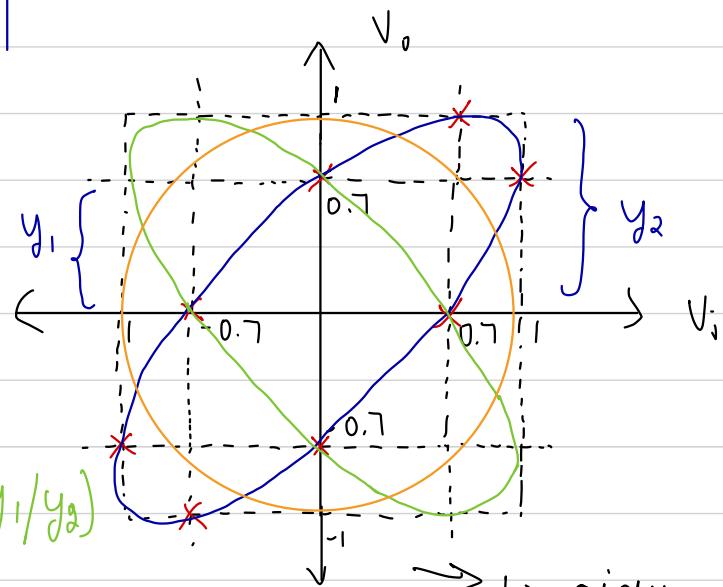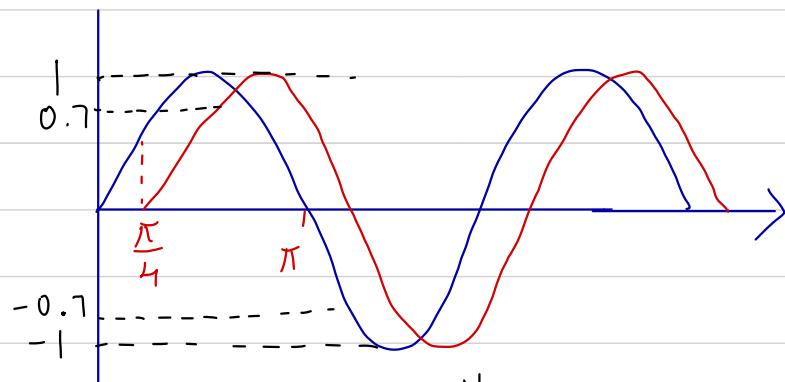

$$\phi < 90^\circ \quad \phi = \sin^{-1}(y_1/y_2)$$

$$\phi > 90^\circ \quad \phi = 180 - \sin^{-1}(y_1/y_2)$$

$$\phi = 90^\circ \quad \phi = \sin^{-1}(1)$$

$$\text{Experiment a)} \quad V_i = 2\sin 4000\pi t$$

$$V_o = 2\sin(4000\pi t - \pi/3)$$

$$-60^\circ = -2\tan^{-1} (2\pi \times 2k\text{Hz}) RC$$


$$\tan 30^\circ = 10000\pi RC$$

$$RC = 4.59 \times 10^{-5}$$

$$\text{let } C = 0.01 \mu\text{F}$$

$$R = 4.59 \text{ k}\Omega$$
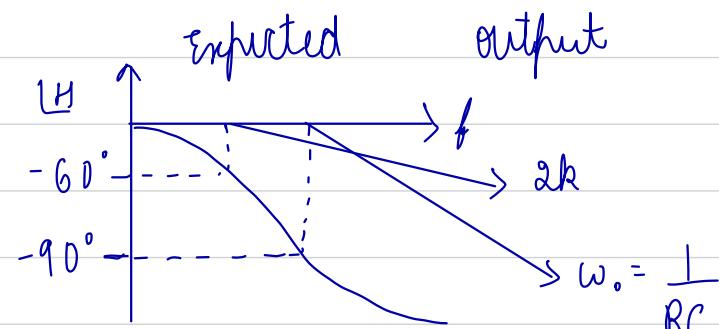
$$\phi = \Delta t \times f \times 360^\circ$$



Interchange $R \& C$ for phase lead

ACTIVE FILTERS

→ Active filters v/s Passive filters

• Active filters have active devices such as opamp, operational etc.

• Passive filters have only passive devices such as R, L, C.

→ Analog filters v/s digital filters

• Analog filters filter analog signals.

• Digital filters also filter analog signal but using digital techniques.

→ Audio frequency v/s radio frequency


• Audio frequencies are smaller \rightarrow RC filter

• Radio frequencies are larger \rightarrow LC filter and crystal oscillators.

Type of filters:

- 1> Low pass filter
- 2> High pass filter
- 3> Band pass filter
- 4> Band reject filter
- 5> All pass filter.

Second order RLC circuit

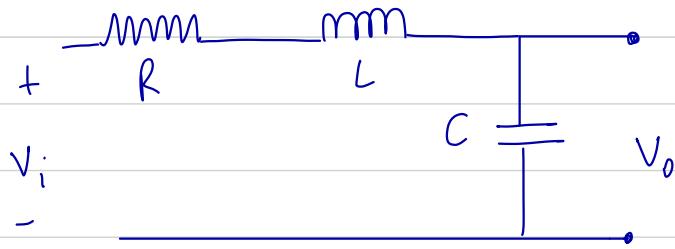

$$\frac{V_o}{V_i} = \frac{\frac{1}{C\omega}}{R + L\omega + \frac{1}{C\omega}} = \frac{1}{RC\omega + LC\omega^2 + 1}$$

$$\frac{V_o}{V_i} = H = \frac{\frac{1}{LC\omega}}{\omega^2 + \frac{R}{L}\omega + \frac{1}{LC\omega}} = \frac{\omega_0^2}{\omega^2 + 2\xi\omega_0\omega + \omega_0^2}$$

$\omega_0 = \frac{1}{\sqrt{LC}}$ = undamped natural frequency

$$\lambda_1, \lambda_2 = -\xi\omega_0 \pm j\omega_0 \sqrt{1 - \xi^2}$$


$$\xi = \frac{R}{2\sqrt{LC}}$$

$\xi = 0 \rightarrow$ undamped

$\xi = 1 \rightarrow$ critically damped

$\xi > 1 \rightarrow$ overdamped

$0 < \xi < 1 \rightarrow$ underdamped

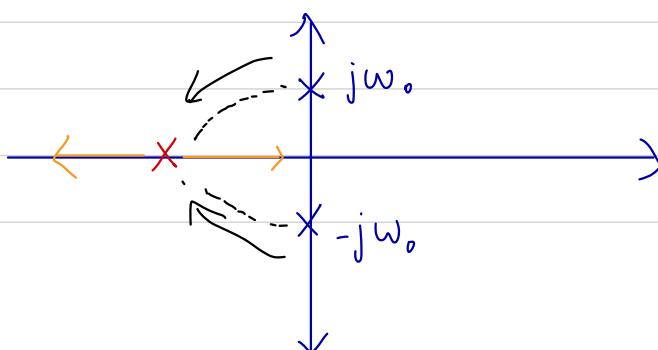


$\times \rightarrow \xi = 0$

$\times \rightarrow \xi = 1$

$\times \rightarrow 0 < \xi < 1$

$\times \rightarrow \xi > 1$

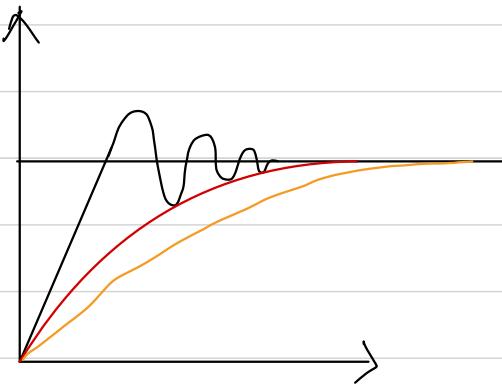

- overdamped
- critically damped
- underdamped

$$Q = \frac{1}{2\xi} = \frac{1}{2} \times \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{\omega_0 L}{R} \quad (\text{newer})$$

$Q \rightarrow$ Quality factor

For parallel circuit, $Q = R \sqrt{\frac{C}{L}}$

Q is the ratio of stored energy to dissipated energy over one radian of oscillation.


$$\frac{V_o}{V_i} = H(s) = \frac{\omega_0^2}{s^2 + \frac{\omega_0 s}{Q} + \omega_0^2} = \frac{1}{\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{\omega_0 Q} + 1}$$

$$H(j\omega) = \frac{1}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j \frac{\omega}{Q\omega_0}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{\left[1 - \left(\frac{\omega}{\omega_0}\right)^2\right]^2 + \left[\frac{\omega}{Q\omega_0}\right]^2}}$$

$$H(j\omega) = -\tan^{-1} \frac{(\omega/\omega_0)}{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)}$$

ω	$ H $	$\angle H$
0	1	0
ω_0	Q	-90°
$\omega \gg \omega_0$	0	$\approx -180^\circ$

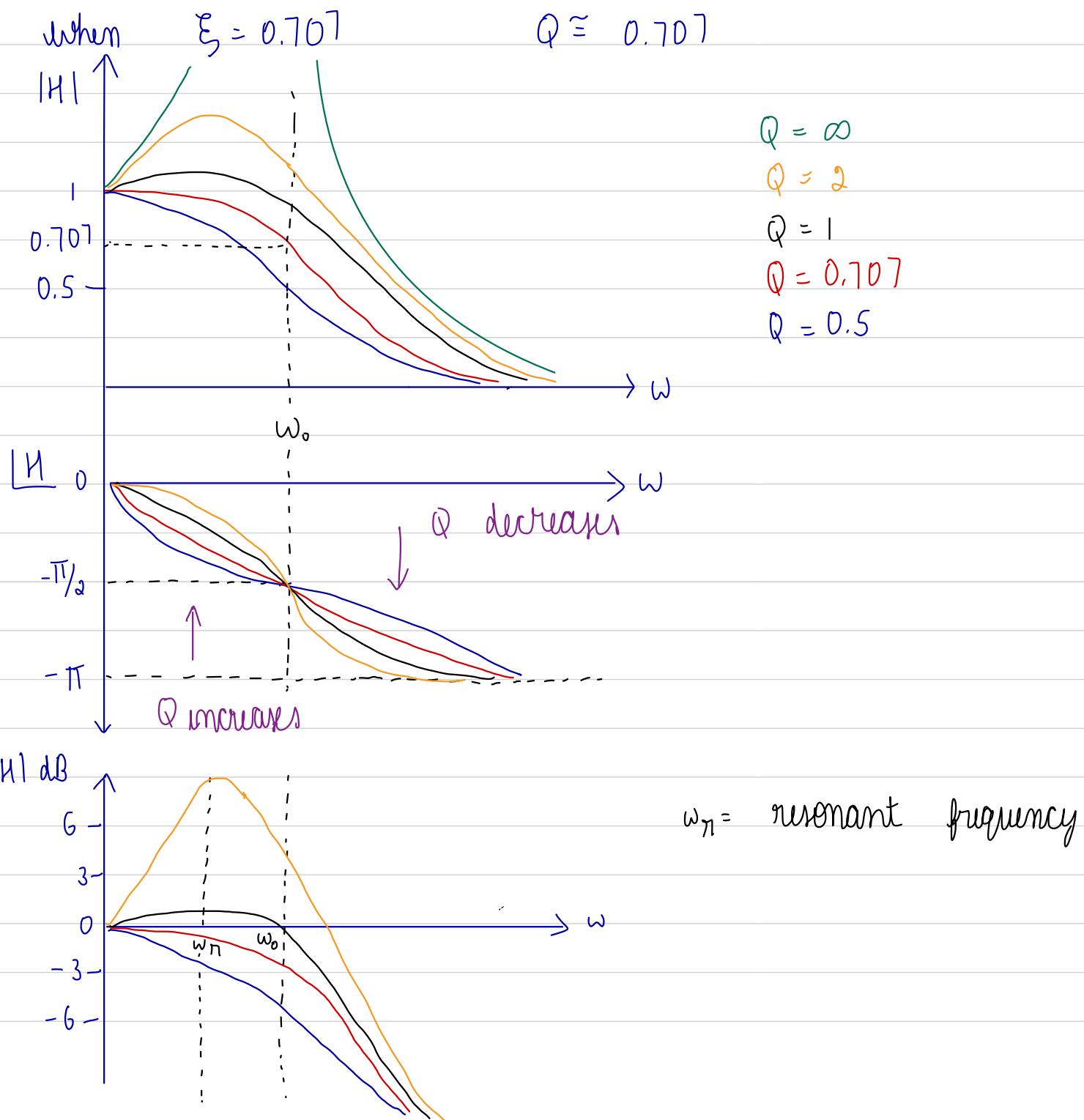

NOTE: Maximally flat response at Butterworth response occurs at $Q = 0.707$

To find $|H(j\omega)|_{\max}$,
Find $\frac{d|H(j\omega)|}{d\omega} = 0 \rightarrow \omega_n$

$$\omega_n = \omega_0 \sqrt{1 - \frac{1}{2Q^2}}$$

$$Q \geq 0.707$$

$$|H(j\omega)|_{\max} = \sqrt{\frac{Q}{1 - \frac{1}{4Q^2}}} \quad Q \geq 0.707$$

Proof:

$$\frac{d|H|}{d\omega} = \frac{1}{\sqrt{(1 - (\frac{\omega}{\omega_0})^2)^2 + (\frac{\omega}{Q\omega_0})^2}} \times \frac{1}{2} \left(2 \left(1 - \left(\frac{\omega}{\omega_0}\right)^2 \right) \left(-\frac{\omega}{\omega_0} + \frac{Q\omega}{Q^2\omega_0} \right) \left(\frac{1}{\omega_0} \right) \right) = 0$$

$$\Rightarrow \frac{\omega}{Q\omega_0} = \left(\frac{\omega}{\omega_0}\right) \cdot 2 \left(1 - \left(\frac{\omega}{\omega_0}\right)^2 \right)$$

$$\Rightarrow \omega = 0 \quad \text{if} \quad 1 - \left(\frac{\omega}{\omega_0}\right)^2 = \frac{1}{2Q^2}$$

$$\Rightarrow \left(\frac{\omega}{\omega_0}\right)^2 = 1 - \frac{1}{2Q^2} \quad \therefore \omega_n = \omega_0 \sqrt{1 - \frac{1}{2Q^2}} //$$

$$\text{At } \omega = \omega_n, |H(j\omega)|_{\max}$$

$$= \frac{1}{\sqrt{\frac{1}{4Q^4} + \left(1 - \frac{1}{2Q^2}\right) \frac{1}{Q^2}}} = \frac{Q}{\sqrt{\frac{1}{4Q^2} + 1 - \frac{1}{2Q^2}}} = \frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}} //$$

A good filter will have steeper curve in transition region. So higher value of Q is desired.


A higher order active filter can be created using :

- 1> Direct synthesis
- 2> Cascading of lower order filters

Ex:


$$H_1(s) = \frac{1}{\left(\frac{1}{\omega_0}\right)^2 + \frac{1}{Q\omega_0} + 1}$$
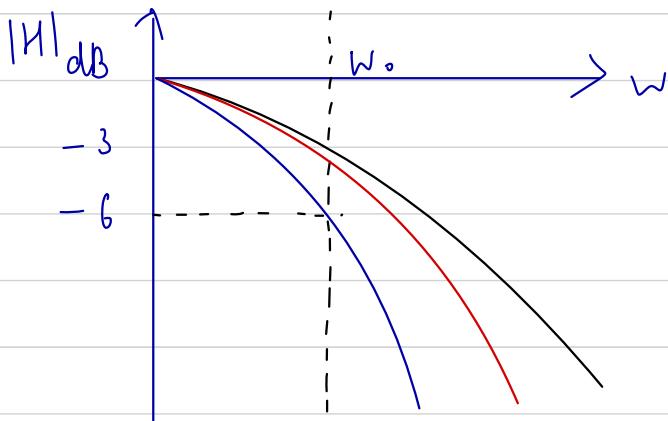
$$H_2(s) = \frac{1}{1 + \frac{s}{\omega_0}}$$



$$\begin{aligned} H_2(s) &= -20 \text{ dB/dec} \\ H_1(s) &= -40 \text{ dB/dec} \\ H_1(s) \cdot H_2(s) &= -60 \text{ dB/dec} \end{aligned}$$


with $Q = 0.707$

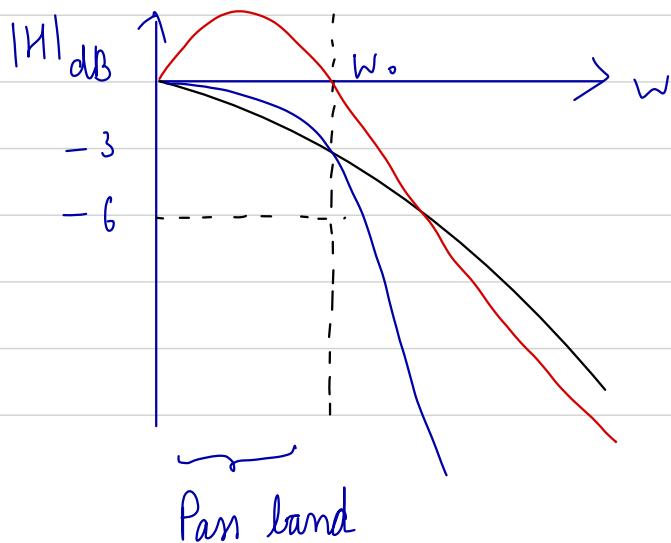

$$\begin{aligned} H_2(s) &= -20 \text{ dB/dec} \\ H_1(s) &= -40 \text{ dB/dec} \\ H_1(s) \cdot H_2(s) &= -60 \text{ dB/dec} \end{aligned}$$

with $Q = 1$

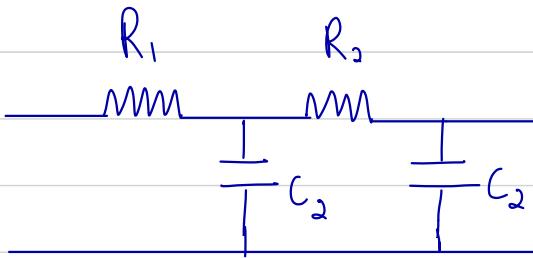experiment q - Sallim - key filter (KRC filter)



$$\begin{bmatrix} 1 & R_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ C_1 s & 1 \end{bmatrix} \begin{bmatrix} 1 & R_2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ C_2 s & 1 \end{bmatrix}$$

$$H(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_2 C_2 + R_1 C_2)s + 1}$$

$$= \frac{1}{s^2 + \frac{R_1 R_2 C_1 C_2}{R_1 C_1 + R_2 C_2 + R_1 C_2} s + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$= \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2} = \frac{1}{\left(\frac{s}{\omega_0}\right)^2 + \frac{2\zeta}{Q\omega_0} s + 1}$$

where $\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 C_1 + R_2 C_2 + R_1 C_2}$$

let $R_1 = R$ $R_2 = mR$

$$C_1 = C \quad C_2 = nC$$

then $Q = \frac{RC\sqrt{mn}}{RC(1+mn+n)}$

$$= \frac{\sqrt{mn}}{1+mn+n}$$

let $m = 1$

$$Q = \frac{\sqrt{n}}{1+2n}$$


$$\frac{dQ}{dn} = \frac{\left(\frac{1}{2}\sqrt{n}\right)(1+2n) - 2\sqrt{n}}{(1+2n)^2} = 0$$

$$\Rightarrow 1+2n = \frac{(2\sqrt{n})^2}{(2\sqrt{n})^2}$$


$$1+2n = 4n$$

$$\therefore n = 0.5 //$$

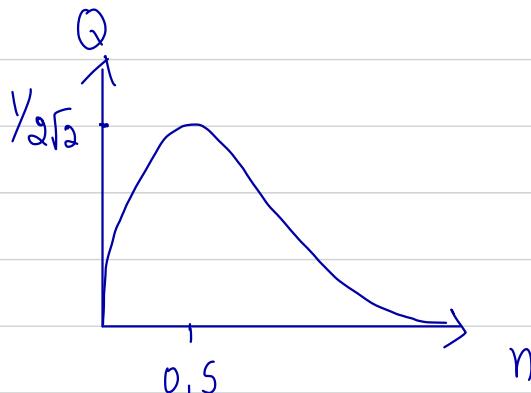
$$\therefore \text{when } n = 0.5, Q_{\max} = \frac{1}{2\sqrt{2}} = 0.3535$$



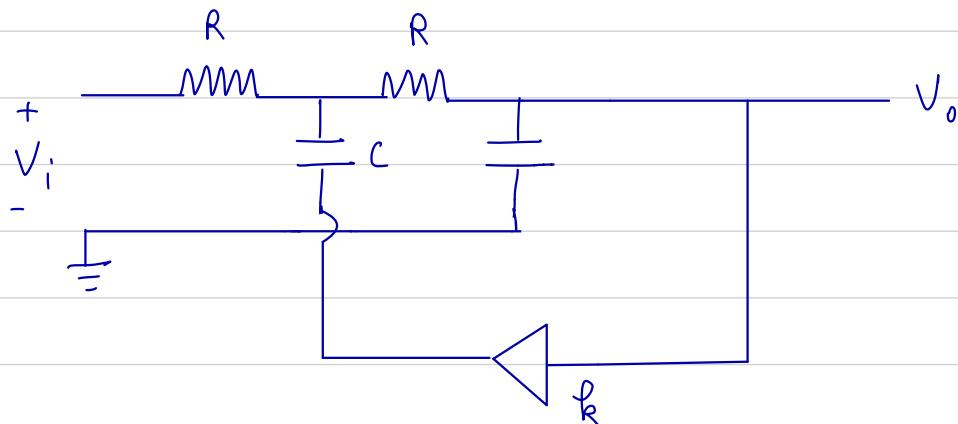
Also considering all combinations of m, n the max value of Q is obtained at $m=1$ and $n=0.5$.




$$V_o = V_{o1} + V_{o2}$$

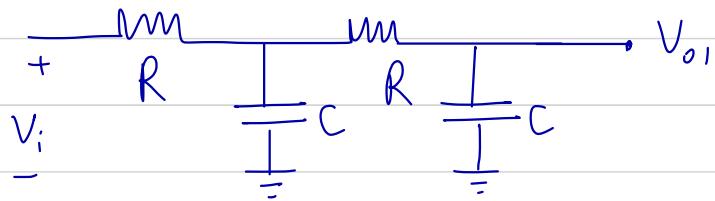
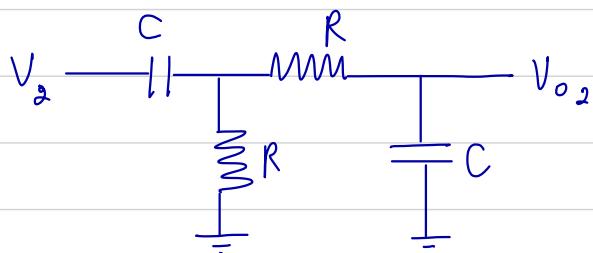
$$\frac{V_{o1}}{V_i} = \frac{1}{(RC_1)^2 + 3RC_1 + 1}$$


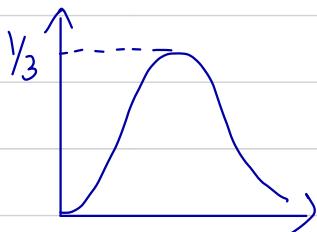
$$\frac{V_{o2}}{V_2} = \frac{RC_1}{(RC_1)^2 + 3RC_1 + 1}$$



$$\frac{V_o}{V_i} = \frac{V_i + RC_1 \cdot k V_o}{(RC_1)^2 + 3RC_1 + 1}$$

$$\frac{V_o}{V_i} = \frac{1}{(RC_1)^2 + 3RC_1 + 1} + \frac{k RC_1}{(RC_1)^2 + 3RC_1 + 1} \left(\frac{V_o}{V_i} \right)$$


$$\frac{V_o}{V_i} = \frac{1}{\frac{(RC_1)^2 + 3RC_1 + 1}{(RC_1)^2 + (3-k)RC_1 + 1}}$$

$$= \frac{1}{(RC_1)^2 + (3-k)RC_1 + 1}$$


$$= \frac{\omega^2}{\omega^2 + \frac{(3-k)\omega}{\omega} + \omega^2}$$

where $\omega = \frac{1}{RC}$

$$\Omega = \frac{1}{3-k}$$

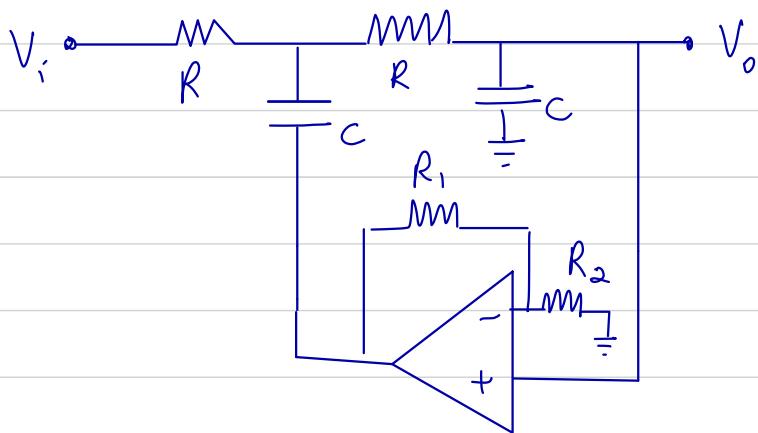


Sallen key filter:

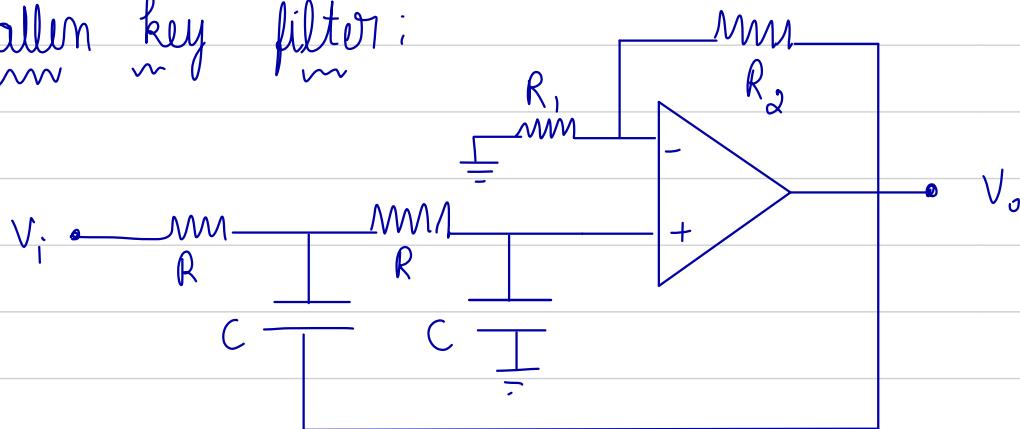

$$\frac{V_o}{V_i} = \frac{k}{(RC_1)^2 + (3-k)RC_1 + 1}$$

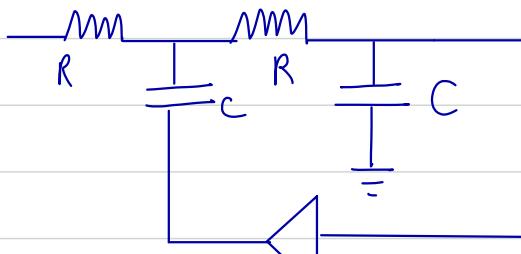Negative feedback is dominant here. Because -ve feedback is instantaneous. In case of positive feedback there is delay due to capacitor connected.




$$|A\beta| = 1 \text{ at phase } 0^\circ$$

$$H = \frac{KRC_1}{(RC_1)^2 + 3RC_1 + 1} \quad \text{when } K = 3, \text{ gain} = 1$$

$$1 + \frac{R_L}{R_2} \leq 3$$

$$k = 3$$

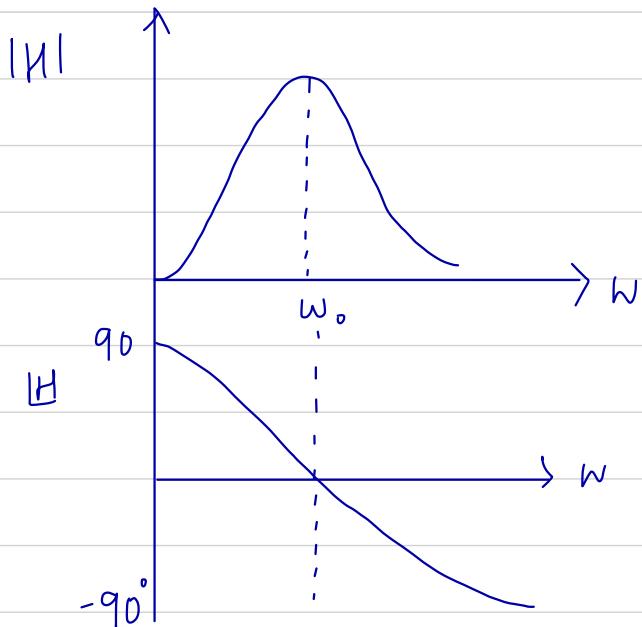


$$H(j\omega) = \frac{k}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{\omega}{Q\omega_0}}$$


$$|H| = \frac{k}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2}}$$

$$\angle H = -\tan^{-1} \frac{\omega/Q\omega_0}{1 - \left(\frac{\omega}{\omega_0}\right)^2}$$

ω	$ H $	$\angle H$
0	k	0°
ω_0	kQ	$-\pi/2$
$\omega > \omega_0$	0	$-\pi$

Q	K	$ H $ at $\omega=0$	$ H $ at $\omega=\omega_0$
0.5	1	1	0.5
0.707	1.586	1.586	1.213
1	2	2	2
2	2.5	2.5	5

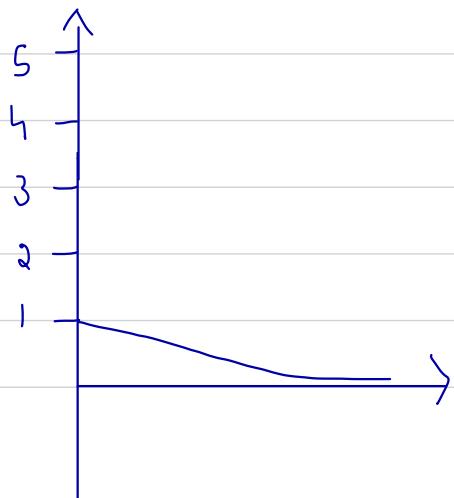


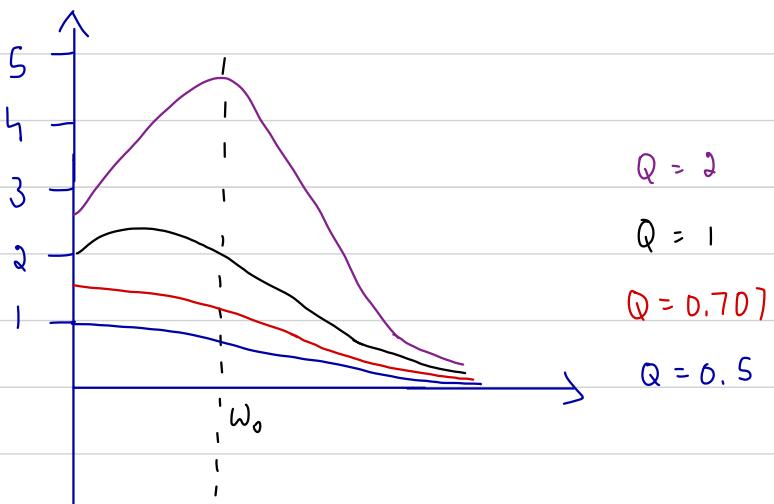

$$\omega_n = \omega_0 \sqrt{1 - \frac{1}{4Q^2}}$$

At ω_n , $|H|_{\max} = \frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}}$

Sallen key filter: 2nd order LPF & HPF

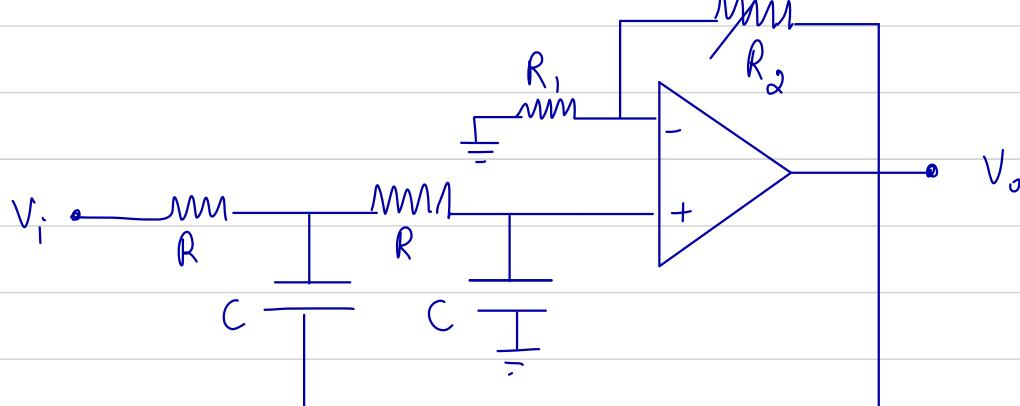

$$R_1 = 1 \text{ k}\Omega$$

$$H(s) = \frac{k}{(RC_s)^2 + (3-k)RC_s + 1}$$

where $k = 1 + \frac{R_2}{R_1}$, $Q = \frac{1}{3-k}$

$V_{i,pp} = 10 \text{ V}$, $R_2 \rightarrow$ Potentiometer is used

Q	$R_2 (\Omega)$	k	$f_o (\text{Hz})$	$ H _p$	$f_p (\text{Hz})$	Stop band roll off (-40 dB/dec)
0.707	586	1.586	1k			
0.5	0	1	1k			
2	1.5 k	2.5	1k			

↓

decrease the i/p to $\downarrow V_{pp}$ for some values beyond ω_o .

$$-40 = 20 \log \left(\frac{V_o}{V_i} \right)$$

$$V_i = 100 \times V_o = 100 \times 100 \times 10^{-3} = 10 \text{ V}_{pp}$$

Phase for $Q = 0.707$



- ctrl + right click on R_2
- change value as {x}
- click on spice directive (.op)
- step param x list | 586 500

- Interchange R & C to get HPF
- Magnitude & phase response for $Q = 0.707, 5, 2$ for LPF
- Magnitude & phase for HPF with $Q = 0.707$
- $\omega_o = \frac{1}{RC}$, when $C = 0.01 \mu\text{F}$
 $R = 15.9 \text{ k}\Omega$

$$|V_p|_{\max} = \frac{Qk}{\sqrt{1 - \frac{1}{4Q^2}}}$$

$$\omega_p = \omega_0 \sqrt{1 - \frac{1}{2Q^2}}$$

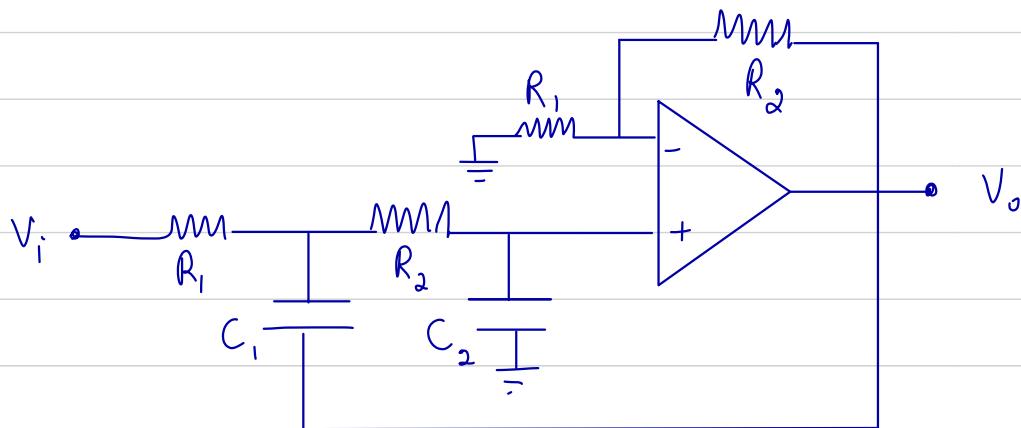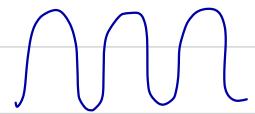ground or disconnect the signal generator, then ground it. This gives sustained oscillations at the output (keep $k > 3$).




$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_p$$


$$V_o = k V_p$$

$$V_p = \frac{V_i}{C_2 s} \left(\frac{1}{R_2 + \frac{1}{C_2 s}} \right) = \frac{V_i}{1 + R_2 C_2 s}$$

$$V_i = (1 + R_2 C_2 s) V_p$$

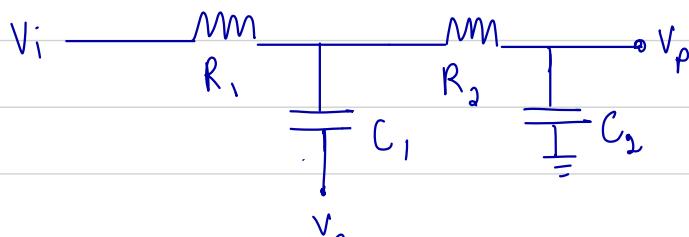
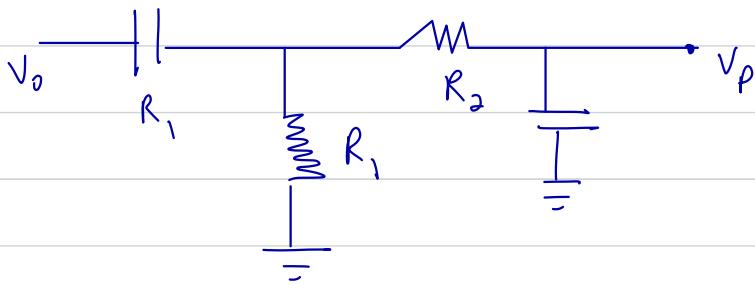
$$V_p = \frac{V_i}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_2 C_2 + R_1 C_2) s + 1}$$



At V_1 ,


$$\frac{V_i - V_1}{R_1} = \frac{V_1 - V_p}{R_2} + \frac{V_1 - V_o}{1/C_1\pi}$$

$$\frac{V_i}{R_1} - \frac{V_1}{R_1} = V_1 \left(\frac{1}{R_2} + C_1\pi \right) - V_o \left[\frac{1}{kR_2} + C_1\pi \right]$$

$$V_1 = \frac{V_o}{k} \left(1 + R_2 C_1 \pi \right) \frac{V_i}{R_1} = V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + C_1 \pi \right) - V_o \left[\frac{1}{kR_2} + C_1 \pi \right]$$

2nd order HPF wries RLC circuit

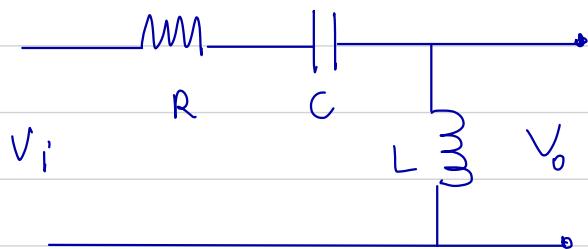Characteristic equation must remain same.
(LPF; 2 poles \rightarrow all pole filter)



$$\frac{V_o}{V_i} = \frac{L\pi}{L\pi + R + 1/C\pi} = \frac{LC\pi^2}{LC\pi^2 + RC\pi + 1}$$

$$\Rightarrow H(\pi) = \frac{(s/\omega_0)^2}{\left(\frac{1}{\omega_0}\right)^2 + \frac{1}{\omega_0} + 1} = \frac{\pi^2}{\pi^2 + 2\xi\omega_0\pi + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q\omega_0 = \frac{1}{RC}$$

$$Q = \frac{1}{\sqrt{RC}} \times \frac{\sqrt{LC}}{RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$H(j\omega) = \frac{-\left(\omega/\omega_0\right)^2}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{\omega}{\omega_0}}$$

$$|H(j\omega)| = \frac{\left(\omega/\omega_0\right)}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2}}$$

$$\angle H(j\omega) = 180^\circ - \tan^{-1} \frac{\left(\omega/Q\omega_0\right)}{1 - \left(\frac{\omega}{\omega_0}\right)^2}$$


ω	$ H $	$\angle H$
0	0	π
ω_0	Q	$\pi/2$
$\omega \gg \omega_0$	1	0

$$Q = 0.5$$

$$Q = 0.707$$

$$Q = 1$$

$$Q = 2$$

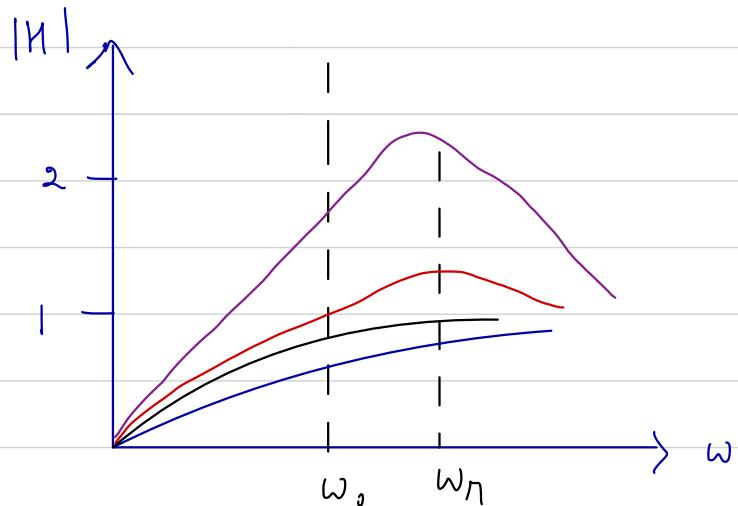


ω_r - resonance frequency
at $Q = 1$

$$\omega_r = \frac{\omega_0}{\sqrt{1 - \frac{1}{2Q^2}}}$$

$$|H|_{max} = \frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}}$$

2nd order Band pass filter - (Prototype)

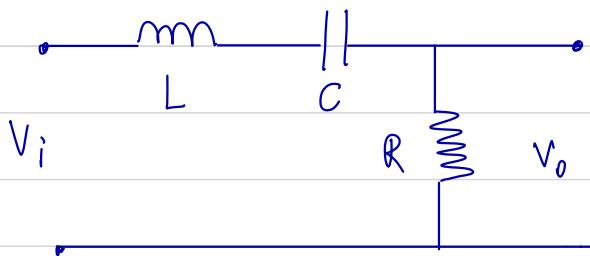

$$\frac{V_o}{V_i} = H(s) = \frac{R}{Ls + \frac{1}{Cs} + R} = \frac{RCs}{LCs^2 + RCs + 1} = \frac{(R/L)s}{s^2 + (R/L)s + \frac{1}{LC}}$$

$$H(s) = \frac{\frac{1}{Q\omega_0}}{\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{Q\omega_0} + 1}$$

where $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$H(j\omega) = \frac{\frac{j\omega}{Q\omega_0}}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + \frac{j\omega}{Q\omega_0}}$$

$$|H(j\omega)| = \frac{\omega}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2}}$$


$$H(j\omega) = \tan^{-1} \left(\frac{\omega/Q\omega_0}{\omega_0} \right) - \tan^{-1} \left(\frac{\omega/Q\omega_0}{1 - (\omega/\omega_0)^2} \right)$$

$$= 90^\circ - \tan^{-1} \left(\frac{\omega/Q\omega_0}{1 - (\omega/\omega_0)^2} \right)$$

ω	$ H $	$\angle H$
0	0	90°
ω_0	1	0°
$\omega \gg \omega_0$	0	-90°

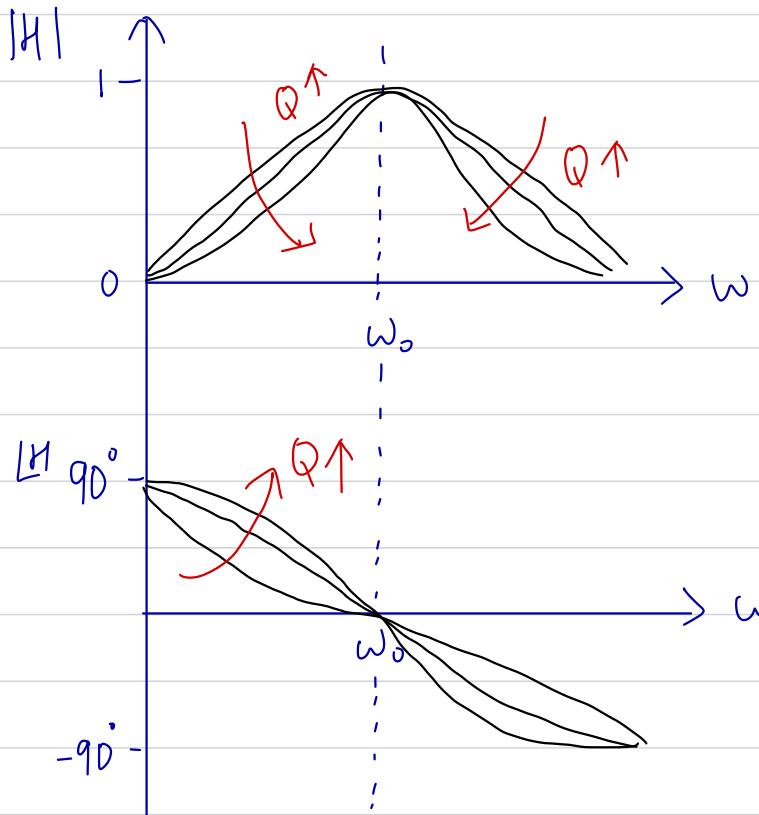

$$\frac{d|H|}{d\omega} = 0 \text{ at } \omega_r = \omega_0 \text{ with } |H|_{\max} = 1$$

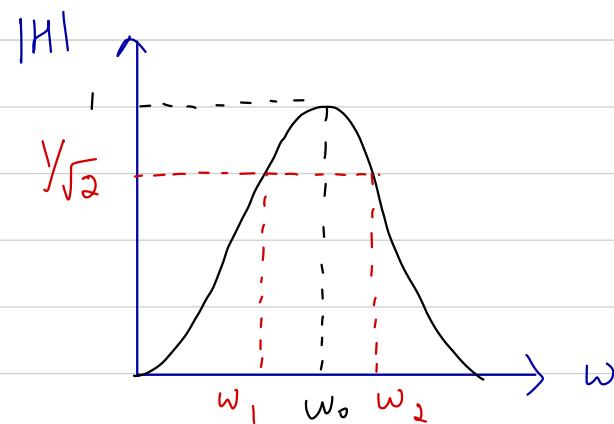

$$\text{Bandwidth} = \omega_2 - \omega_1 \quad \text{also} \quad \omega_2 - \omega_1 = \frac{\omega_0}{Q}$$

So as Q increases bandwidth decreases.

Proof: At $\omega_1 \in \omega_2$ $|H| = \sqrt{2}$

$$|H|^2 = \frac{1}{2}$$

$$|H|^2 = \frac{\left(\omega/Q\omega_0\right)^2}{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2} = \frac{1}{2}$$

$$\Rightarrow 2 \left(\frac{\omega}{Q\omega_0}\right)^2 = \left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2$$

$$\Rightarrow \left(\frac{\omega}{Q\omega_0}\right)^2 = \left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2$$

$$\text{Let } \frac{\omega}{\omega_0} = \alpha$$

$$\frac{\alpha^2}{Q^2} = 1 - 2\alpha^2 + \alpha^4$$

$$\Rightarrow \alpha^4 - \alpha^2 \left(2 + \frac{1}{Q^2}\right) + 1 = 0$$

$$\alpha^2 = \left(2 + \frac{1}{Q^2}\right) \pm \sqrt{\left(2 + \frac{1}{Q^2}\right)^2 - 4}$$

$$\alpha^2 = 2 + \frac{1}{Q^2} \pm \sqrt{\frac{1}{Q^4} + 4 + \frac{4}{Q^2} - 4}$$

$$\alpha^2 = \frac{1}{2} \left(2 + \frac{1}{Q^2}\right) \pm \frac{1}{Q} \sqrt{\frac{1}{Q^2} + 4}$$

$$\omega^2 = \omega_0^2 \alpha^2$$

$$= \frac{\omega_0^2}{2} \left(\left(\frac{1}{Q^2} + 2\right) \pm \frac{1}{Q} \sqrt{4 + \frac{1}{Q^2}} \right)$$

$$\text{let } \left(\frac{1}{Q^2} + 2 \right) = a$$

$$\text{Eq } \left(\frac{1}{Q} \sqrt{4 + \frac{1}{Q^2}} \right) = b$$

$$\omega_2^2 = \frac{\omega_0^2}{2} (a+b)$$

$$\omega_1^2 = \frac{\omega_0^2}{2} (a-b)$$


$$\omega_2^2 \omega_1^2 = \frac{\omega_0^4}{4} (a^2 - b^2) = \frac{\omega_0^4}{4} \left(4 + \frac{1}{Q^2} + \frac{1}{Q^2} - \frac{1}{Q^4} - \frac{1}{Q^2} \right) = \omega_0^4$$

$$\therefore \boxed{\omega_0 = \sqrt{\omega_1 \omega_2}}$$

$$\begin{aligned} (\omega_2 - \omega_1)^2 &= \frac{\omega_0^2}{2} \left(\sqrt{a+b} - \sqrt{a-b} \right)^2 \\ &= \frac{\omega_0^2}{2} \left(a+b + a-b - 2\sqrt{a^2 - b^2} \right) \\ &= \omega_0^2 \left(a - \sqrt{a^2 - b^2} \right) \\ &= \omega_0^2 \left(2 + \frac{1}{Q^2} - \sqrt{4} \right) = \frac{\omega_0^2}{Q^2} \end{aligned}$$

$$\therefore \boxed{\omega_2 - \omega_1 = \frac{\omega_0}{Q}}$$

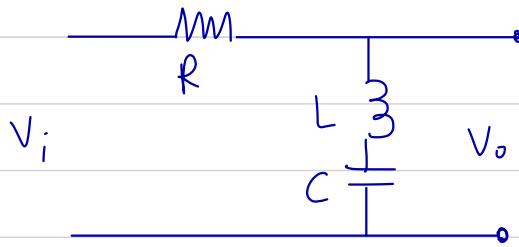Second order band reject filter - (Prototype)




$$\frac{V_o}{V_i} = H(s) = \frac{1 + L C s^2}{1 + R C s + L C s^2} = \frac{\left(\frac{s}{\omega_0}\right)^2 + 1}{\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{Q\omega_0} + 1}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$H(j\omega) = \frac{1 - \frac{\omega^2}{\omega_0^2}}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{\omega}{Q\omega_0}}$$

$$|H(j\omega)| = \frac{1 - \left(\frac{\omega}{\omega_0}\right)^2}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2}}$$



$$\angle H(j\omega) = -\tan^{-1} \left(\frac{\omega/Q\omega_0}{1 - (\omega/\omega_0)^2} \right)$$

ω	$ H $	$\angle H$
0	1	0°
ω_0	0	-90° (at $\omega = \omega_0^-$)
$\omega \gg \omega_0$	1	90° (at $\omega = \omega_0^+$)

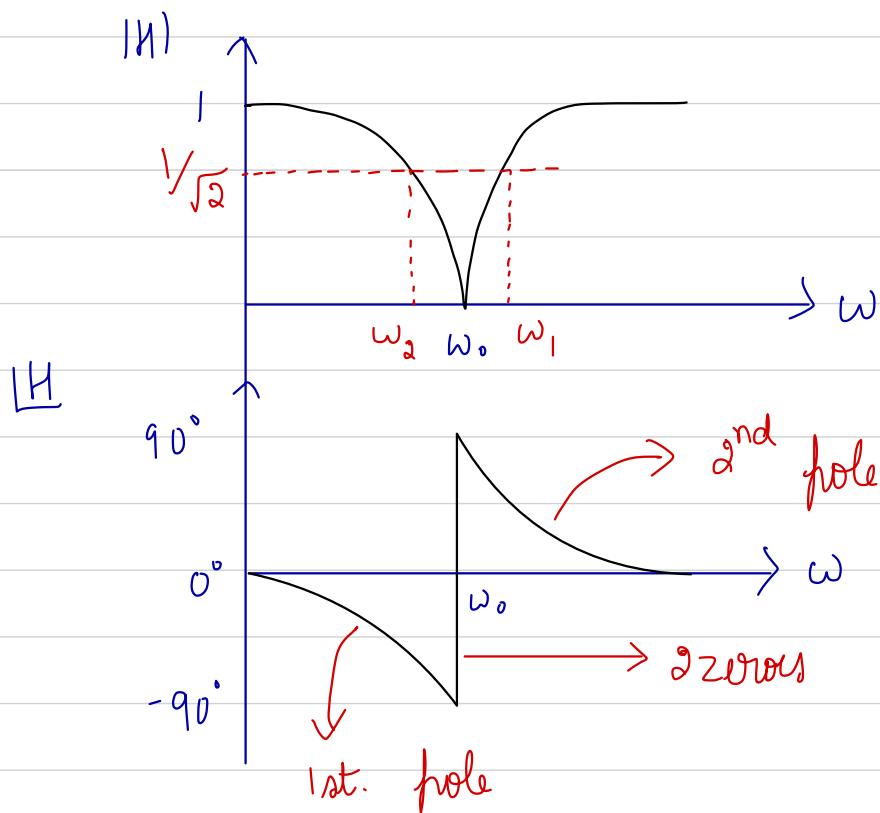

$$\omega_1 - \omega_2 = \frac{\omega_0}{Q}$$

Second order Sallen - key HPF

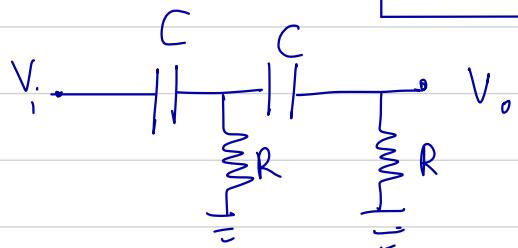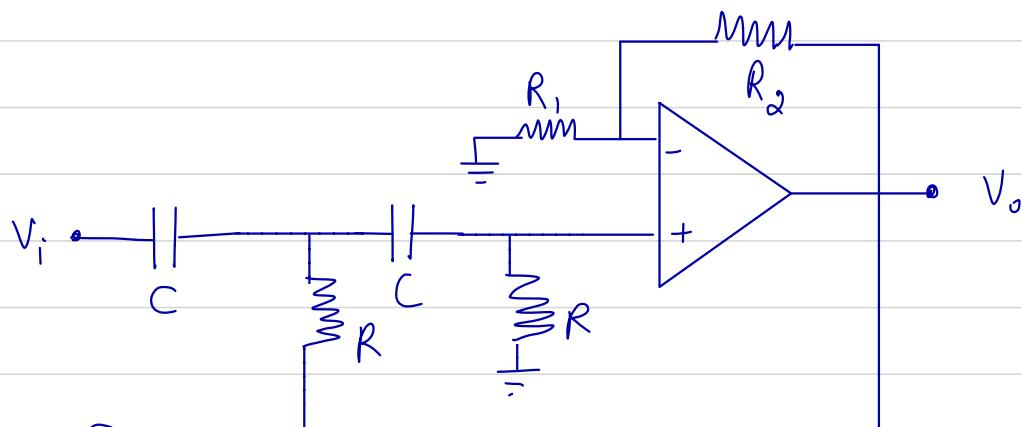

$$V_o = \frac{k (R C_s)^2}{(R C_s)^2 + (3-k) R C_s + 1} V_i$$

$$\begin{bmatrix} 1 & Y_{SC} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y_R & 1 \end{bmatrix} \begin{bmatrix} 1 & Y_{SC} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y_R & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{1}{RCA} & \frac{1}{sC} \\ \frac{1}{R} & 1 \end{bmatrix} \begin{bmatrix} 1 + \frac{1}{RCA} & \frac{1}{sC} \\ \frac{1}{R} & 1 \end{bmatrix}$$

$$\frac{V_p}{V_o} = \frac{1}{A} = \frac{1}{\left(1 + \frac{1}{RCS}\right)^2 + \frac{1}{RC_s}}$$

$$V_p = \frac{R^2 C^2 A^2}{(RCS)^2 + 3RCS + 1} V_o$$

$$\therefore V_o = \left(1 + \frac{R_2}{R_1}\right) V_p = k V_p = \frac{k R^2 C^2 A^2}{(RCS)^2 + 3RCS + 1}$$

$$V_o = k V_p$$

$$\frac{V_i - V_1}{\frac{1}{sC}} = \frac{V_1 - V_o}{R} + \frac{V_1 - V_p}{\frac{1}{sC}}$$

$$\frac{V_1 - V_p}{\frac{1}{sC}} = \frac{V_p}{R}$$

$$\therefore V_i - V_1 = \frac{V_1 - V_o}{RCA} + V_1 - V_p$$

$$V_i = V_p + \frac{V_p}{RCA}$$

$$\therefore V_i = \frac{-V_o}{RCA} + 2V_1 - \frac{V_1}{RCS} - V_p$$

$$= \frac{-V_o}{RCA} - V_p + \frac{2V_p}{RCA} + \frac{2V_p}{RCS} + \frac{V_p}{RCS} + \frac{V_p}{(RCA)^2}$$

$$\therefore V_i = \frac{(3-k)}{RCA} V_p + \frac{V_p}{(RCS)^2} + V_p$$

$$V_i = \frac{V_0}{R} \left[\frac{(RC_1)^2 + (3-k)RC_1 + 1}{(RC_1)^2} \right]$$

$$\therefore \frac{V_0}{V_i} = H(s) = \frac{k(RC_1)^2}{(RC_1)^2 + (3-k)RC_1 + 1}$$

$$H(j\omega) = \frac{k \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{Q\omega_0} + 1}$$

$$|H(j\omega)| = \frac{k \left(\frac{\omega}{\omega_0}\right)^2}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2}}$$

$$\angle H = 180^\circ - \tan^{-1} \left(\frac{\omega/Q\omega_0}{1 - \left(\frac{\omega}{\omega_0}\right)^2} \right)$$


ω	$ H $	$\angle H$
0	0	180°
ω_0	$\frac{k}{Q}$	90°
$\omega \gg \omega_0$	$\frac{k}{\omega^2}$	0°

$$Q=2, K=2.5$$

$$Q=1, K=2$$

$$Q=0.707, K=1.586$$

$$Q=0.5, K=1$$

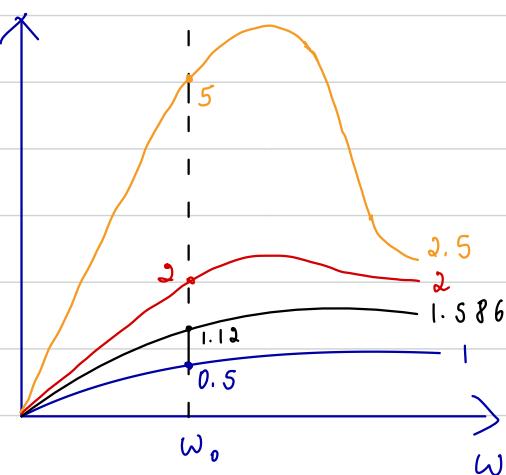

Butterworth response:

Pole frequency = cutoff frequency.

$$Q = 0.707 = \frac{1}{\sqrt{2}}$$

Consider the general equation for LPF:

$$|H(j\omega)| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2}}$$


$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^4}}$$

$$Q = 0.707$$

For n^{th} order Butterworth response:


$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^{2n}}}$$

n	$ H $ at		
	$\omega = 0.9\omega_0$	$\omega = \omega_0$	$\omega = 1.1\omega_0$
1	0.746 (-2.545 dB)	0.71 (-2.97 dB)	0.67 (-3.478 dB)
2	0.78 (-2.15 dB)	0.71 (-2.97 dB)	0.64 (-3.876 dB)
3	0.81 (-1.83 dB)	0.71 (-2.97 dB)	0.6 (-4.43 dB)
4	0.84 (-1.51 dB)	0.71 (-2.97 dB)	0.56 (-5.036 dB)

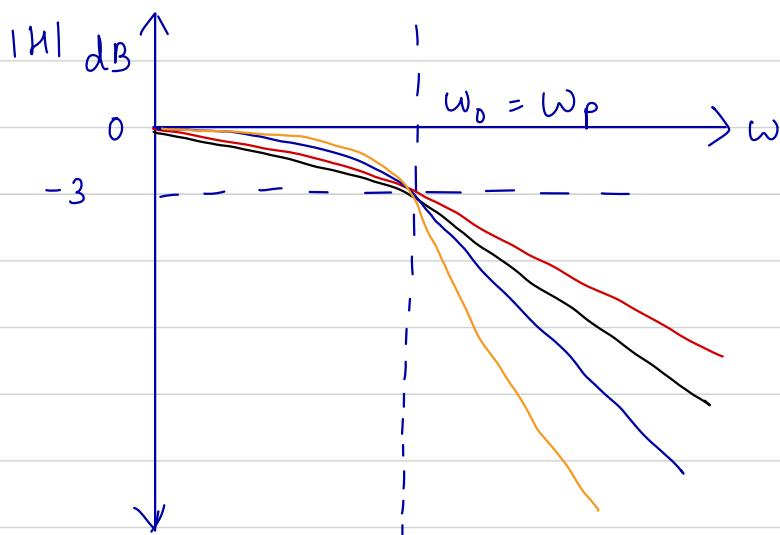



$n = 4$, -80 dB/dec
 $n = 3$, -60 dB/dec
 $n = 2$, -40 dB/dec
 $n = 1$, -20 dB/dec

Consider Sallen key stages:

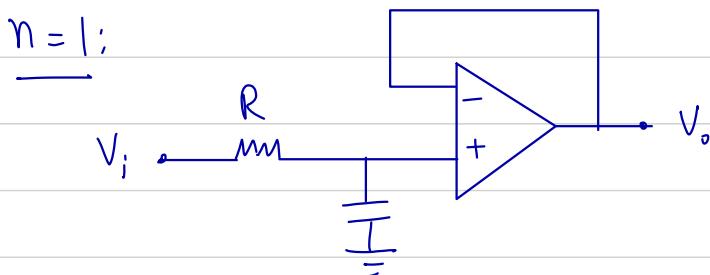

$$H(s) = \frac{1}{1 + RCs} = \frac{1}{1 + \frac{s}{\omega_0}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}}$$

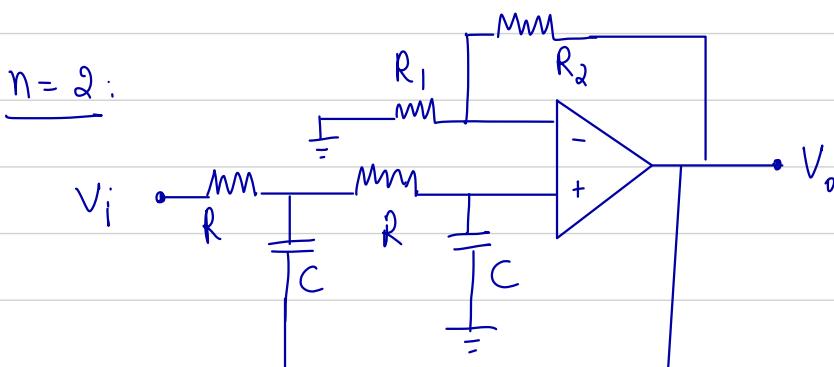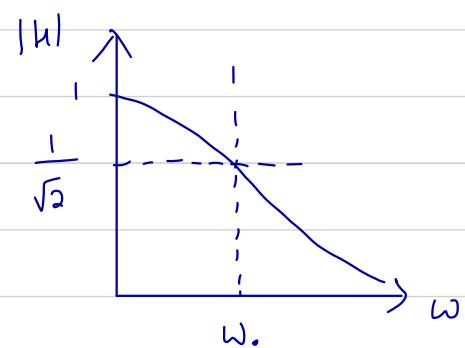

$$Q = \frac{1}{3 - k}$$


$$k = 1 + \frac{R_2}{R_1}$$

At $\omega = \omega_0$, $|H| = k Q$

$$|H(j\omega)| \text{ at } \omega = 0 = k$$

$$|H(j\omega_0)| = \frac{|H(j0^\circ)|}{\sqrt{2}} \quad \therefore Q = \frac{1}{\sqrt{2}}$$

Pole locations

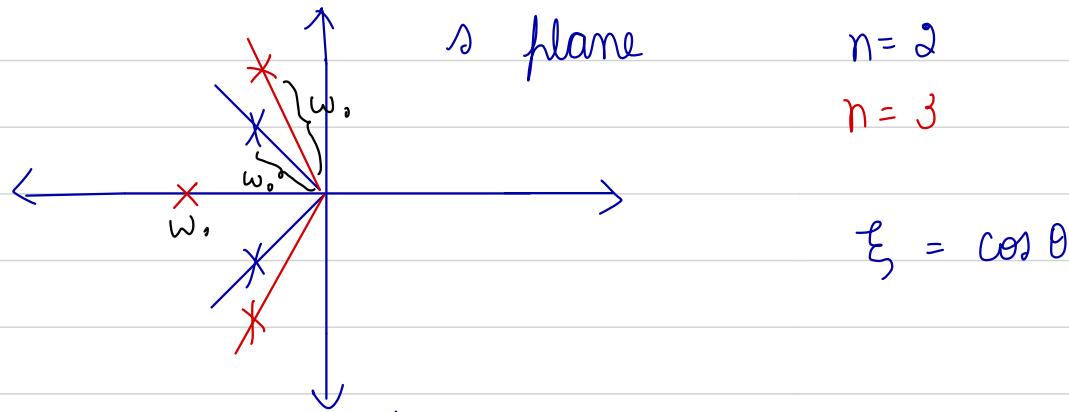


Angle subtended between any 2 poles $= 180/n$

$$\theta = \frac{1}{\sqrt{2}} = \frac{1}{2\xi}$$

where $\xi = 0, 707$

$n=3$:

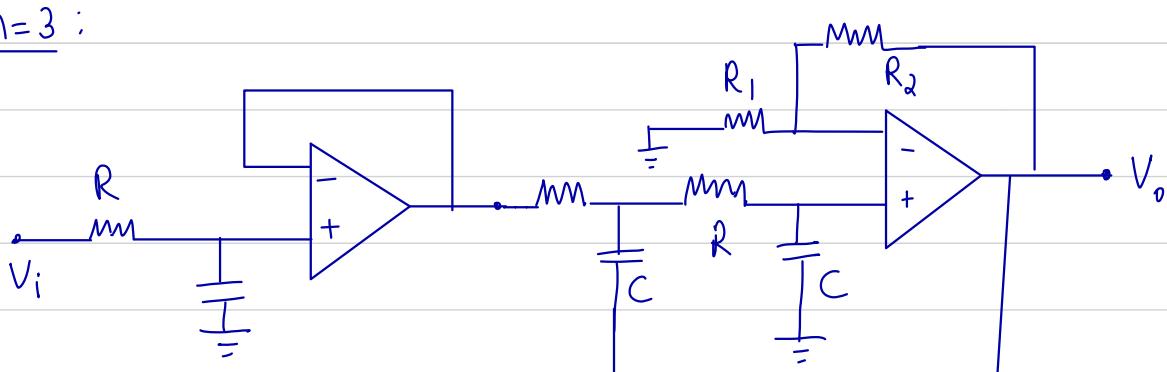

$H_1(j\omega)$

$$H_1(j\omega) \Big|_{\omega=\omega_0} = \frac{1}{\sqrt{2}}$$

DC gain $= K_1 = 1$

$H_2(j\omega)$

$$H_2(j\omega) \Big|_{\omega=\omega_0} = k_2 Q_2$$

DC gain $= k_2$

At $\omega = \omega_0$, $|H(j\omega)| = \frac{|H(j\dot{\omega})|}{\sqrt{2}}$ for Butterworth response


$$|H(j\omega)| = |H_1(j\omega)| |H_2(j\omega)|$$

$$|H(j\omega)| = |H_1(j\omega)| |H_2(j\omega)| = k_1 k_2 = k_2$$

$$|H(j\omega)|_{\omega=\omega_0} = \frac{k_2}{\sqrt{2}}$$

$$\frac{k_2 Q_2}{\sqrt{2}} = \frac{k_2}{\sqrt{2}}$$

$$\Rightarrow Q_2 = 1, \quad k_2 = 2$$

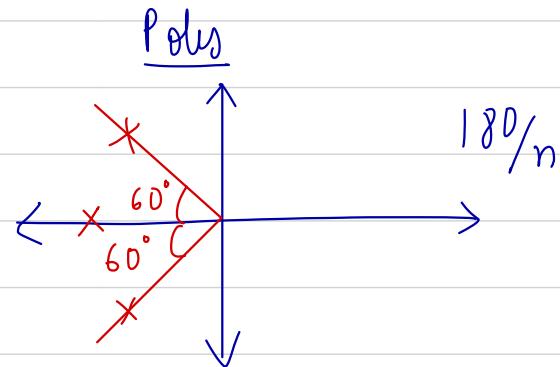


$$H(s) = \frac{k_2}{(1+s)(s^2 + s + 1)}$$


with $\omega_0 = 1 \text{ rad/s}$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^6}}$$

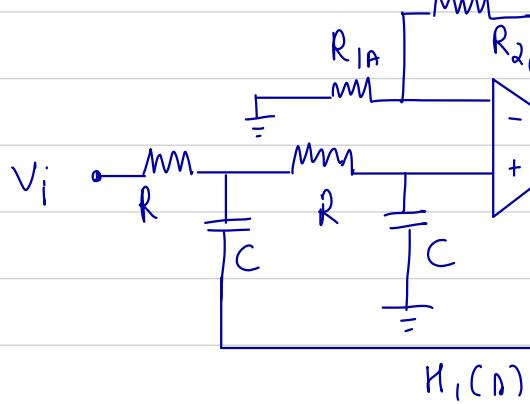Fourth order Sallen-key Butterworth response



$$k_1, Q_1, \omega_0$$

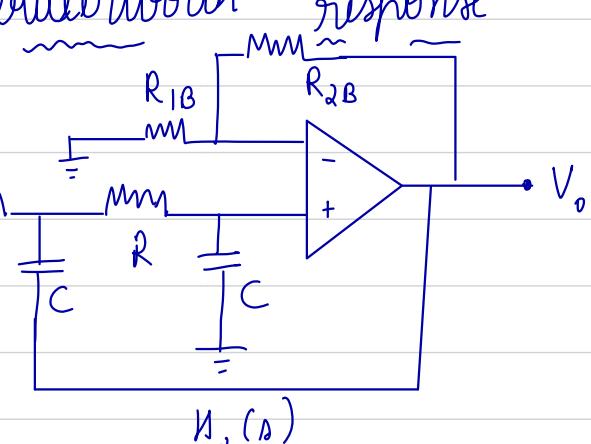

$$k_2, Q_2, \omega_0$$

$$|H(j\omega)| = |H_1(j\omega)| |H_2(j\omega)|$$

$$= k_1 k_2$$

$$|H(j\omega_0)| = |H_1(j\omega_0)| |H_2(j\omega_0)|$$


$$= k_1 Q_1 k_2 Q_2$$

$$|H(j\omega_0)| = \frac{|H(j\omega)|}{\sqrt{2}}$$

$$\frac{k_1 k_2}{\sqrt{2}} = k_1 k_2 Q_1 Q_2$$

$$Q_1 Q_2 = \frac{1}{\sqrt{2}}$$
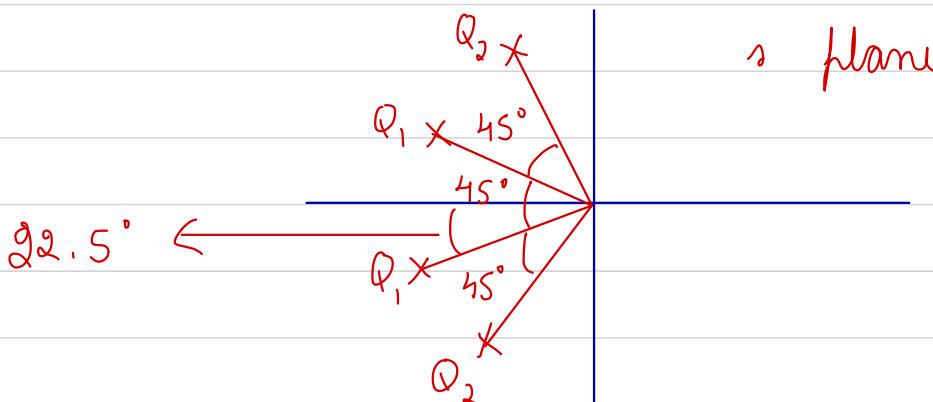
$$H \text{ poles: } \frac{180}{2} = 45^\circ$$



$$Q_1 = \frac{1}{2 \xi_1} = \frac{1}{2 \cos \theta_1} = \frac{1}{2 \cos(22.5^\circ)} = 0.5414$$

$$Q_2 = \frac{1}{2 \xi_2} = \frac{1}{2 \cos \theta_2} = \frac{1}{2 \cos(45^\circ + 22.5^\circ)} = 1.306,$$

$$Q_1 Q_2 = \frac{1}{\sqrt{2}}$$

$$K_1, K_2 \Rightarrow K_1 = 3 - \frac{1}{Q_1} = 1.153 = 1 + \frac{R_{2A}}{R_{1A}}$$

$$K_2 = 3 - \frac{1}{Q_2} = 2.234 = 1 + \frac{R_{2B}}{R_{1B}}$$


$$K_1 K_2 = |H(j0^\circ)| = 2.5758$$

$$H(j\omega) = \frac{k_1 k_2}{\left[\left(\frac{1}{\omega_0} \right)^2 + \frac{1}{Q_1 \omega_0} + 1 \right] \left[\left(\frac{1}{\omega_0} \right)^2 + \frac{1}{Q_2 \omega_0} + 1 \right]}$$


$$|H(j\omega)| = \frac{k_1 k_2}{\sqrt{1 + \left(\frac{\omega}{\omega_0} \right)^8}}$$

Experiment 10: Comparator Σ Schmitt triggers


Comparator:

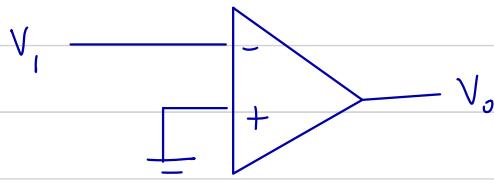

→ Zero crossing
Detector (ZCD)


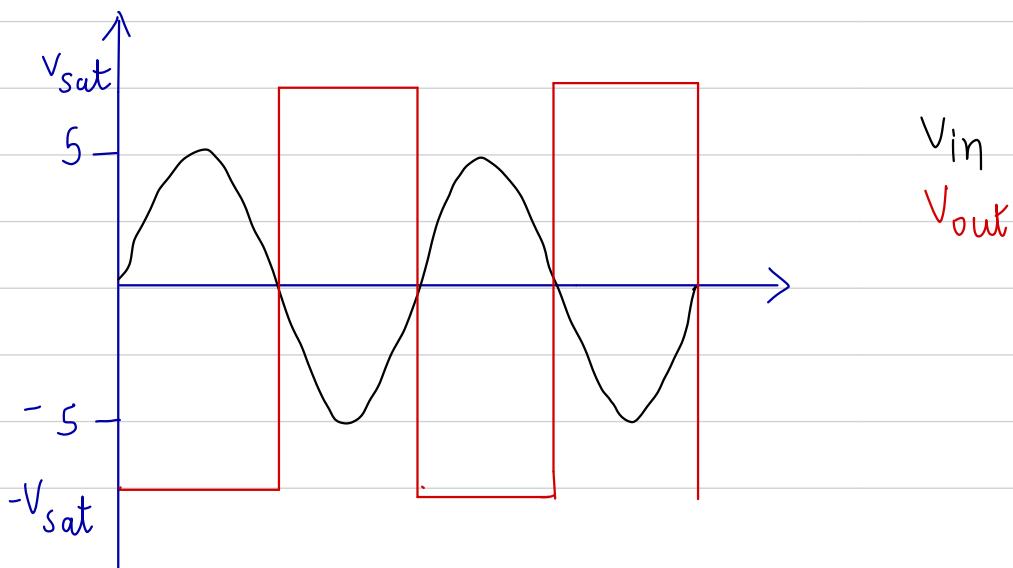


7m lab:

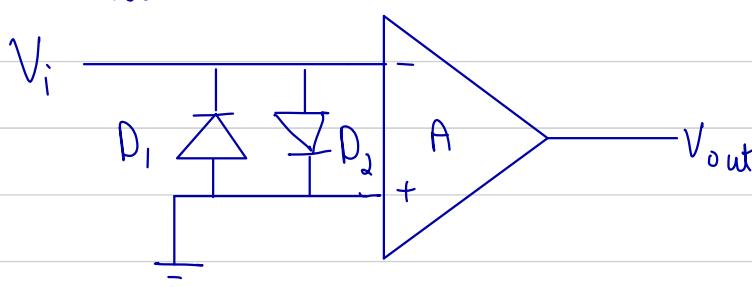


D_1 & D_2 are connected to maintain small differential voltage.

To detect 3V crossing:

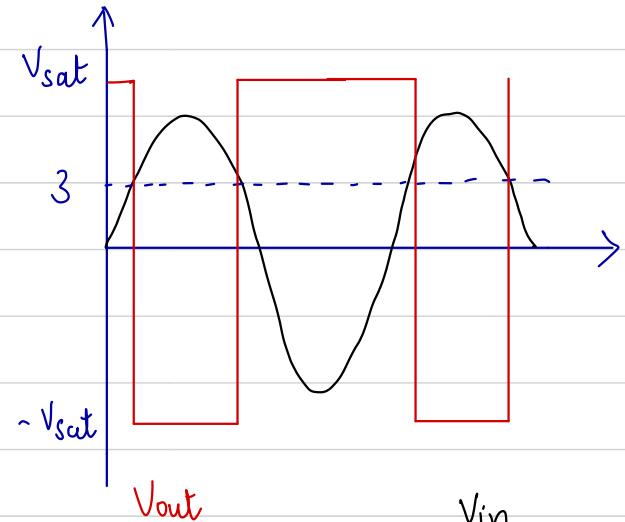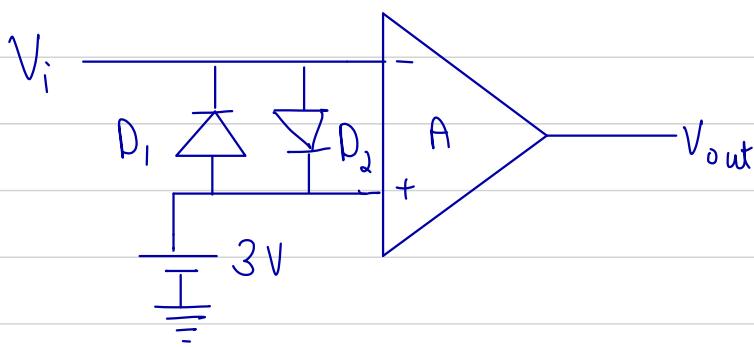

Q> For $V_{in} = 5 \sin 1000\pi t$. Indicate all the salient features assuming ideal shamp comparators with power supply $\pm 12V$ with $V_{ref} = 3V$


Ans

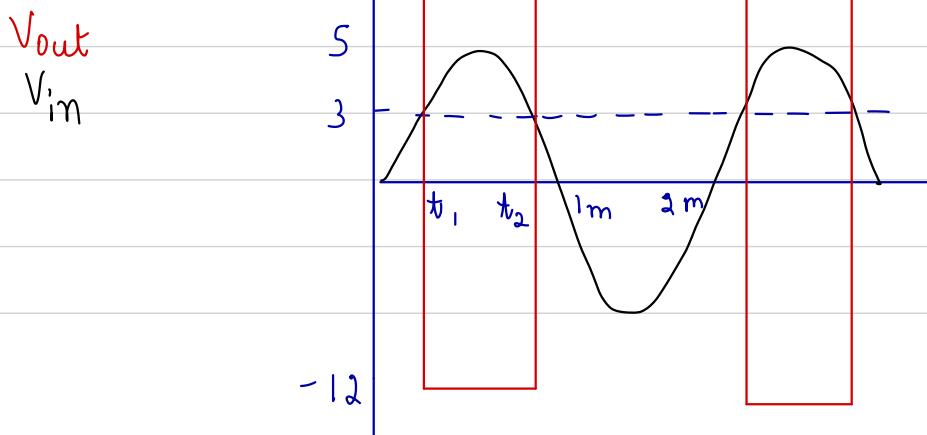


$$t_1 = 0.2 \text{ ms}$$

$$t_2 = \frac{T}{2} - t_1$$

$$= 0.8 \mu\text{s}$$

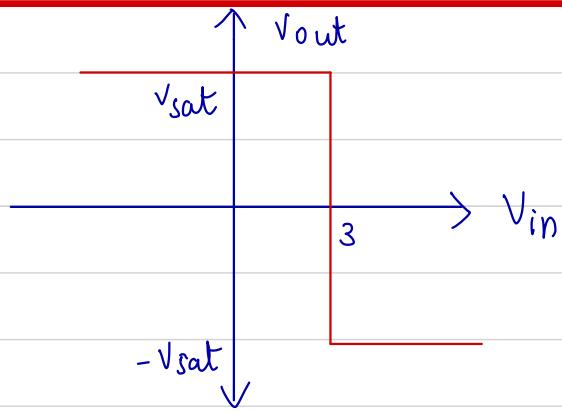


i> Inverting Schmitt trigger:

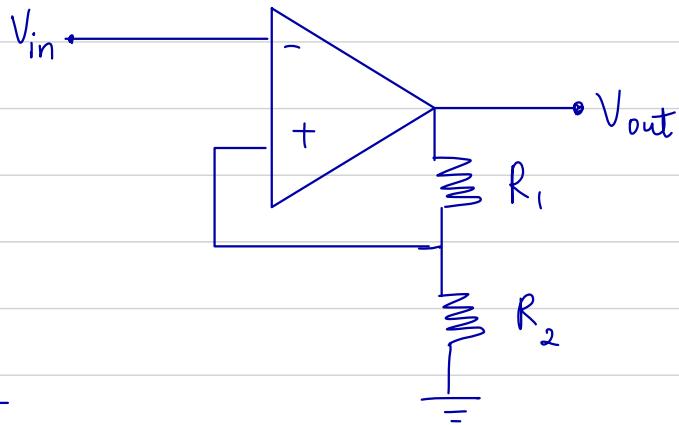



reinforce Perturbation (noise / disturbance)
 \rightarrow Regenerative effect

NOTE:

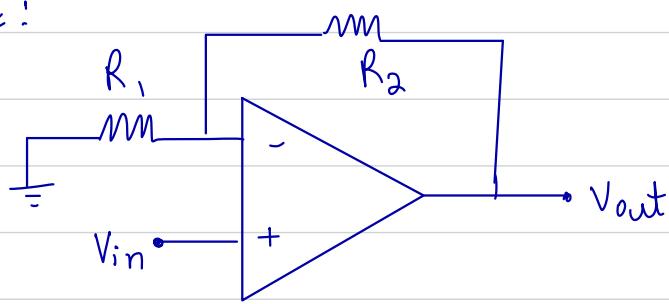

\rightarrow Negative feedback
 \rightarrow Neutralizes Perturbation
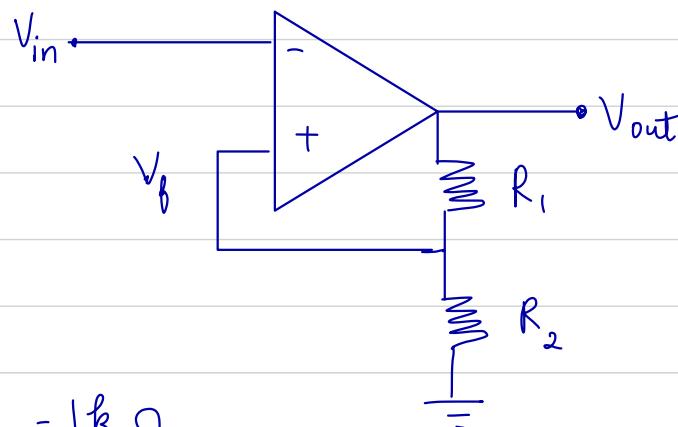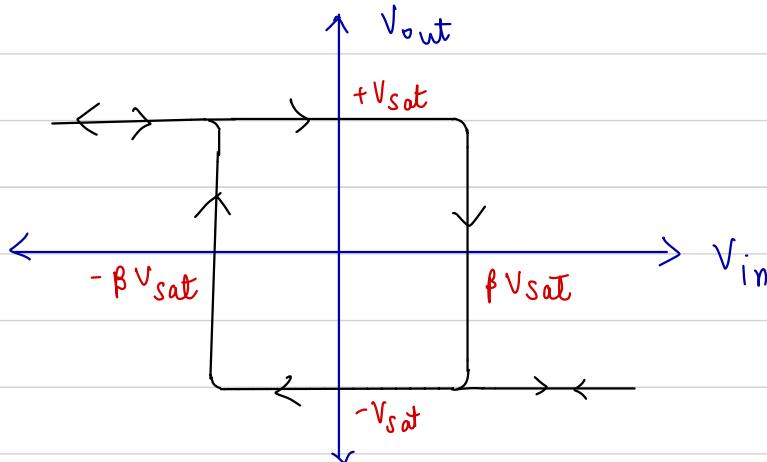
$$V_f = \frac{R_2}{R_1 + R_2} V_{sat} = \beta V_{sat}$$



$$R_2 = 1 k\Omega$$


$$R_1 = 3 k\Omega$$


$$ff \quad V_{sat} = 12$$

$$\beta = \frac{R_2}{R_1 + R_2}$$

$$\beta = \frac{1}{4}$$

$$\therefore V_f = 3 V_i$$

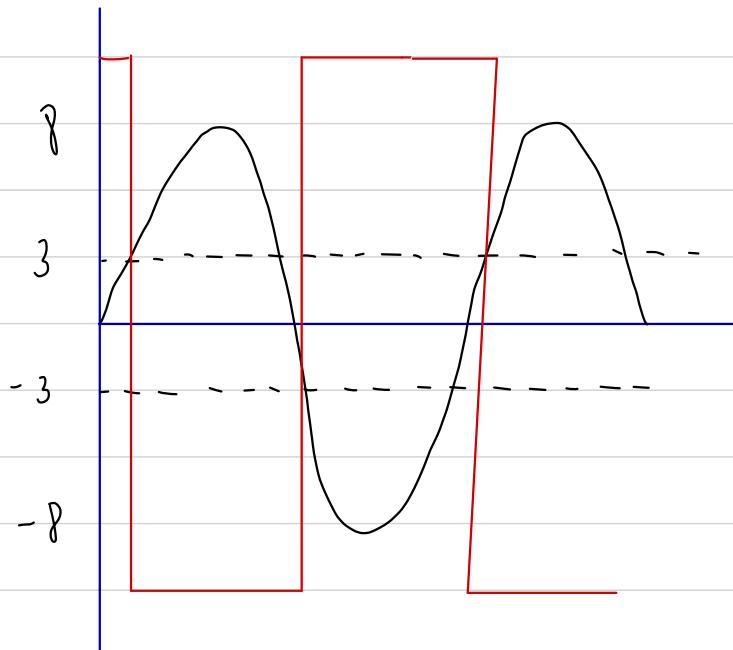

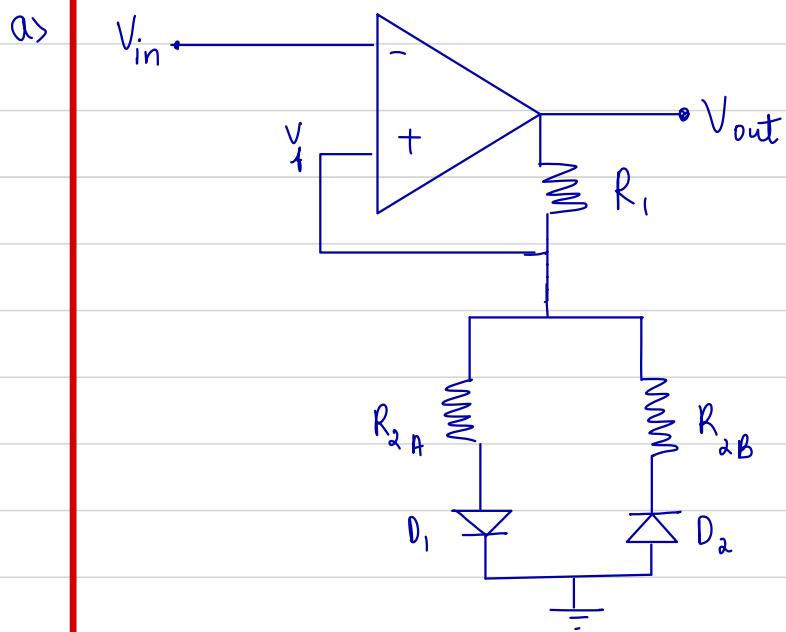

$$f_f \quad V_o = V_{sat}$$

$$V_f = \frac{R_{2A}}{R_{2B} + R_1} V_{sat} \quad (\text{Ideal})$$

$$f_f \quad V_o = -V_{sat}$$

$$V_f = -\frac{R_{2B}}{R_{2B} + R_1} (V_{sat}) \quad (\text{Ideal})$$


Practical :

$$V_o = V_{sat}$$

$$V_f = \frac{R_{2A}}{R_{2B} + R_1} (V_{sat} - V_{D_{on}})$$

$$V_o = -V_{sat}$$
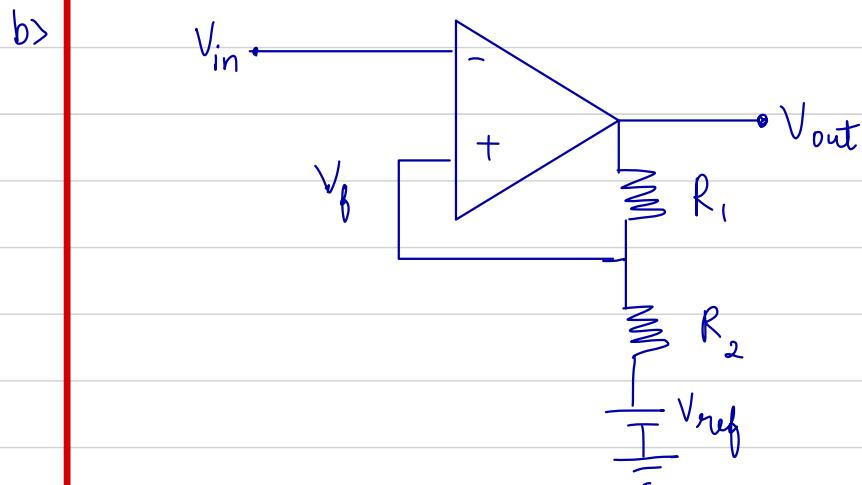
$$V_f = -\frac{R_{2B}}{R_{2B} + R_1} (V_{sat} - V_{D_{on}})$$



$$V_f > V_i \rightarrow V_o = V_{sat}$$

$$V_f < V_i \rightarrow V_o = -V_{sat}$$

$$V_f = \frac{R_2 V_{sat}}{R_1 + R_2} + \frac{R_1 V_{ref}}{R_1 + R_2} = V_{UT}$$

at $V_o = V_{sat}$

UT \rightarrow upper

threshold

LT - lower threshold

$$\text{at } V_o = -V_{sat}, \quad V_f = \frac{-R_2 V_{sat}}{R_1 + R_2} + \frac{R_1 V_{ref}}{R_1 + R_2} = V_{LT}$$


$$\text{Also } V_{VT} = \beta V_{sat} + \frac{R_1}{R_2} \beta V_{ref} \quad \text{at } V_o = V_{sat}$$

$$V_{LT} = -\beta V_{sat} + \frac{R_1}{R_2} \beta V_{ref} \quad \text{at } V_o = -V_{sat}$$

$$V_{VT} - V_{LT} = 2\beta V_{sat} \rightarrow \text{width of hysteresis curve}$$

$$V_{VT} + V_{LT} = 2 \frac{R_1}{R_2} \beta V_{ref}$$

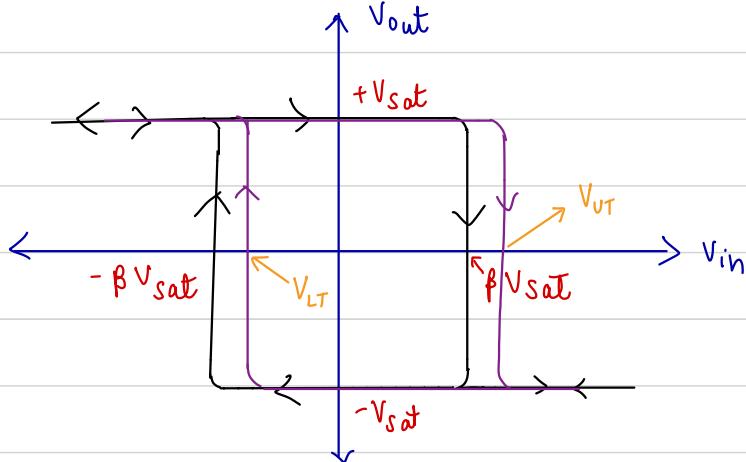$V_{VT} - V_{LT}$ is also known as Deadzone or deadband



Q) Design a schmitt trigger for $V_{VT} = 5 \text{ V}$ $V_{LT} = -3 \text{ V}$

$$\text{Ans } V_{VT} = \beta V_{sat} + \frac{R_1}{R_2} \beta V_{ref}$$

$$R_2 = 1 \text{ k}\Omega$$

$$R_1 = 2 \text{ k}\Omega$$


$$\beta = \frac{R_2}{R_1 + R_2} = \frac{1}{3}$$

$$V_{sat} = 12$$


$$\therefore 5 = 4 + \frac{2}{3} V_{ref}$$

$$\therefore V_{ref} = 1.5 V_d$$

ii) Non Inverting Schmitt trigger

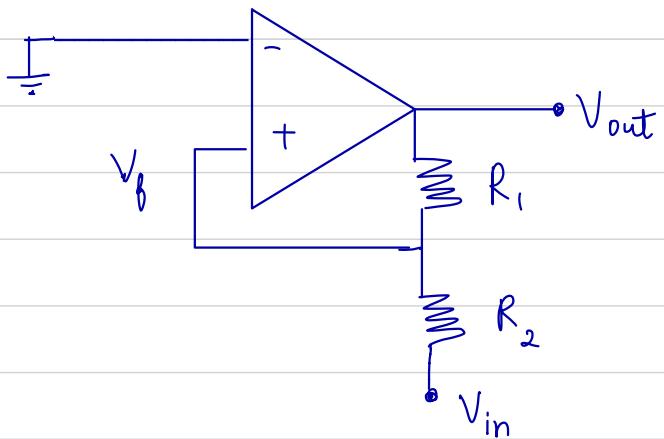

Hysteresis curve:

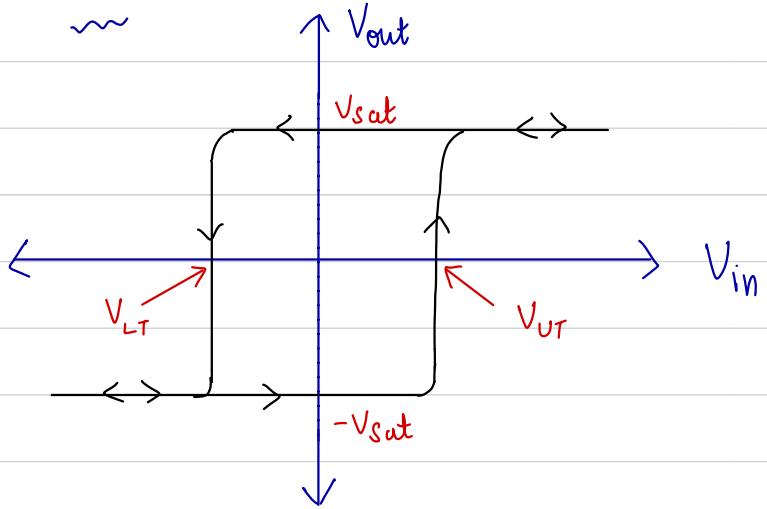

Non inverting Schmitt trigger = Inverting schmitt trigger + ZCD.

$$V_f = \frac{R_2 V_{sat}}{R_1 + R_2} + \frac{R_1 V_i}{R_1 + R_2}$$

at $V_o = V_{sat}$

$$V_f > 0 \longrightarrow V_o = +V_{sat}$$

$$V_f < 0 \longrightarrow V_o = -V_{sat}$$

$$\frac{R_2 V_{sat}}{R_1 + R_2} > \frac{-R_1 V_i}{R_1 + R_2} \quad \text{at } V_o = V_{sat}$$

$$\Rightarrow V_i > \frac{-R_2}{R_1} V_{sat}$$

$$\therefore V_{LT} = -\frac{R_2}{R_1} V_{sat}$$

$$V_f = \frac{-R_2 V_{sat}}{R_1 + R_2} + \frac{R_1 V_i}{R_1 + R_2} \quad \text{at } V_o = -V_{sat}$$

$$\frac{R_1 V_i}{R_1 + R_2} < \frac{-R_2 V_{sat}}{R_1 + R_2}$$

$$V_i < \frac{R_1}{R_2} V_{sat}$$

$$\Rightarrow V_{UT} = \frac{R_2}{R_1} V_{sat}$$

If V_{ref} is used.


$$\text{at } V_o = V_{sat}, \quad V_f > V_{ref}$$

$$\text{at } V_o = -V_{sat}, \quad V_f < V_{ref}$$

$$\therefore V_{UT} = \frac{R_1 + R_2}{R_1} V_{ref} + \frac{R_2}{R_1} V_{sat}$$

$$\therefore V_{LT} = \frac{R_1 + R_2}{R_1} V_{ref} - \frac{R_2}{R_1} V_{sat}$$

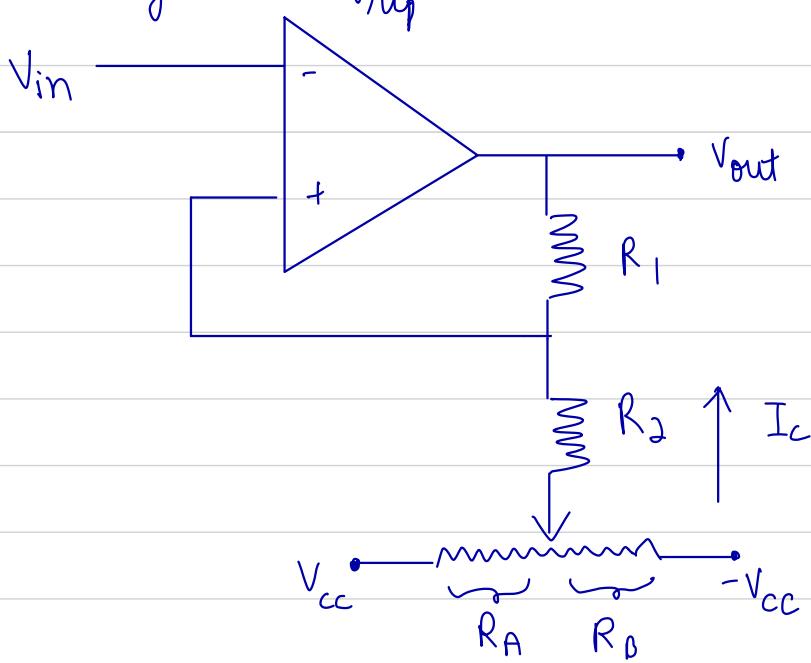To get V_{ref} we connect in following manner





$$V_{ref} = \frac{R_A}{R} (-V_{cc}) + \frac{R_B}{R} V_{cc} \quad (R \rightarrow \text{Total resistance of potentiometer})$$

To avoid damage of opamp

$$R_1, R_2 \gg R \quad \text{so that } I_A \approx I_B \quad \text{if } I_C = 0$$

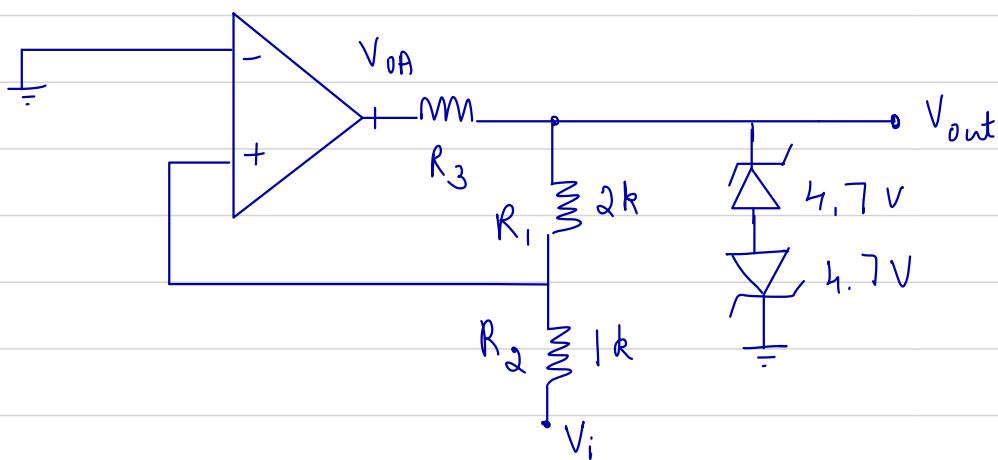Ex: Plot V_o vs V_i . Find R_3 min. $V_i = 8 \sin \omega t$
Power supply = 12V





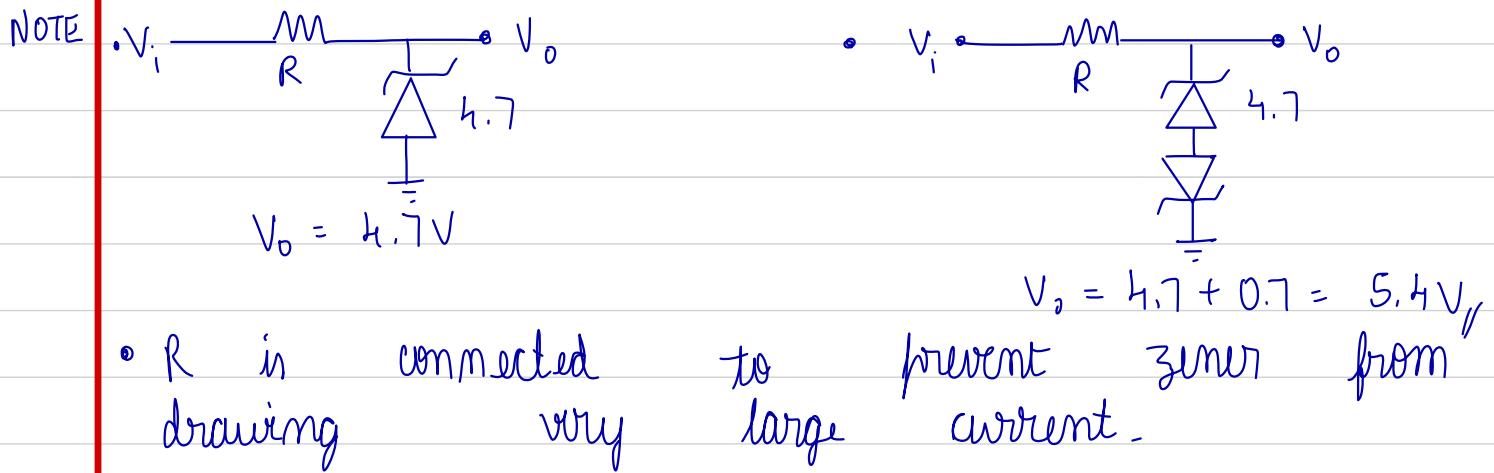

Ans $\therefore V_{\text{clamp}} = \pm 5.4 \text{ V}$

$$V_{UT} = \frac{R_2}{R_1} = \frac{1}{2} \times 5.4 = 2.7 \text{ V}, \quad \text{by } V_{LT} = -2.7 \text{ V}$$

$$V_{\text{out}} = \pm 5.4 \text{ V}$$

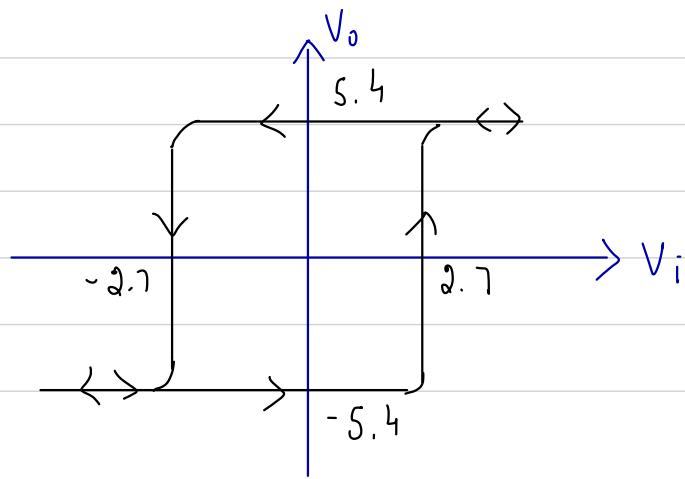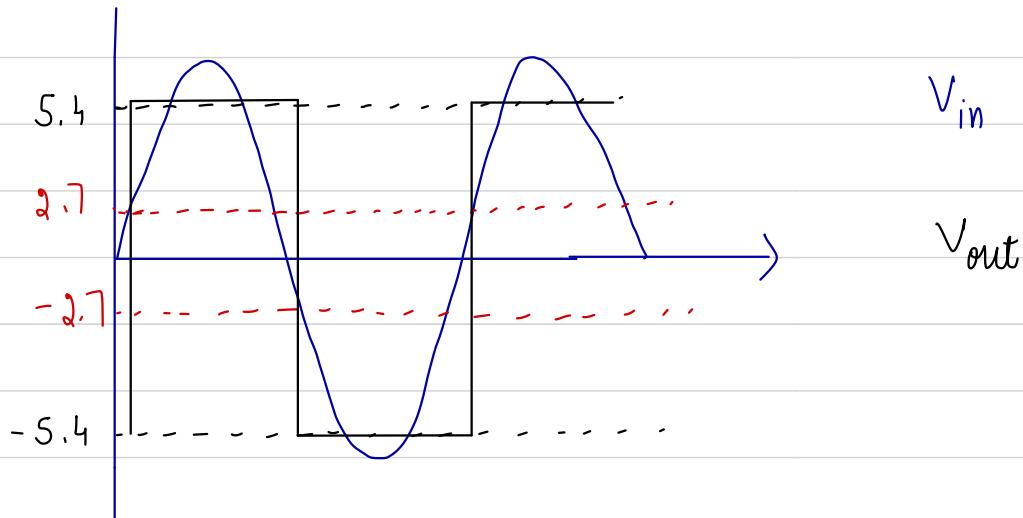



$$12 - 5.4 < 25 \text{ mA}$$

R_3

$$R_3 > 264 \Omega,$$


$$\therefore R_3 \text{ min} = 264 \Omega$$

Astable multivibrator

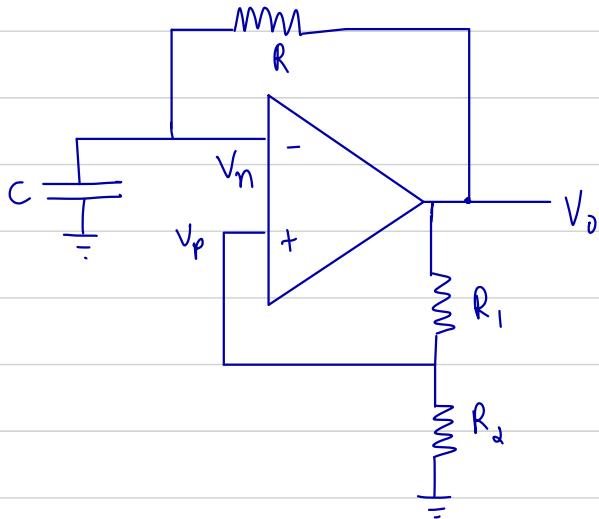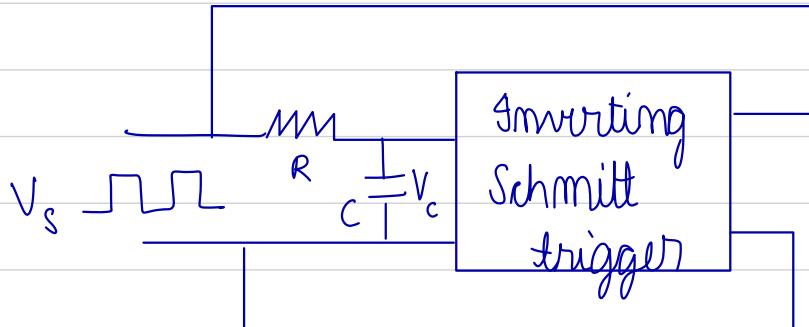

Positive feedback is dominant as there is a capacitor in negative feedback which takes time to change
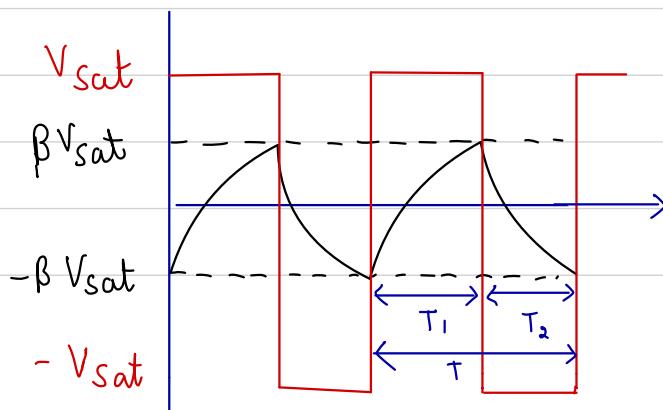
$$V_p = \frac{R_2}{R_1 + R_2} V_{sat} \quad V_{sat} = \beta V_{sat}$$



$$\text{Duty cycle} = 50\%$$

$$T_1 = T_2$$

$$V_C = V_f + (V_i - V_f) e^{-t/\tau}$$

$$\beta V_{sat} = V_{sat} + (-\beta V_{sat} - V_{sat}) e^{-T_2/RC}$$

$$\beta = 1 - (1+\beta) e^{-T_2/RC}$$

$$e^{-T_2/RC} = \frac{1+\beta}{1-\beta}$$

$$\Rightarrow T_2 = RC \ln \left(\frac{1+\beta}{1-\beta} \right) = T_1$$

$$T_2 = T_1 = RC \ln \left(\frac{2R_2 + R_1}{R_1} \right)$$


$$\therefore T = 2T_2 = 2RC \ln \left(\frac{2R_2 + R_1}{R_1} \right)$$

$$g_f \quad R_1 = R_2$$

$$T = 2RC \ln 3$$

$$T = 2.2RC$$

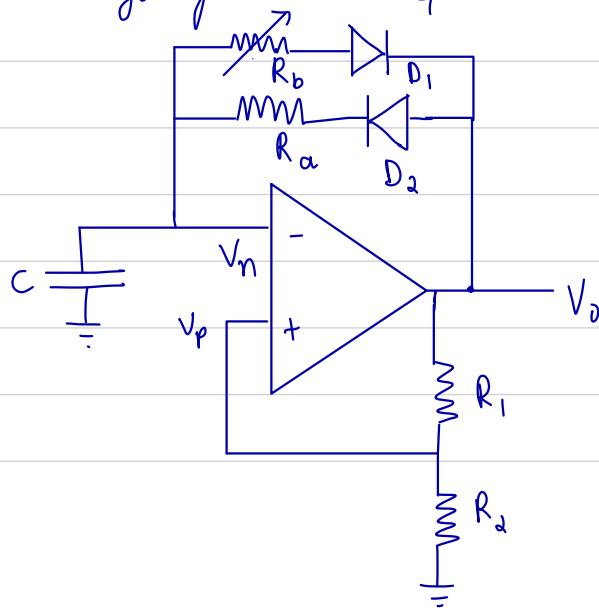To change duty cycle we can either connect V_{ref} or we can have 2 different paths for charging and discharging.




$$T_{ON} = R_a C \ln 3$$

$$T_{OFF} = R_b C \ln 3$$

$$\therefore \text{Duty cycle} = \frac{T_{ON}}{T} = \frac{R_a}{R_a + R_b}$$

Q

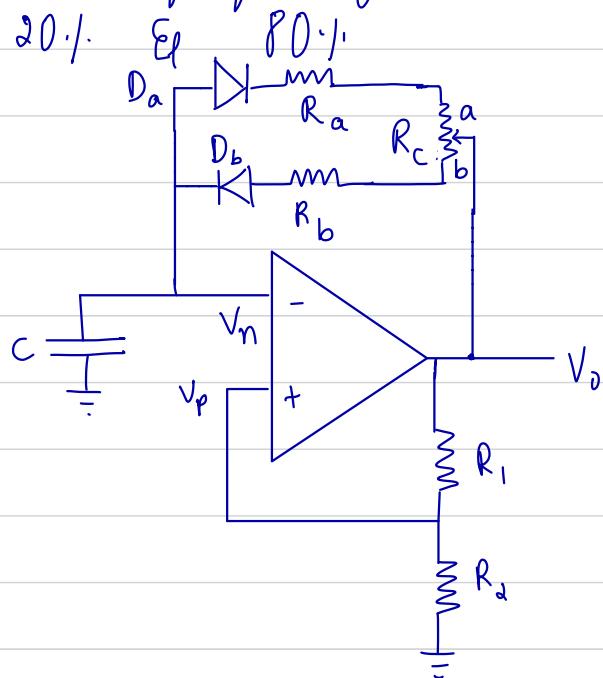Design an Astable multivibrator using an opamp having frequency between 1 kHz and 20 kHz with duty cycle varying



$$T = T_{on} + T_{off} = 1 \text{ ms}$$

$$\text{FOR } 20\% \text{ duty cycle} \quad T_{on} = 0.2 \text{ ms} \\ = 1.1 R C \\ = 1.1 R_b C$$

$$\text{Let } C = 0.1 \mu\text{F}$$

$$\therefore R_b = 1.81 \text{ k}\Omega$$

$$T_{off} = 0.8 \text{ ms} = 1.1 R C = 1.1 (R_a + R_c) C$$

$$R_a = R_b = 1.81 \text{ k}\Omega$$

$$R_c = 5.46 \text{ k}\Omega \quad (\text{Potentiometer})$$

Eg 2: $v_1 = 5 \cos 2\pi 100t \text{ V} - 2 \cos 2\pi 10^3 t \text{ mV}$,

$$v_2 = 5 \cos 2\pi 100t \text{ V} - 2 \cos 2\pi 10^3 t \text{ mV}.$$

Find A_{cm} , A_{dm} , CMRR (in dB).

$$v_o = 25 \cos 2\pi 100t \text{ mV} + \cos 2\pi 10^3 t \text{ V}$$

Ans
 $v_{cm} = \frac{v_1 + v_2}{2} = 5 \cos 2\pi 100t \text{ V}$

$$v_{dm} = v_2 - v_1 = 4 \cos 2\pi \times 10^3 t \text{ mV}$$

$$A_{cm} = \frac{25 \text{ mV}}{5} = 5 \times 10^{-3} = 0.005 //$$


$$A_{dm} = \frac{1}{4} \times 10^3 = 250 //$$

$$\text{CMRR} = \frac{A_{dm}}{A_{cm}} = \frac{250}{0.005} = 50 \times 10^3$$

$$\text{CMRR}_{dB} = 20 \log \frac{A_{dm}}{A_{cm}} = 20 \log (50 \times 10^3) = 93.97 \text{ dB}$$

Eg 3. In the difference amplifier circuits values of resistors are $R_1 = 1.05 \text{ k}\Omega$, $R_2 = 99 \text{ k}\Omega$, $R_3 = 0.998 \text{ k}\Omega$, $R_4 = 100.2 \text{ k}\Omega$.

Find A_{cm} , A_{dm} , CMRR dB.

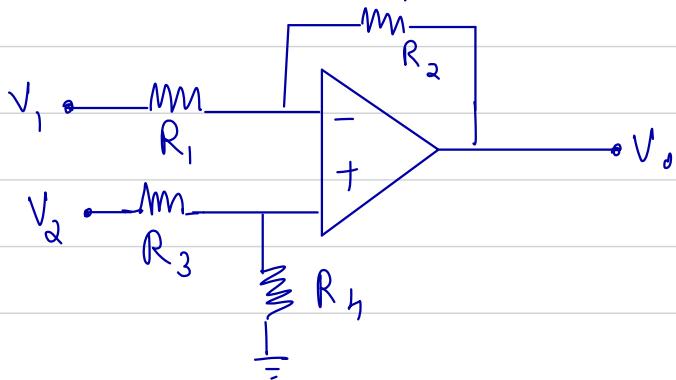

$$V_o = -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_3}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_o$$

$$= \frac{-99}{1.05} V_1 + \left(1 + \frac{99}{1.05}\right) \frac{100.2 V_2}{(100.2 + 0.998)}$$

$$= -94.285 V_1 + 95.285 (0.990) V_2$$

$$V_o \approx 94.3 (V_2 - V_1)$$

$$\Rightarrow A_{dm} \approx 94.3 = 39.49 \text{ dB}$$

When V_{cm} is connected

$$V_o = (-94.285) V_{cm} + 94.33 V_{cm}$$


$$V_o = 0.04715 V_{cm}$$

$$\therefore A_{cm} = -24.392$$

$$\therefore CMRR = 39.49 - (-24.392) = 63,8836 \text{ dB}_{\text{v}}$$

Eg: Single op amp band circuit where
 $V_o = V_y - 2V_x$. Where V_x & V_y are 2 tvc inputs.

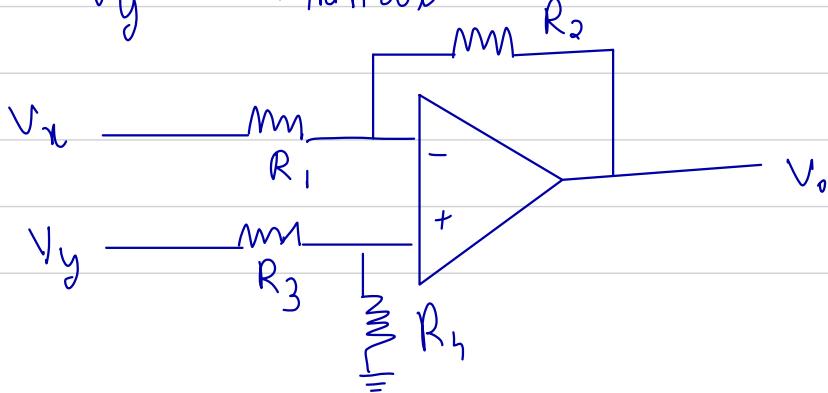Also, sketch V_o for:
a) $V_x = 2 \sin \omega t$, $V_y = 2V$
b) $V_x = V_y = 2 \sin \omega t$



$$V_o = -\frac{R_2}{R_1} V_x + \left(1 + \frac{R_2}{R_1}\right) \frac{R_4 V_y}{R_3 + R_4} V_y$$


$$= -2V_x + V_y$$

$$\frac{R_2}{R_1} = 2 \Rightarrow g_f \quad R_1 = 10 \text{ k}\Omega \quad R_2 = 20 \text{ k}\Omega$$


$$\left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} = 1$$

$$\frac{3R_4}{R_3 + R_4} = 1 \Rightarrow R_4 = 5 \text{ k}\Omega \quad R_3 = 10 \text{ k}\Omega$$

a) $V_o = 2 - 4 \sin \omega t$

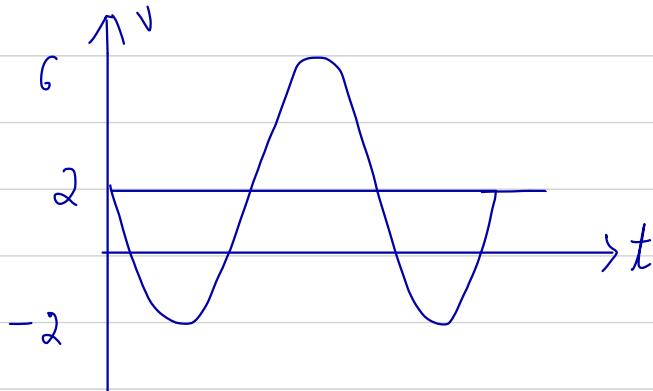


b) $V_o = -4 \sin \omega t$

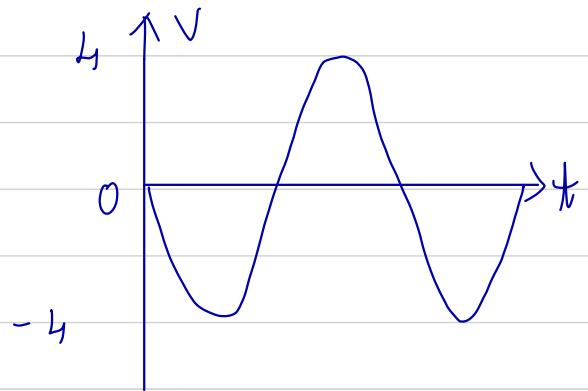

Eg: Using a single opamp and minimum number of resistors design a 4 input amplifier

$$V_o = V_A - 4V_B + 10V_C - 2V_D$$

Ans

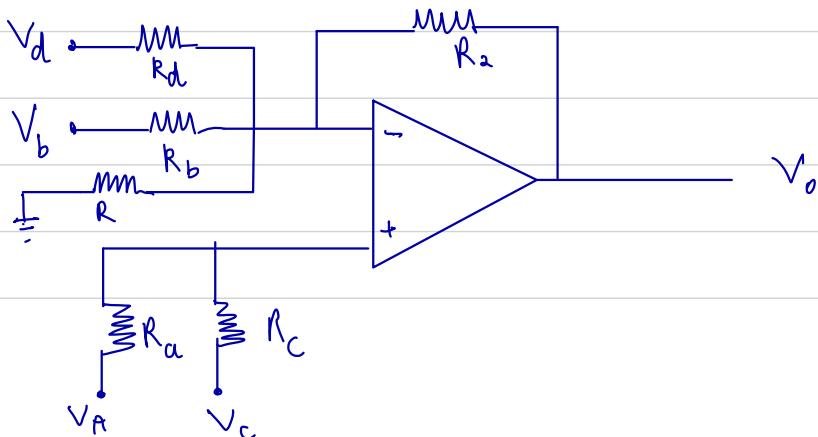

$$V_o = V_A - 4V_b + 10V_c - 2V_D \quad (R_p = R \parallel R_b \parallel R_d)$$

$$\text{But } V_o = \left(1 + \frac{R_a}{R_p}\right) \frac{R_c}{R_a + R_c} V_A - \frac{R_b}{R_2} V_b + \left(1 + \frac{R_d}{R_p}\right) \left(\frac{R_a}{R_c + R_a}\right) V_c - \frac{R_d}{R_2} V_D$$

$$\underline{R_2} = 4 \Rightarrow \text{If } R_B = 10 \text{ k}\Omega \quad R_2 = 40 \text{ k}\Omega$$

R_b

$$\frac{R_2}{R_d} = 2 \quad \therefore R_d = 20 \text{ k}\Omega$$

$$\left(1 + \frac{R_a}{R_p}\right) \frac{R_c}{R_a + R_c} = 1 \rightarrow \textcircled{1} \quad \text{Eq}$$

$$\left(1 + \frac{R_d}{R_p}\right) \left(\frac{R_a}{R_c + R_a}\right) = 10 \rightarrow \textcircled{2}$$

$$\textcircled{2} \div \textcircled{1} \Rightarrow R_a = 10R_c$$

$$\text{If } R_c = 10 \text{ k}\Omega \Rightarrow R_a = 100 \text{ k}\Omega$$

From \textcircled{1}


$$\left(1 + \frac{40}{R_p}\right) \times \frac{1}{11} = 1 \quad \Rightarrow \frac{40}{R_p} = 10$$

$$R_p = 4 \text{ k}\Omega$$

$$\Rightarrow \frac{1}{4} = \frac{1}{R} + \frac{1}{10} + \frac{1}{20} \quad \Rightarrow \frac{1}{R} = \frac{1}{4} - \frac{1}{10} - \frac{1}{20} = \frac{5-2-1}{20} = \frac{2}{20}$$


$$\therefore R = 10 \text{ k}\Omega$$

Final circuit:

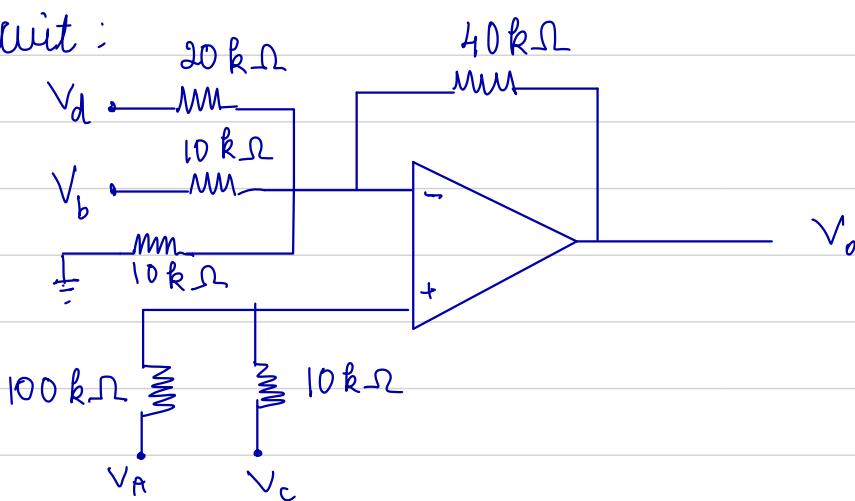

Q1) In some applications such as function generators there is a need to "offset" the amplifier output voltage such that $V_o = V_o + kV_i$; where V_o is offset desired at output. Design a circuit using summing amplifier to realize $V_o = 4 - 5V_i$. You may use the power supply $\pm 12V$ as one of the inputs to provide the desired output offset voltage.

Ans

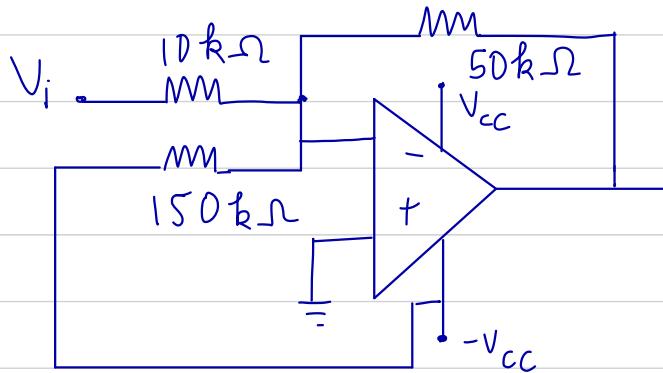

$$V_{cc} = 12V$$


$$V_o = -\frac{50}{10}V_i - \left(\frac{50}{150}\right)(-12)$$

$$V_o = 4 - 5V_i$$

Q2) Design a single opamp band circuit to realize $a > V_o = 12V_i + 6V$

Ans

$$V_{cc} = 12V$$

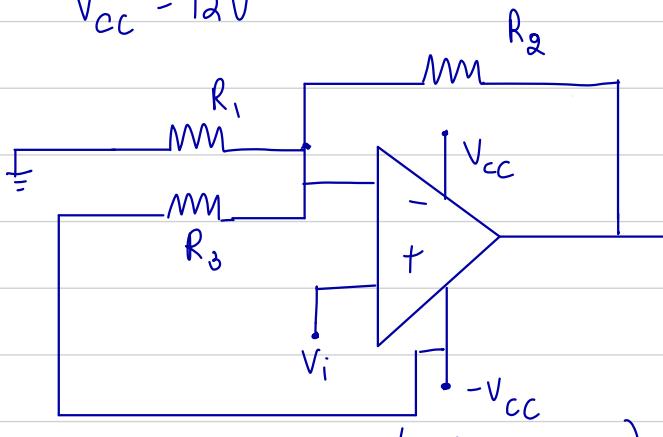

$$b > V_o = 8(V_2 - V_1) - 4V$$

a)

$$V_o = \left(1 + \frac{R_2}{R_1 \parallel R_3}\right) V_i + \left(\frac{-R_2}{R_3}\right) (-12)$$

$$\frac{R_2}{R_3} \times 12 = 6$$

$$\frac{R_2}{R_3} = \frac{1}{2}$$

If

$$R_2 = 10 \text{ k}\Omega$$


$$R_3 = 20 \text{ k}\Omega$$

$$\Rightarrow 1 + 1.0 \left(\frac{1}{R_1} + \frac{1}{20} \right) = 12$$

$$\frac{1}{10} = \frac{1}{R_1} + \frac{1}{20}$$

$$\frac{1}{R_1} = \frac{2(20 - 10)}{200}$$
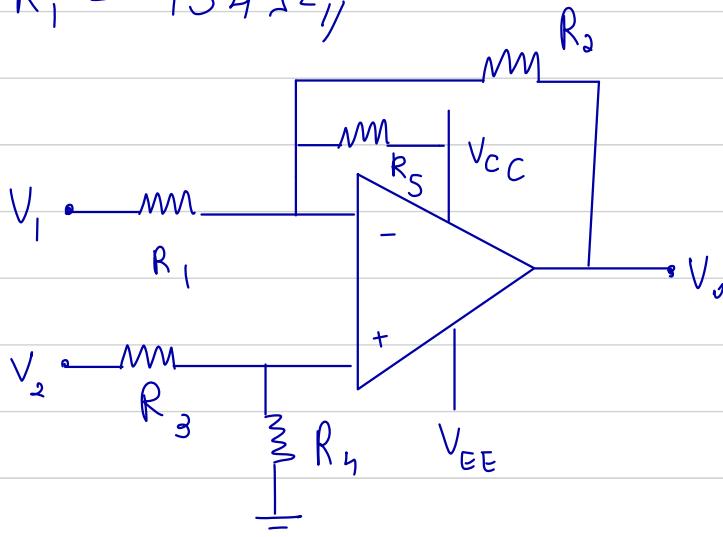
$$\therefore R_1 = 954 \text{ }\Omega_{\text{II}}$$



$$V_o = \left(1 + \frac{R_2}{R_1 \| R_s} \right) \cdot \frac{R_4}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1 - \frac{R_2}{R_s} 12$$


$$\text{Let } R_1 = 10 \text{ k}\Omega \Rightarrow R_3 = 80 \text{ k}\Omega \quad R_s = 240 \text{ k}\Omega$$

$$\text{Let } R_3 = 10 \text{ k}\Omega \Rightarrow R_s = 60.1 \text{ k}\Omega$$

(3) Design a 2 input sum & 2 output difference circuit that yields

the minimum number of components.


Ans

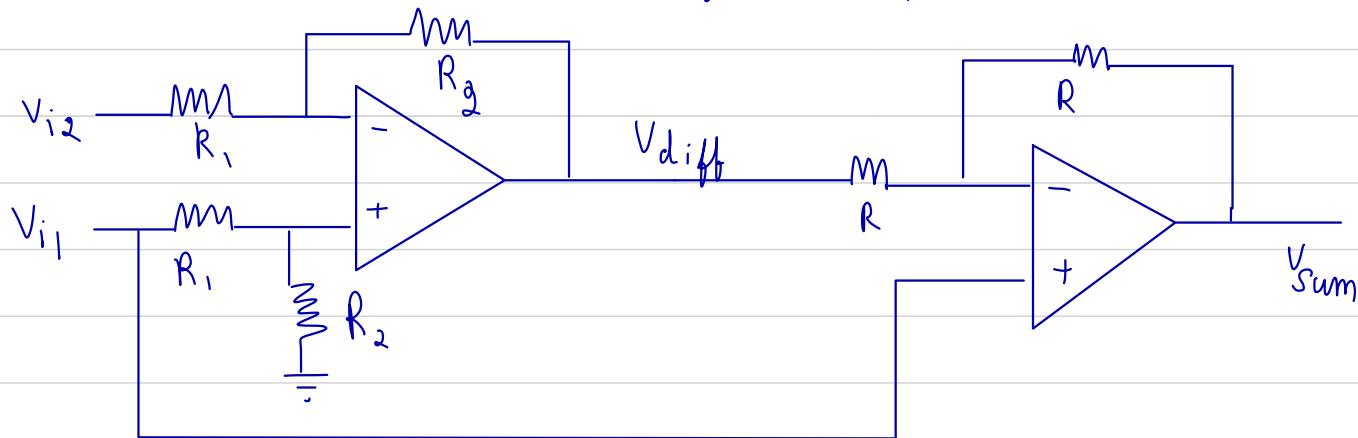

$$V_{\text{diff}} = V_{i2} - V_{i1}$$

$$V_{\text{sum}} = 2V_{i1} - V_{\text{diff}} = 2V_{i1} - V_{i1} + V_{i2} = V_{i1} + V_{i2}$$

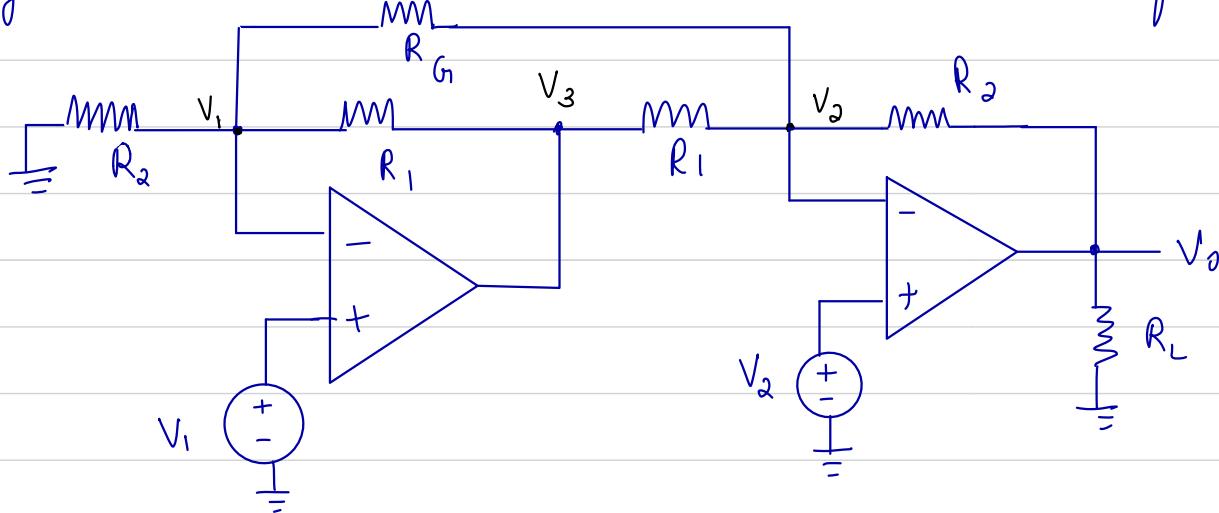Q4) Consider the circuit shown in following figure. Derive V_o in terms of inputs.




Ans

$$\text{1} \Rightarrow \frac{0 - V_1}{R_2} = \frac{V_1 - V_2}{R_g} + \frac{V_1 - V_2}{R_1}$$

$$\text{2} \Rightarrow \frac{V_1 - V_2}{R_g} + \frac{V_3 - V_2}{R_1} = \frac{V_2 - V_0}{R_2}$$


$$\therefore V_o = (V_2 - V_1) \left[1 + \frac{R_2}{R_1} + \frac{2R_2}{R_{Gn}} \right]$$

(Q5) Find V_o

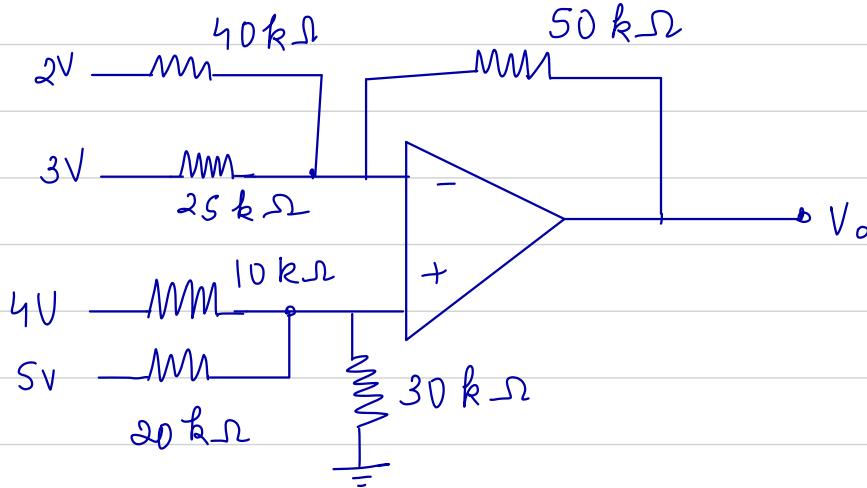


$$\text{Ans} \quad V_o = -\frac{50 \times 2}{40} - \frac{50 \times 3}{25} + 4 \times \left(1 + \frac{50}{15.38}\right) \times \frac{12}{22} + 5 \left(1 + \frac{50}{15.38}\right) \left(\frac{7.5}{27.5}\right)$$
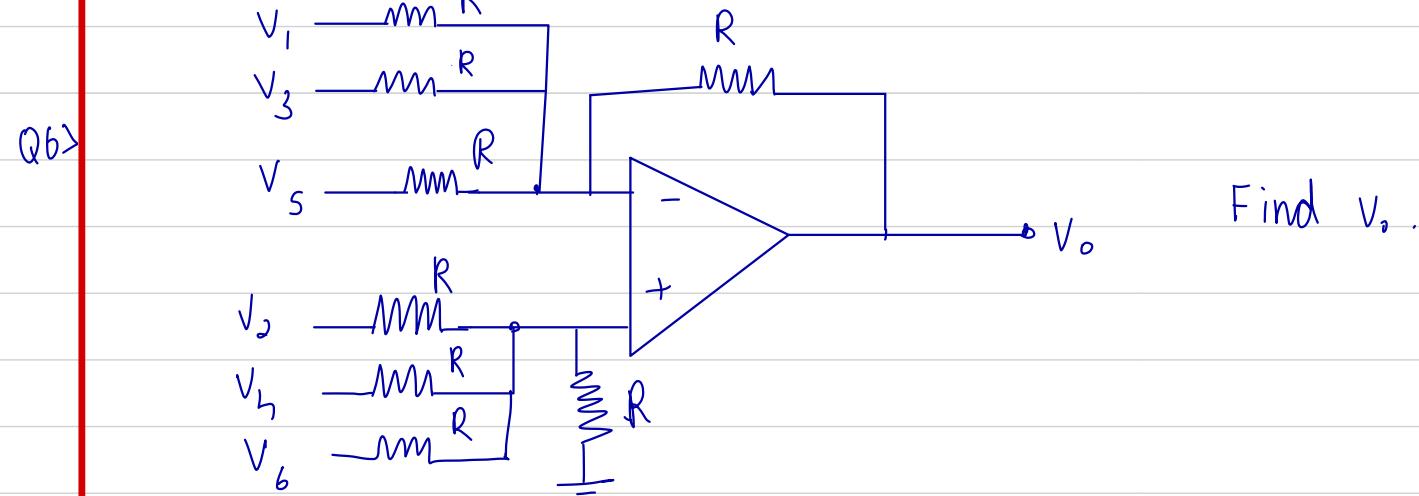
$$= -2.25 - 6 + 9.2727 + 5.79 = 6.56 V_g$$



$$\text{Ans} \quad V_o = V_2 + V_4 + V_6 - V_1 - V_3 - V_s$$


Q7)

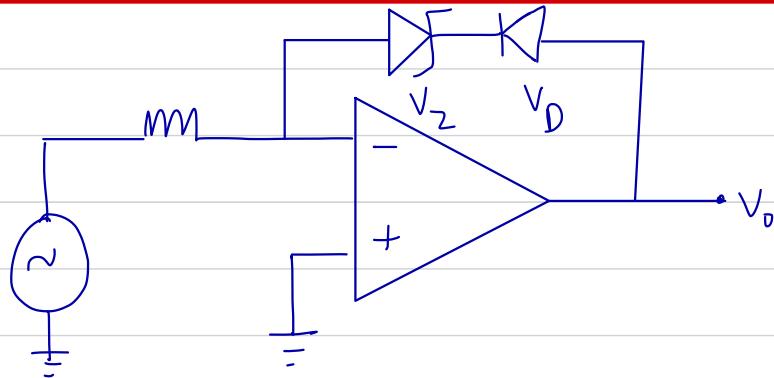


Draw output waveform w.r.t input waveform
and find transfer characteristics

Ans

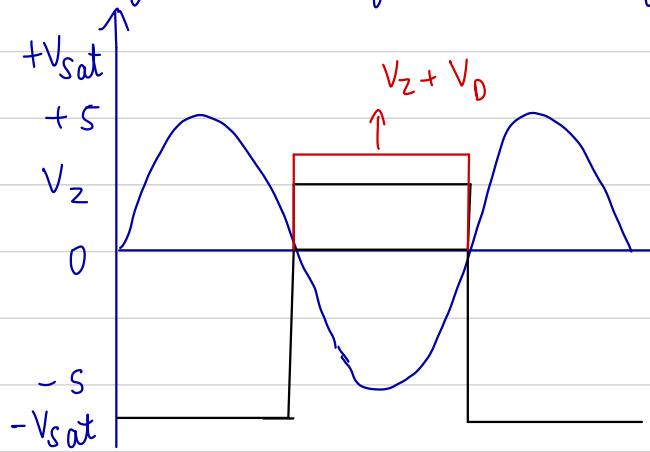During positive cycle, +ve feedback.
During negative cycle, -ve feedback



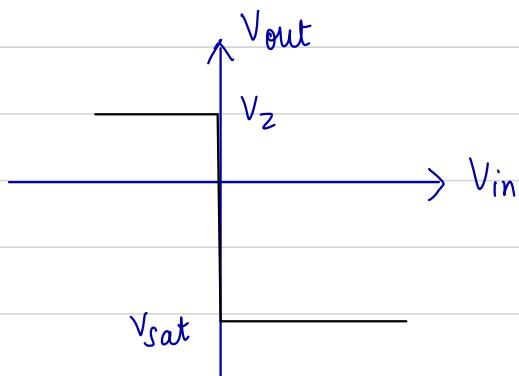
- input
- output for ideal diode
- output for non ideal diode




Q8)

For the circuit shown, plot the transfer characteristics if opamp is with a) $V_{z1} = V_{z2} = 9V$

b) repeat (a) if open loop gain is 10^4

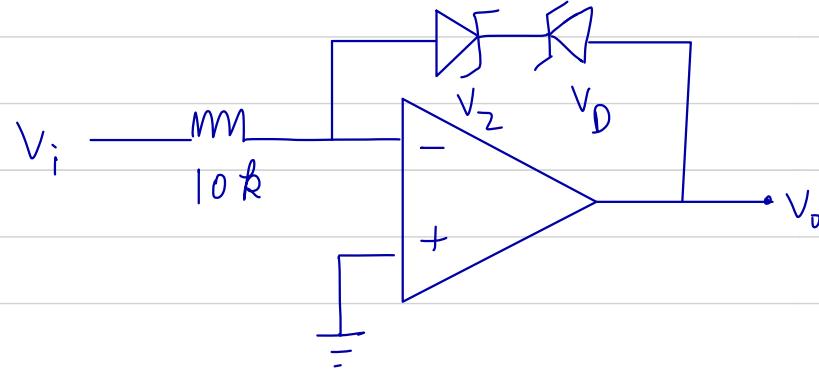


Ans a)

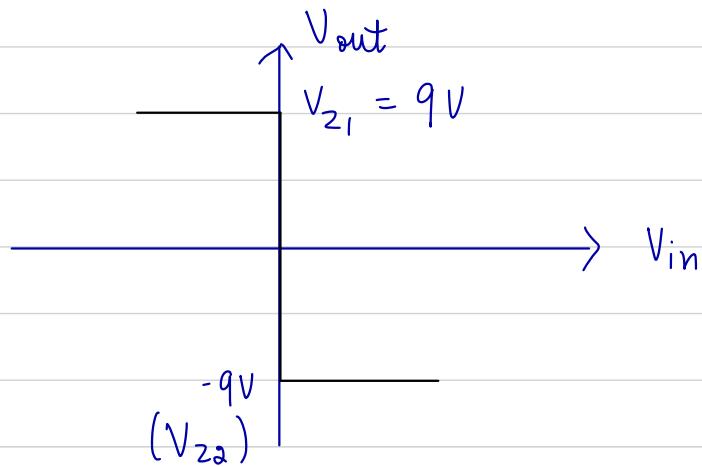


V_o must be greater than V_z

b)

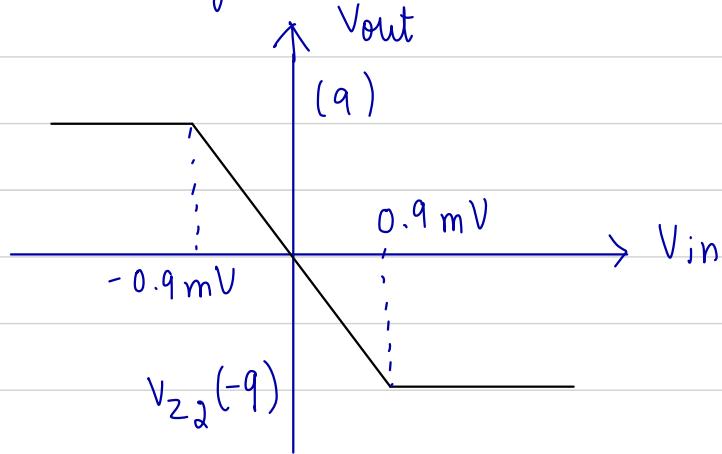

$$V_{id} = \frac{9}{10^4} = 0.9 \text{ mV}$$

Q8)

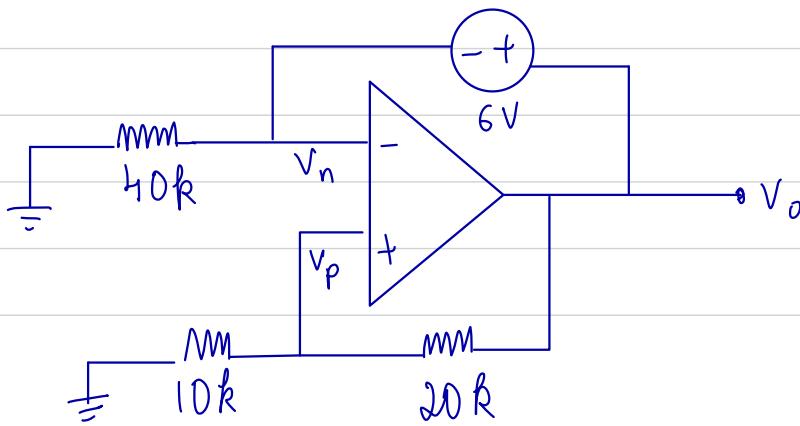

Find V_p , V_n & V_o

Ans -ve feedback is dominant

$$\Rightarrow V_p = V_n$$

$$\frac{V_o - V_p}{20k} = \frac{V_p}{10k}$$

$$\Rightarrow V_0 - V_p = 2V_p$$

$$V_0 = 3V_p$$

$$V_n + 6 = V_0$$


$$\Rightarrow V_p + 6 = 3V_p$$

$$\therefore V_p = 3V_{||}$$

$$\therefore V_n = 3V$$

$$\therefore V_0 = qV_{\parallel}$$

Q9) Find the gain

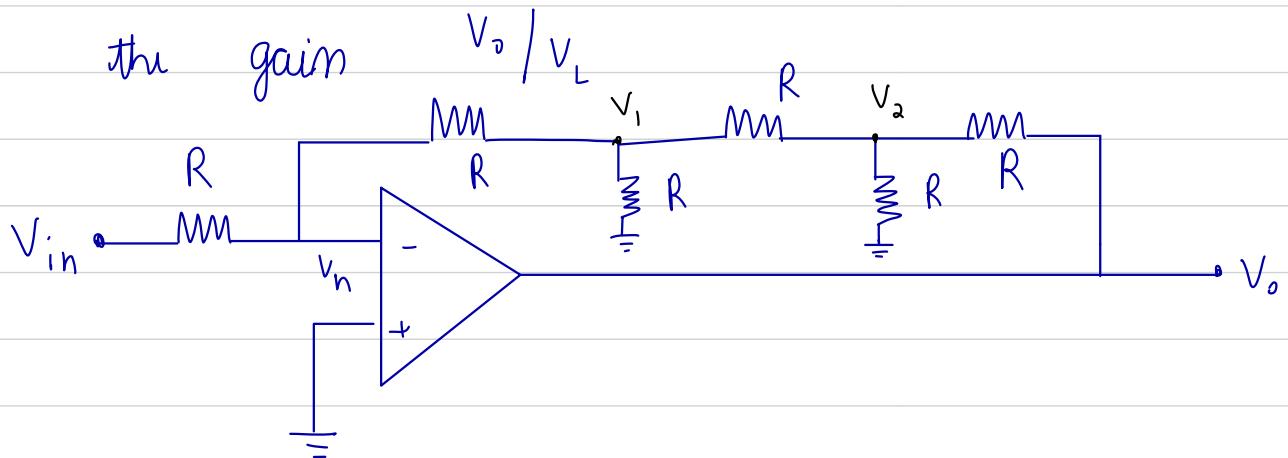

$$V_p = V_n = 0V$$

$$\frac{V_{in} - 0}{R} = \frac{0 - V_1}{R} \quad \therefore V_1 = -V_{in}$$

$$\frac{0 - V_1}{R} = \frac{V_1}{R} + \frac{V_1 - V_2}{R}$$


$$\frac{-V_1}{R} = \frac{2V_1 - V_2}{R} \Rightarrow \therefore V_2 = 3V_1$$

$$\frac{V_1 - V_2}{R} + \frac{V_2}{R} = \frac{V_2 - V_0}{R} \Rightarrow \therefore V_1 = 3V_2 - V_0$$

$$\Rightarrow V_o = 3V_2 - V_1 = 9V_1 - V_1 = 8V_1 = -8V_{in}$$

$$\therefore \frac{V_o}{V_{in}} = -8$$

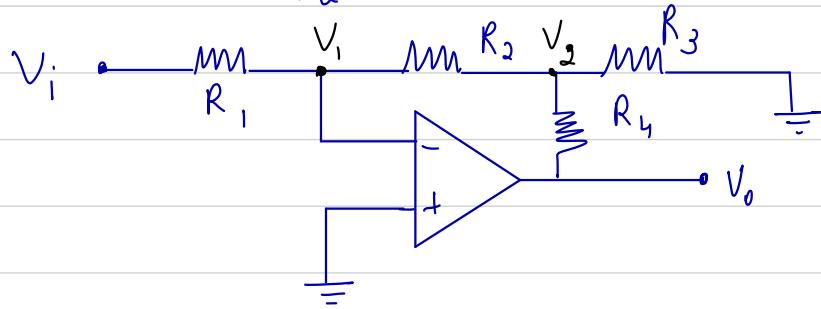Q10) Show that the circuit has $A = \frac{V_o}{V_i} = -\frac{k R_2}{R_1}$ with $k = 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3}$



Ans $V_1 = 0$

$$-\frac{V_2}{R_2} = \frac{V_2}{R_3} + \frac{V_2 - V_o}{R_4}$$

$$\frac{V_o}{R_4} = V_2 \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right]$$


$$\frac{V_i}{R_1} = -\frac{V_2}{R_2}$$

$$V_2 = -\frac{R_2}{R_1} V_i$$

$$V_o = -\frac{R_2}{R_1} V_i \left[1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right]$$

$$\therefore k = \left[1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right]$$

Q11)

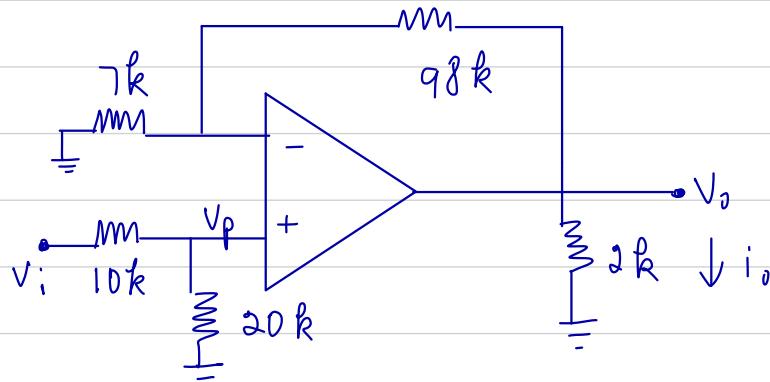

Find V_o , ϵ , i_o
if $V_i = 0.5 \sin \omega t$

Ans

$$V_o = \left(1 + \frac{98}{7} \right) V_p$$

$$V_p = \frac{20}{30} V_i = \frac{2}{3} \times 0.5 \sin \omega t$$


$$= 15 V_p$$

$$= 15 \times \frac{2}{3} \times 0.5 \sin \omega t$$

$$\therefore V_o = 5 \sin \omega t$$


$$i_o = \frac{V_o}{2k\Omega} = \frac{5 \sin \omega t}{2 \times 10^3} = 2.5 \sin \omega t \text{ mA}$$

Q12) Find V_o

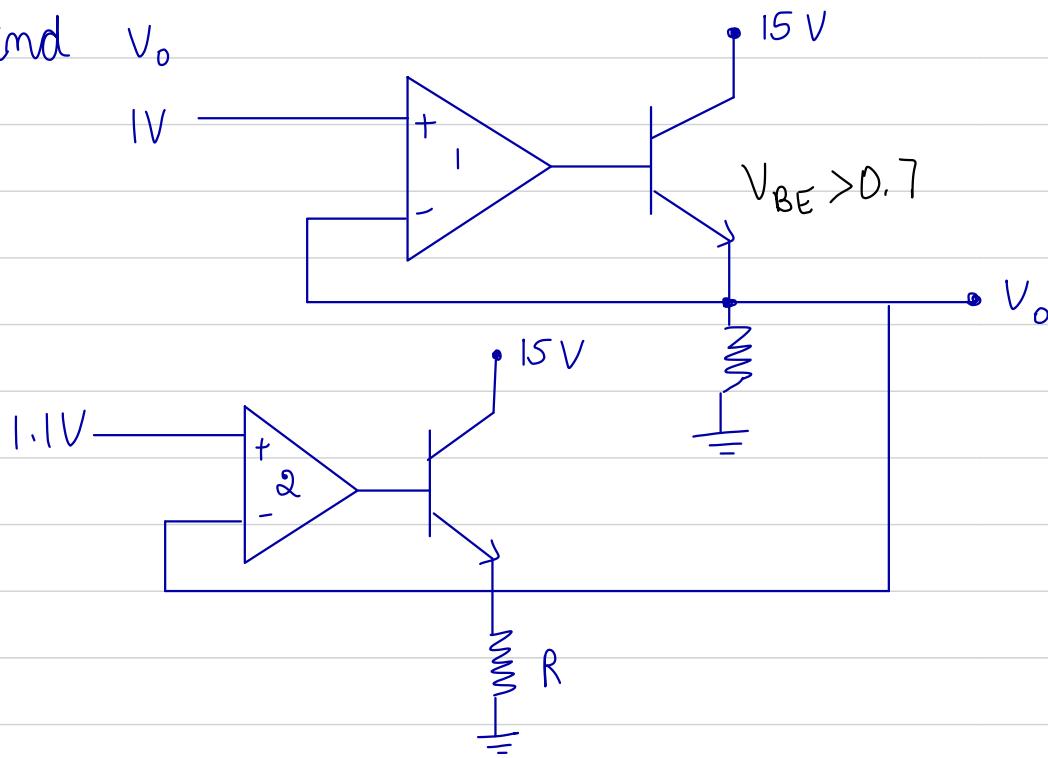


Ans Here both are voltage buffer:
 $\therefore V_o = 1.1 \text{ V}$

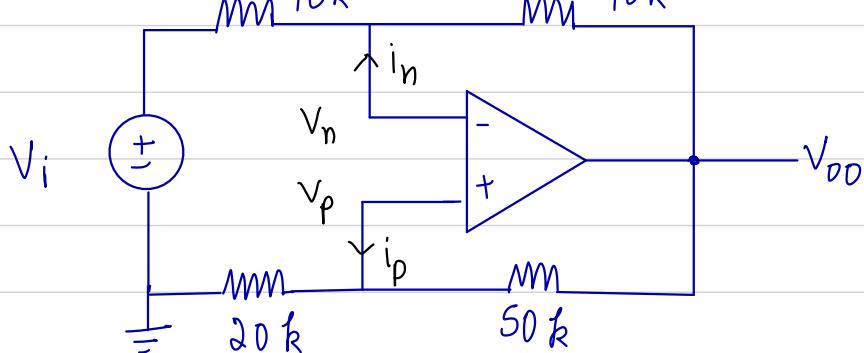Q13) Consider the following circuit, what is the min of max o/p offset voltage flowing out of the opamps if the bias i/p pins. $I_B = 100 \text{ nA}$ $I_{io} = 20 \text{ nA}$.



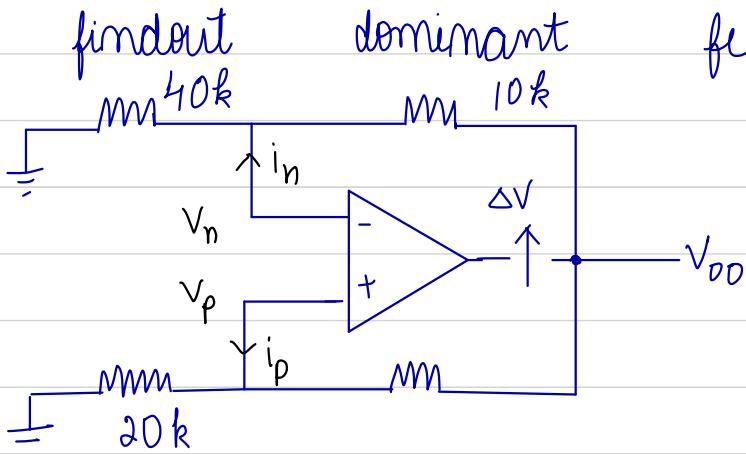A_m To find out dominant feedback response:



$$\frac{40}{50} \Delta V_o = V_n$$

$$\frac{20}{70} \Delta V_o = V_p$$

$\because V_n > V_p$, negative feedback is dominant.

$$I_B = \frac{i_n + i_p}{2}, \quad I_{io} = |i_n - i_p|$$

$$\frac{V_{OO} - V_n}{10k} + i_n = \frac{V_n}{40k}$$

$$\frac{V_{OO} - V_p}{50k} + i_p = \frac{V_p}{20k}$$

Also $V_n = V_p$

$$\frac{V_{OO}}{10k} + i_n = V_p \left[\frac{5}{40k} \right]$$

$$\frac{V_{OO}}{50k} + i_p = V_p \left[\frac{7}{100k} \right]$$

$$\Rightarrow \frac{V_{OO}}{10k} + i_n = \left(\frac{V_{OO}}{50k} + i_p \right) \cdot \frac{100k \times 5}{7 \times 40k}$$

$$\frac{V_{OO}}{10k} + i_n = \frac{25}{14} \left(\frac{V_{OO}}{50k} + i_p \right)$$

$$\therefore \left(5 - \frac{25}{14}\right) \frac{V_{DD}}{50k} = \frac{25}{14} i_p - i_n$$

$$\therefore \frac{9}{140k} V_{DD} = \frac{25}{14} i_p - i_n$$

$$\therefore V_{DD} = \frac{250k}{9} i_p - \frac{140k}{9} i_n$$

$$V_{DD} = 27.77k i_p - 15.55k i_n$$

When, $i_p = 90 \text{ nA}$

$i_n = 110 \text{ nA}$

$$\therefore (V_{DD})_{\min} = 27.77k \times 90 \text{ nA} - 15.55k \times 110 \text{ nA}$$

$$= 788.8 \mu\text{V} = 0.788 \text{ mV}_\parallel$$

When $i_p = 110 \text{ nA}$


$i_n = 90 \text{ nA}$

$$\therefore (V_{DD})_{\max} = 27.77k \times 110 \text{ nA} - 15.55k \times 90 \text{ nA}$$

$$= 1655.2 \mu\text{V} = 1.6552 \text{ mV}_\parallel$$

(14) An Omega band control system for room heater with following specification. When room temperature goes below 16°C , the heater is turned on and it is turned off if temperature is above 24°C . Assume that a thermistor band sensor gives voltage output proportional to room temperature. Suggest a scheme to control heater with a circuit diagram.

Ans

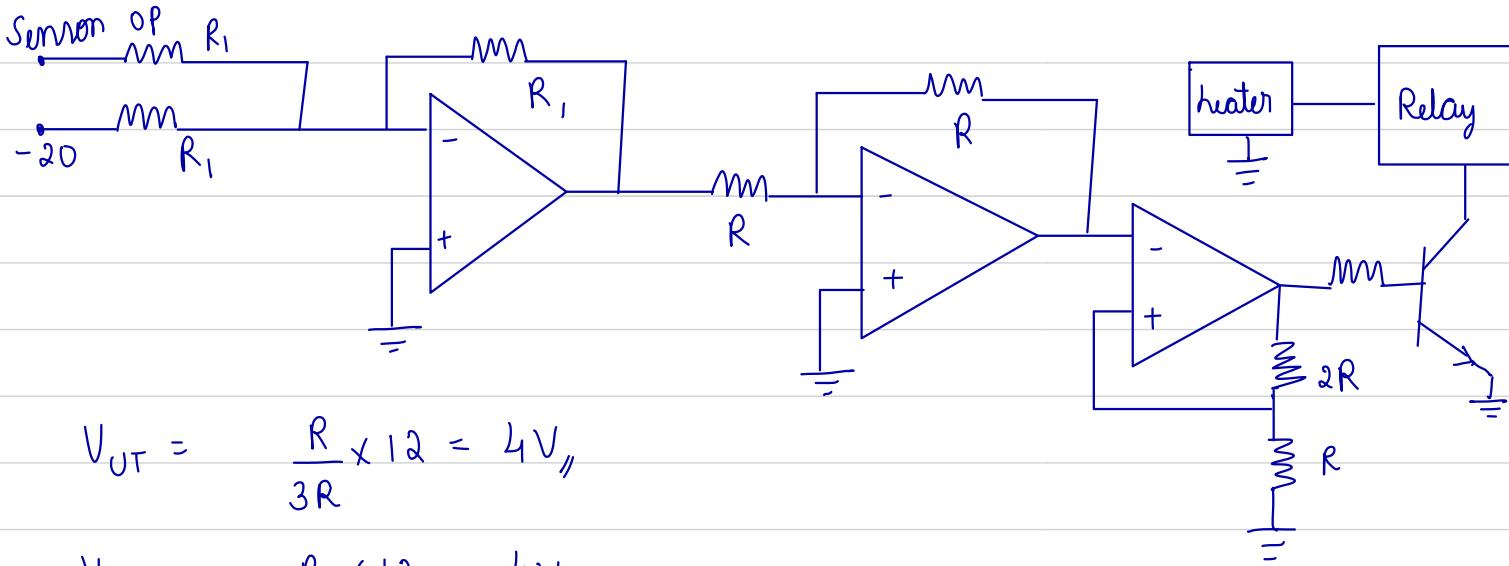


$$V_{UT} = \frac{R}{3R} \times 12 = 4V_{\parallel}$$

$$V_{LT} = -\frac{R}{3R} \times 12 = -4V_{\parallel}$$

S_0 at 16 V $\rightarrow V_{out} = V_{sat}$
 at 24 V $\rightarrow V_{out} = -V_{sat}$


Relay internal circuit

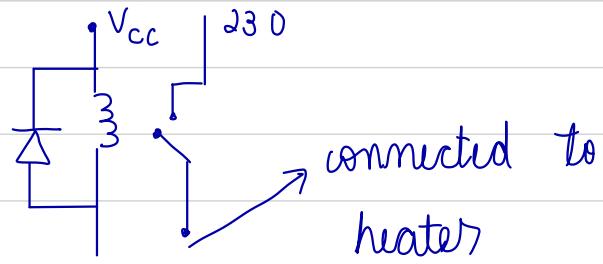

Q15) A 6V battery with charge indicator has to be designed with following specifications:
 Battery voltage
 Below 3V No LED should glow
 3-4V 1 LED should glow
 4-5V 2 LED should glow
 Above 5V 3 LED should glow
 You are provided with 5, 7, 9V zener diodes, opamps, LEDs (which will drop 1V when they conduct), resistors.

Using these components design a battery indicator circuit. Design the circuit diagram and find appropriate values.

Ans

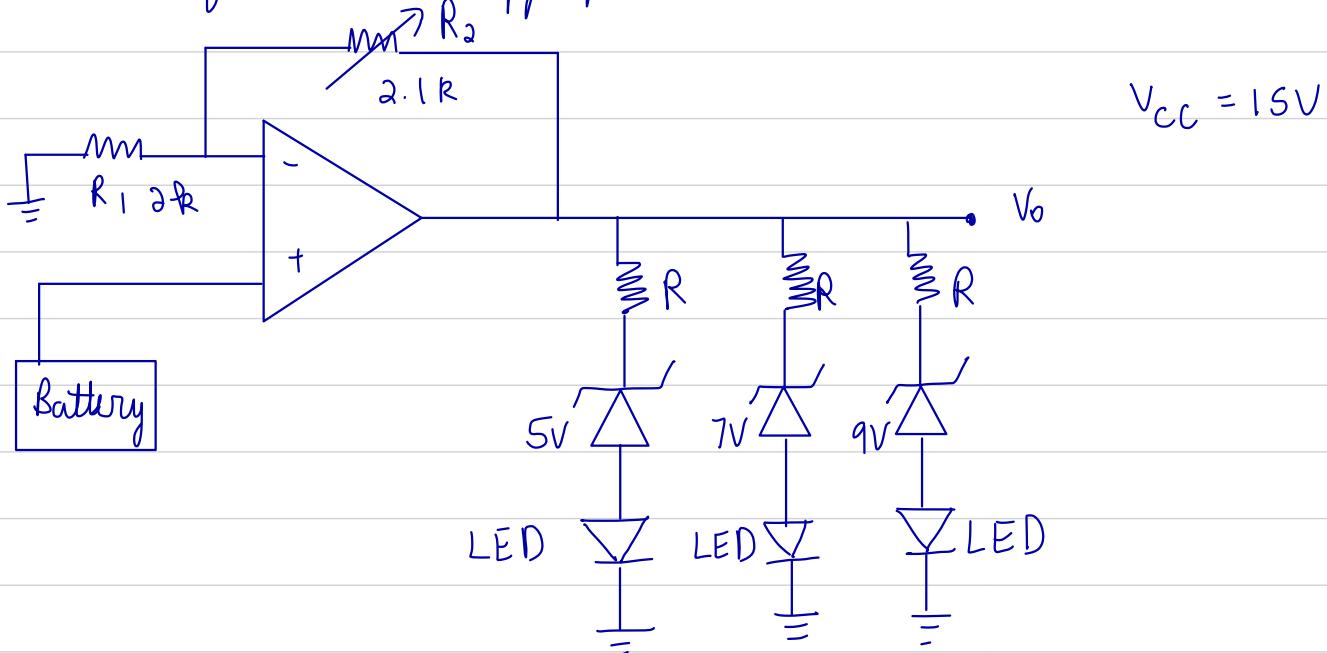

R_2 should be slightly greater than R_1 .

$$R_T = R \parallel R \parallel R \parallel (R_1 + R_2)$$

$$R = 3.3\text{k} \quad \text{then}$$

$$R_T \approx 0.8\text{k}$$

$$\therefore \frac{12}{0.8\text{k}} = 15\text{ mA} < 25\text{ mA}$$

Q16) A flasher has to produce 12 flashes of light per minute, the duration of each flash is 1 sec. Design a driver circuit. Flasher bulb has to be driven by a npn transistor.

Ans

$$T = \frac{6.0}{12} = 5\text{s}$$


$$T_{on} = 1\text{s}$$

$$T_{off} = 4\text{s}$$

Ansible

multivibrator

should be used,

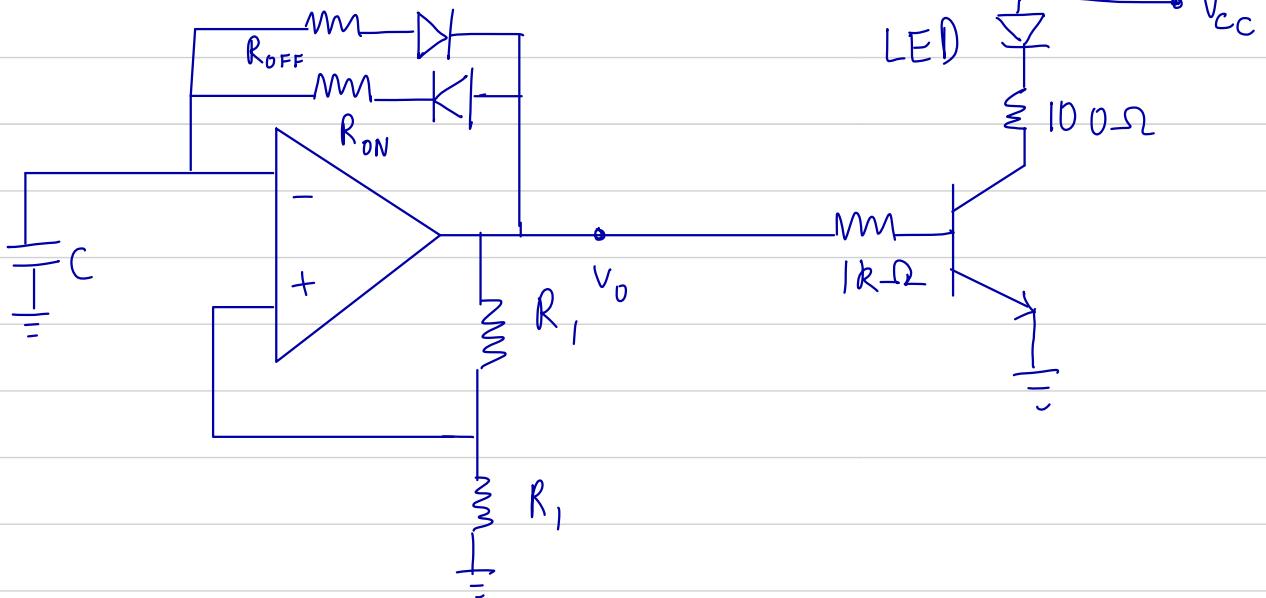

$$\text{Let } C = 0.01 \text{ mF}$$


$$1.1 \quad R_{on} C = 1\text{s}$$

$$R_{on} = 90.90 \text{ k}\Omega$$


$$1.1 \quad R_{off} C = 4\text{s}$$

$$R_{off} = 363.64 \text{ k}\Omega$$

Q17) Generate the following waveform

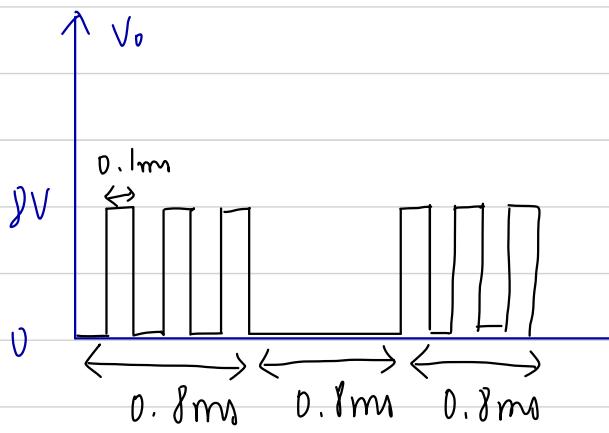




Ans

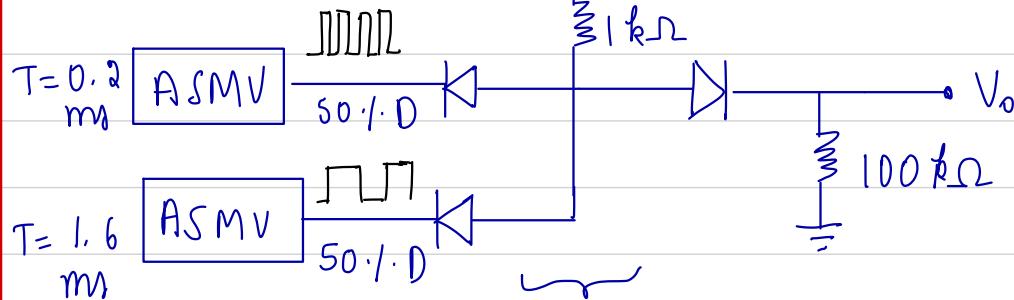



Diode AND

NOTE: ASMV + Integrator + Triangular wave generator are included along with 10 experiments for AE lab exam.

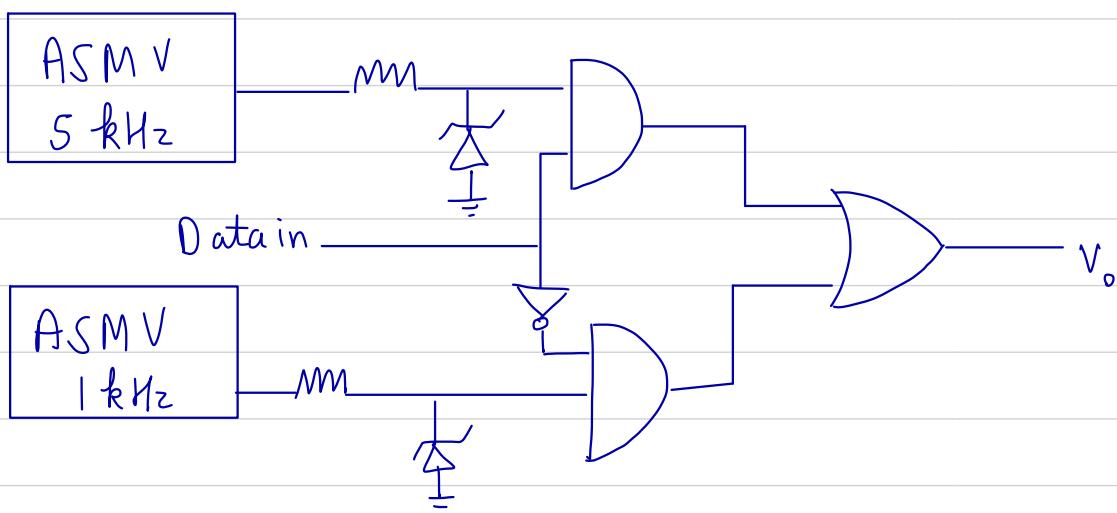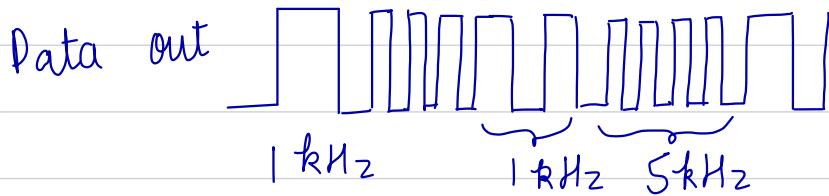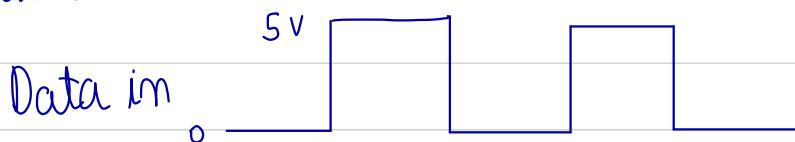Q18) In digital communication system, the logic symbols & logic 0 are transmitted as FSK frequencies of 5 kHz & 1 kHz respectively. Design a circuit for such a FSK (frequency shift keying), assume opamps, digital ICs & zener diodes are available.



NOTE:

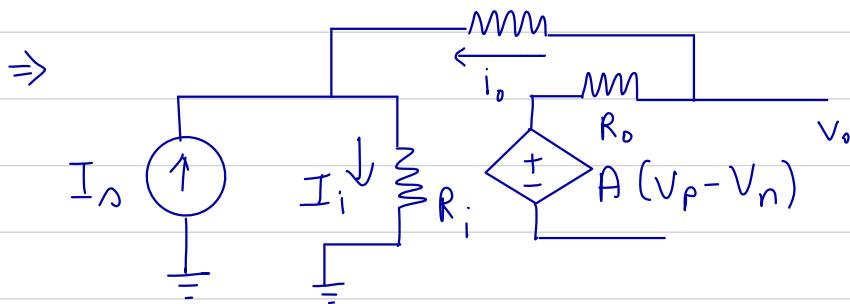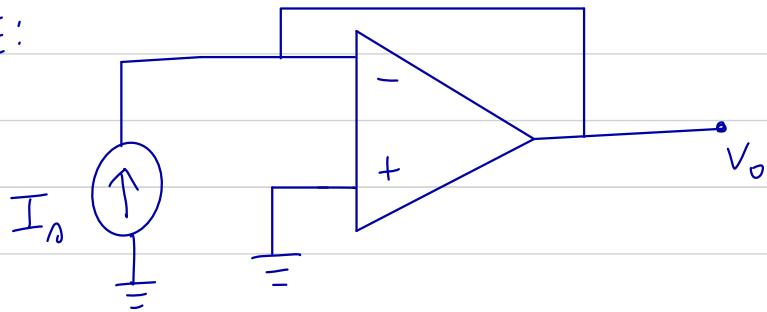


$$I_s + i_o = I_i$$

$$I_s = -I_i$$

$$Z_{if} = \frac{V_n}{I_s} = 0$$


A should be as large as possible.

Integrator

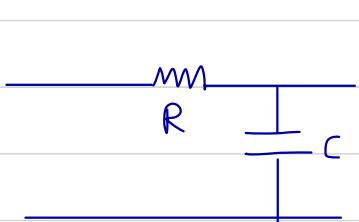

constant input voltage integrator
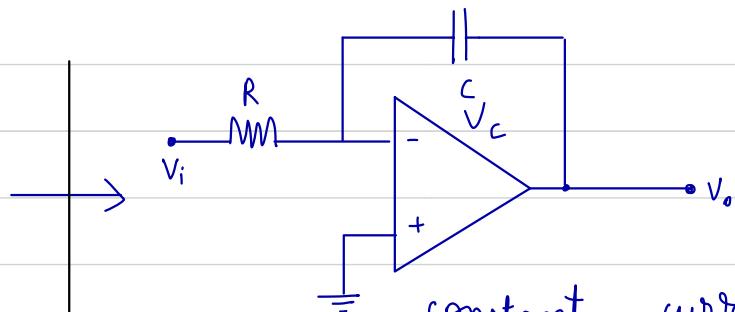
$$i : \frac{V_i - 0}{R} \rightarrow \frac{V_i - V_c}{R}$$



constant current integrator


$$C \Delta V = I_c t$$

$$V_{it} = V_f + (V_{im} - V_f) e^{-t/RC}$$

$$I_c = C \frac{dV}{dt}$$

ΔV = peak to peak voltage

For opamp integrator:

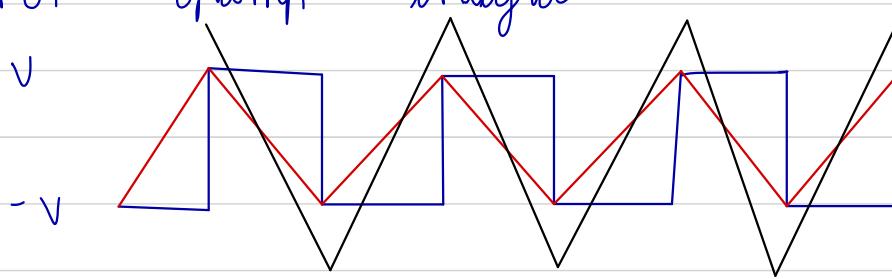

$$V_{in} \\ RC = \tau/2$$

$$V_{opp} > V_{inpp}$$



$$V_{in} \\ RC > T/2$$

$$V_c = \frac{1}{C} \int i_c dt$$

$$V_c = \frac{1}{RC} \int V_i dt$$

$$V_o = V_p - V_c = -V_c$$

$$\therefore V_o = -\frac{1}{RC} \int V_i dt$$

$$\frac{V_o}{V_i} = -\frac{1}{RC_n}$$


$$\Rightarrow H(s) = -\frac{1}{RC_n}$$

$$H(j\omega) = -\frac{1}{RC_j\omega}$$


$$\therefore |H| = \frac{1}{RC\omega}$$

$$\boxed{|H(j\omega)| = 90^\circ //}$$


Pole at $s=0$

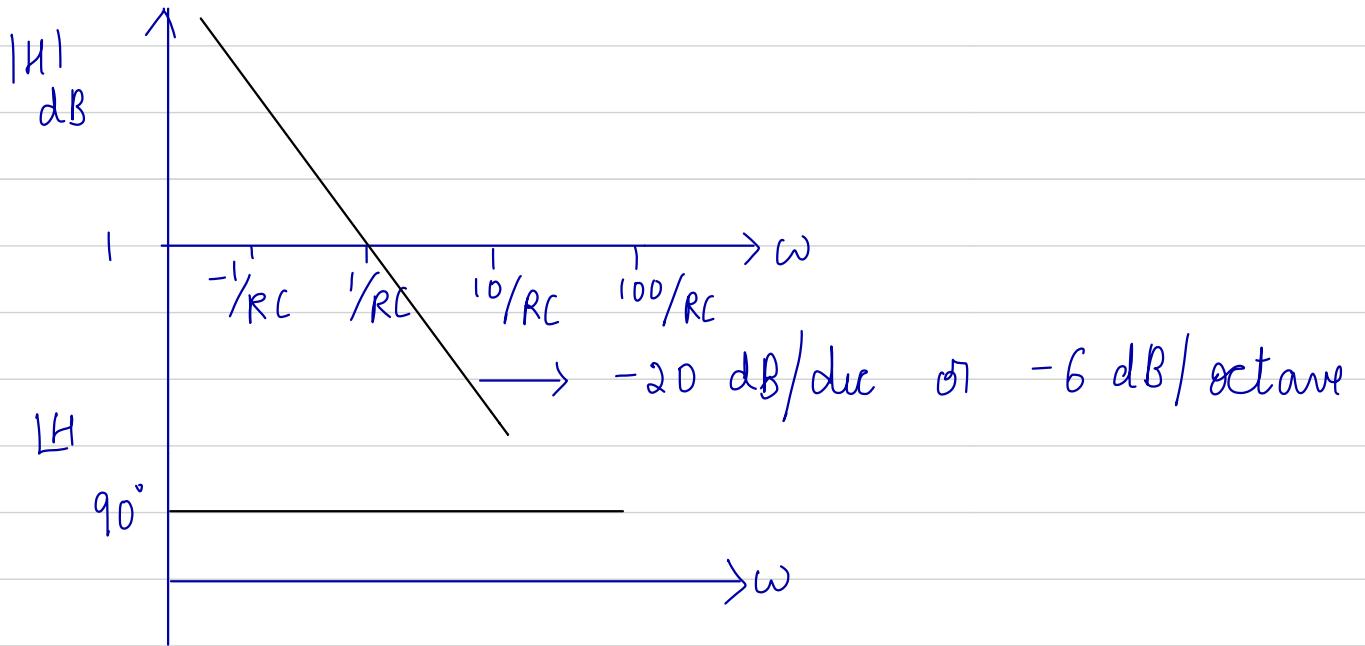

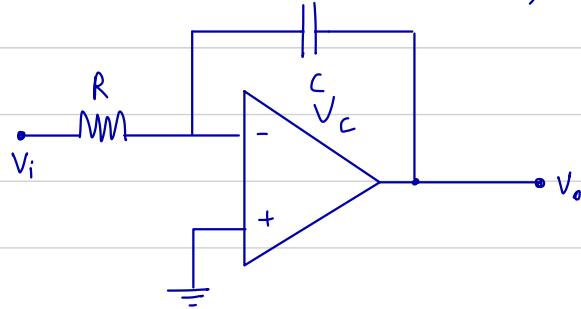Q19) Plot V_o if $R = 1 \text{ k}\Omega$, $C = 10 \mu\text{F}$ & $V_i = 2u(t)$ in



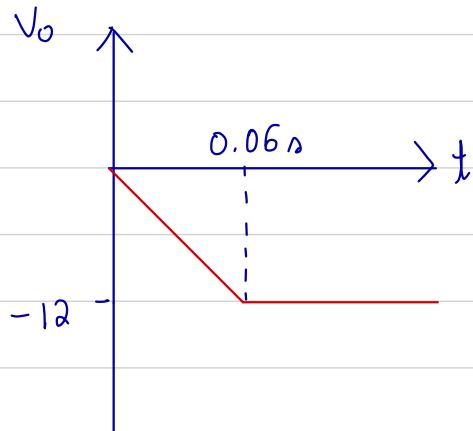
$$\text{Ans} \quad V_o = \frac{-1}{RC} \int v_i dt = \frac{-1}{10^4 \times 10^{-6}} \int 2u(t) dt = -200t$$



$$-12 = -200t$$

$$t = \frac{6}{100} = 0.06 \text{ s}$$

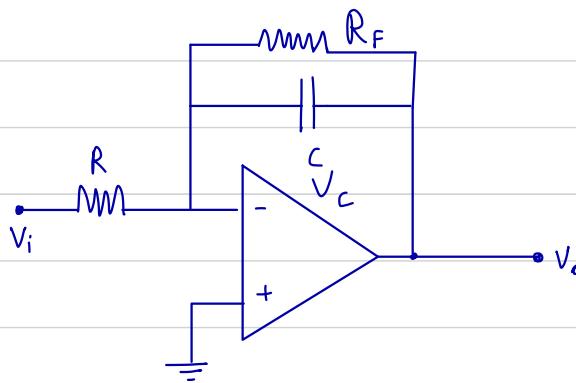

← Practical integrator circuit.

A large resistance of R_F is connected parallel to capacitor so that V_o does not get saturated when capacitor acts as an open circuit.

For DC, $Z_f \approx R_f$

$Z_F \approx \frac{1}{\omega C}$, for AC

$$\frac{V_o}{V_i} = \frac{R_F \parallel \frac{1}{\omega C}}{R}$$



$$H(s) = \frac{-\left(R_F/R\right)}{1 + \frac{s}{\omega_0}}$$

where $\omega_0 = \frac{1}{R_F C}$

$$H(s) = \frac{-\left(R_F/R\right)}{1 + R_F C s}$$

Pole at $s = -\frac{1}{R_F C}$
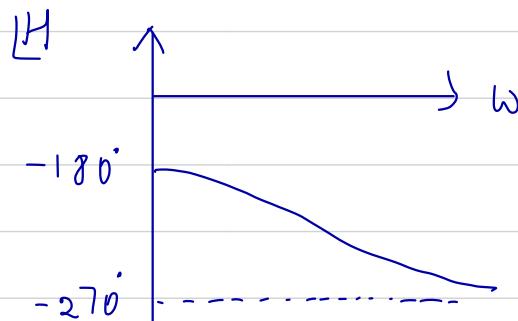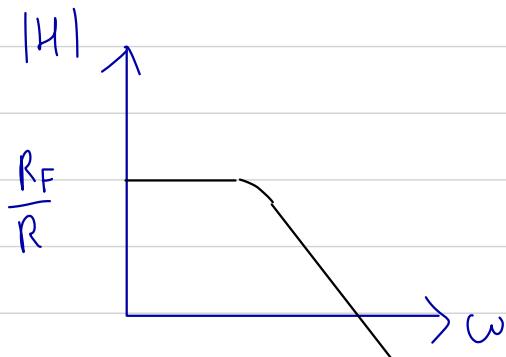
$$\therefore \text{cutoff frequency} = \frac{1}{R_F C}$$



$$|H| = \frac{R_F / R}{\sqrt{1 + \omega^2 C^2 R_F}}$$

$$\angle H = \pm 180^\circ - \tan^{-1} \omega C R_F$$

Q20) Design a voltage integrator for a sinusoidal signal
 $v_i(t) = 2 \sin 4000\pi t$ with gain equal to unity.

a) Design a practical integrator with $f_{-3dB} = \frac{f_{in}}{15}$

b) If a square wave input of 4V p-p is applied with $f_{in} = 2\text{ kHz}$. Plot v_o w.r.t v_i

c) If a square wave input of 4V p-p is applied with $f_{in} = 130\text{ Hz}$. Plot v_o w.r.t v_i

Ans

$$v_o = -\frac{1}{RC} \int 2 \sin 4000\pi t dt$$

$$= \frac{1}{RC} \frac{2 \cos 4000\pi t}{4000\pi}$$

$$\text{Gain} = \text{unity} \Rightarrow v_o = 2 \cos 4000\pi t$$

$$\Rightarrow RC = \frac{1}{4000\pi}$$


$$2t \quad C = 0.01 \mu F$$

$$\text{then } R = 7.96 k\Omega \approx 8 k\Omega$$

$$\text{as } f_0 = \frac{f_{in}}{15} = \frac{2k}{15} = 133.33 \text{ Hz}$$

$$\frac{1}{R_F C} = \omega_0 = 2\pi \times 133.33$$

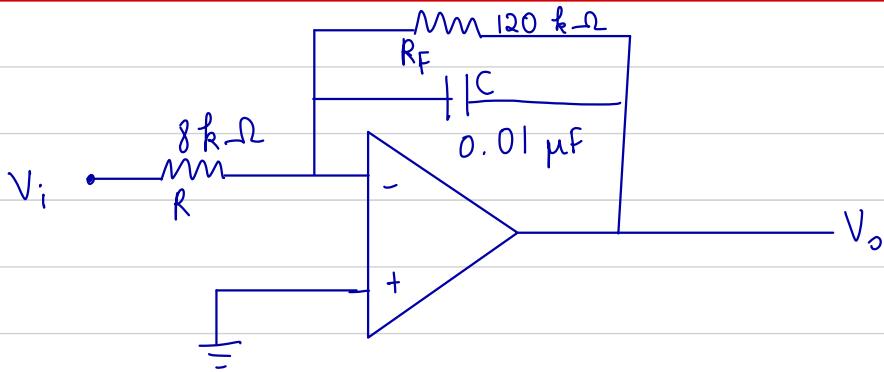
$$\therefore R_F = \frac{119.36 k\Omega}{120} \approx 120 k\Omega$$



b> $C \Delta V = I \Delta t$

$$\Delta V = \frac{2}{RC} \times \frac{I}{2}$$

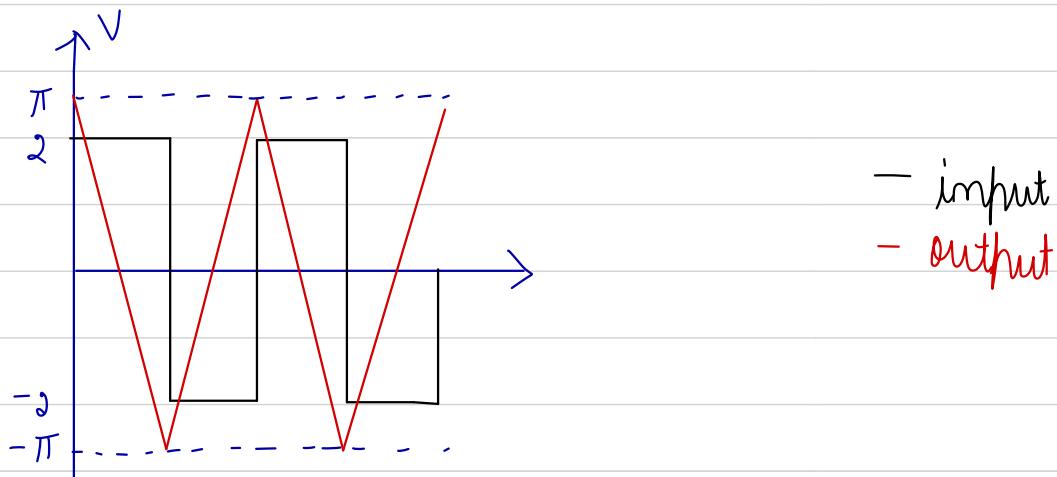
$$\Delta V = 4000\pi \times \frac{1}{2k} = 2\pi/$$




c> $C \Delta V = I \Delta T$

$$\Delta V = \frac{2}{RC} \times \frac{I}{2}$$
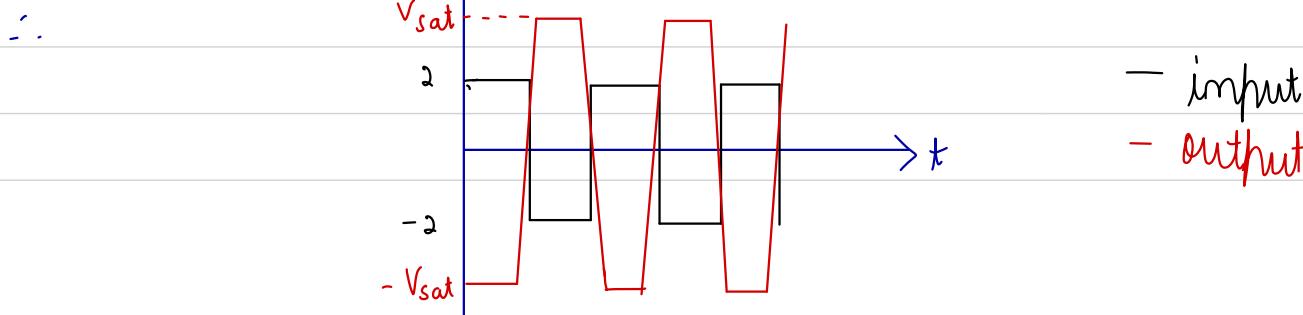
$$\Delta V = \frac{4000\pi}{130} = 96.6 \text{ V} > V_{sat}$$



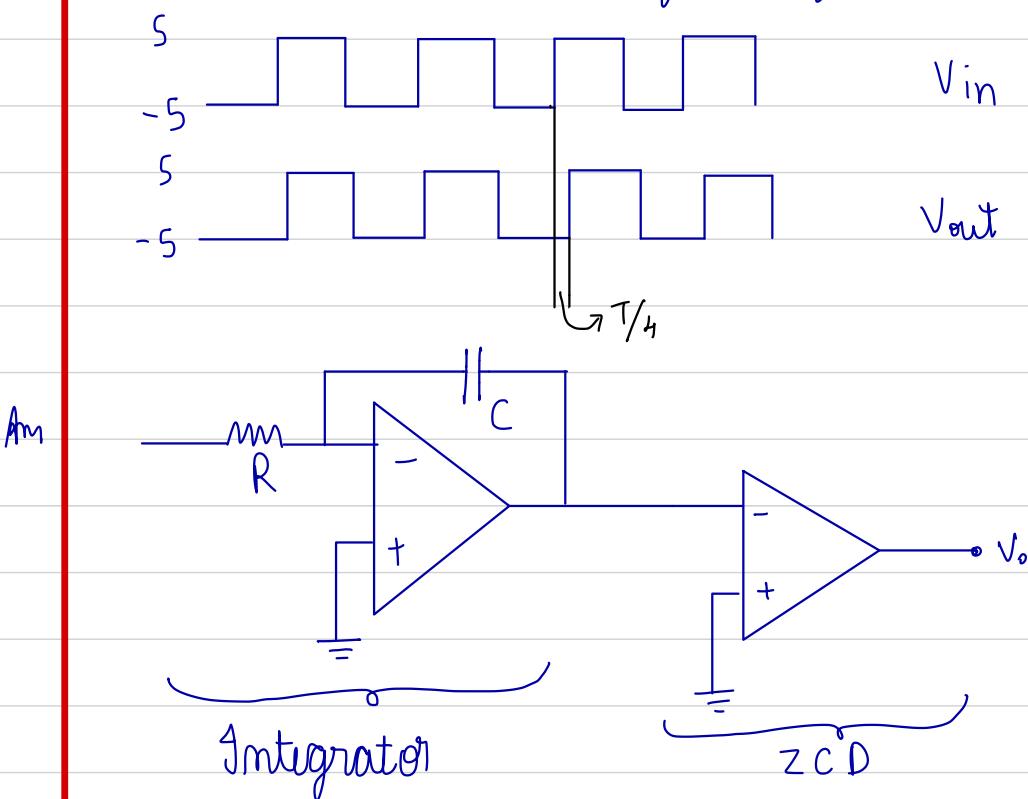Q21) Design an opamp based circuit for the following waveform. The output must be delayed exactly by $T/4$ seconds from the input. An frequency of input varies, so does the output. But duty cycle remains the same.




$$C \Delta V = I \Delta t$$

$$C \times 10 = \frac{5}{R} \times \frac{T}{2}$$


$$\Rightarrow T = 4RC$$

i.e


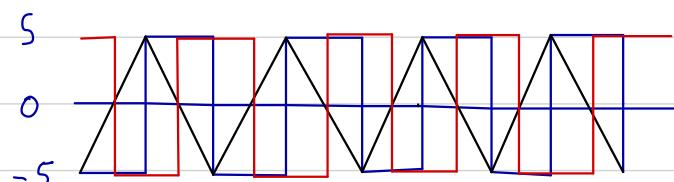


— input
— integrator output
— ZCD output

Triangular waveform generator

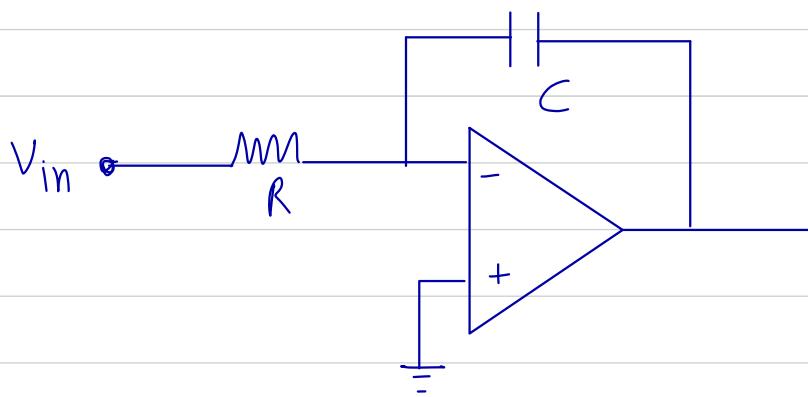

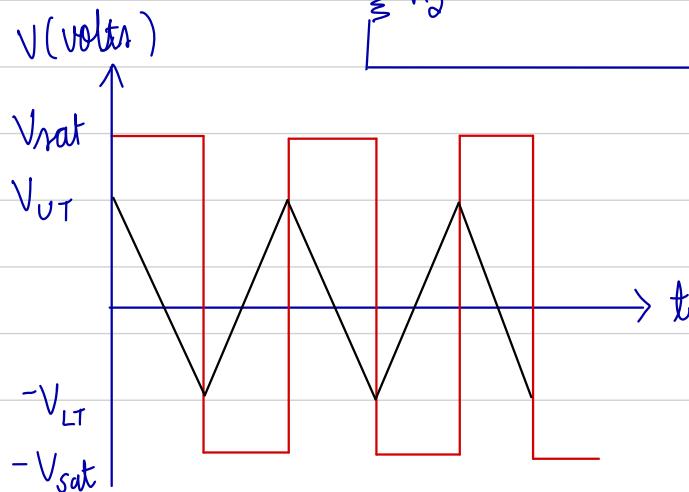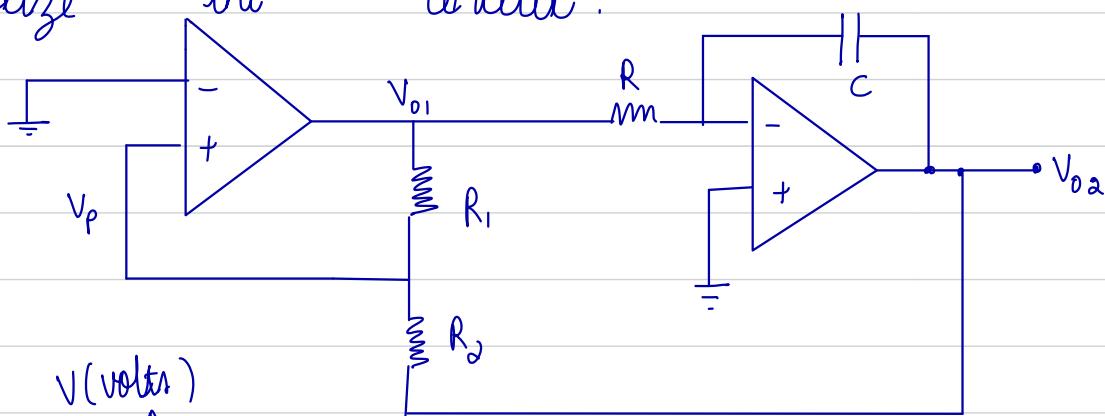- Integrator also generates triangular waveform.
- But a small DC in input is enough to make output go to saturation.
- So we have to increase input level if it is going to $-V_{sat}$ & decrease level if it is going to $+V_{sat}$.
- Therefore Schmitt trigger is connected to stabilize the circuit.



— output (V_{o2})
— input (V_{o1})

$$V_{VT} = \frac{R_2}{R_1} V_{sat}$$

$$V_{LT} = -\frac{R_2}{R_1} V_{sat}$$


$$C \Delta V = I \Delta t$$

$$C \times \frac{2R_2}{R_1} V_{sat} = \frac{V_{sat}}{R} \times \frac{I}{2}$$


$$T = \frac{4R_2 RC}{R_1}$$

$$f = \frac{R_1}{4R_2 RC}$$


T_0 get duty cycle other than 50% :

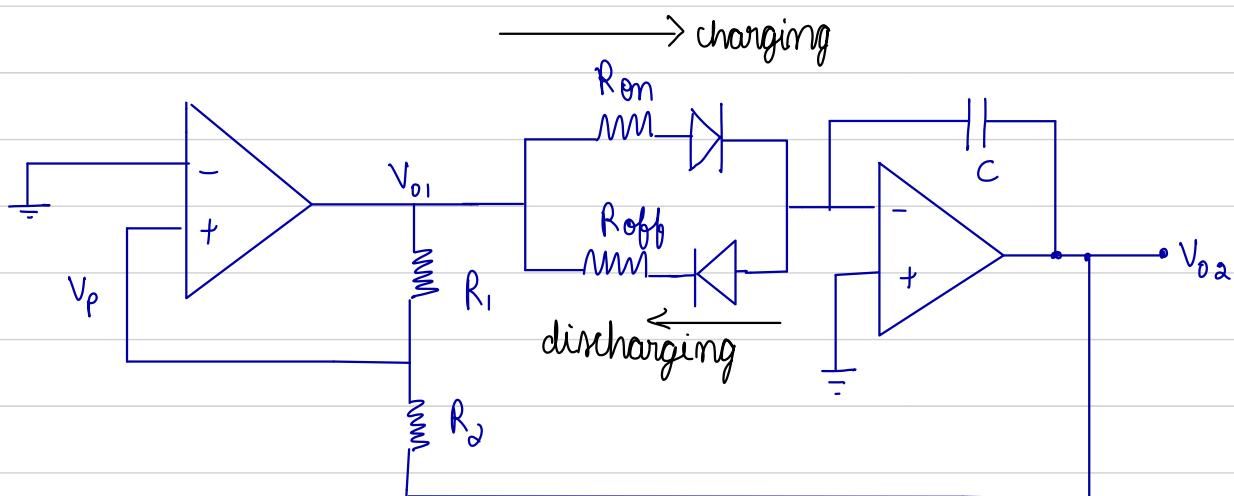

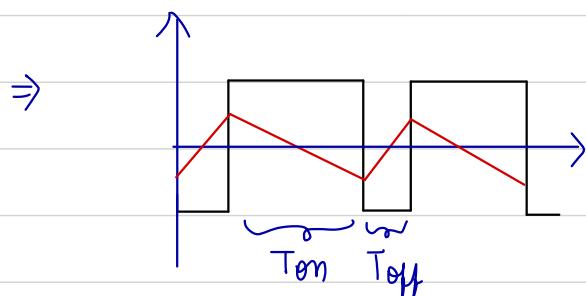
$$\text{If } R_{on} > R_{off} \\ \Rightarrow R_{on} C > R_{off} C$$


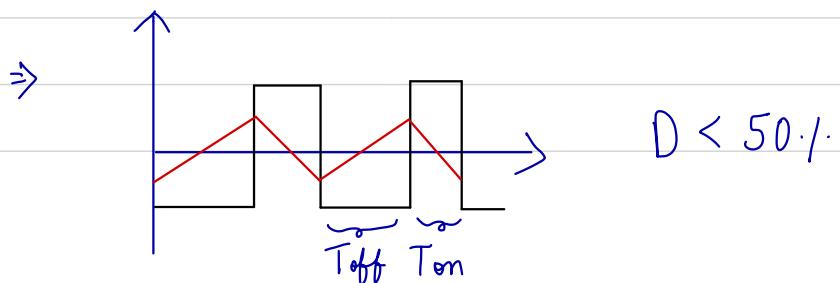
$$\text{If } R_{off} > R_{on} \\ \Rightarrow R_{off} C > R_{on} C$$



and method to vary duty cycle:

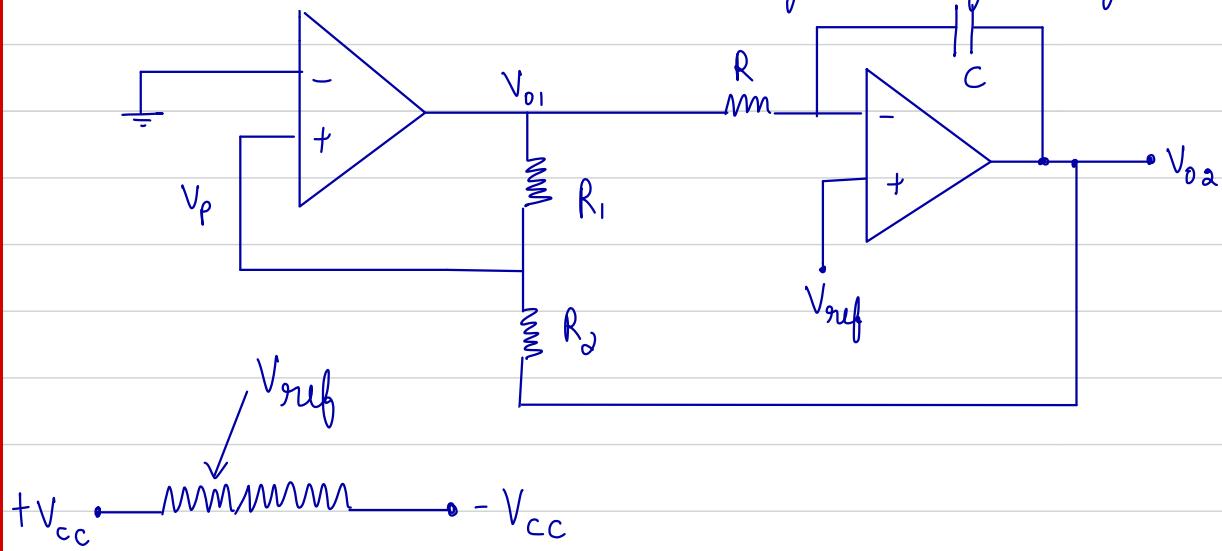

$$\text{charging current} = \frac{V_{sat} - V_{ref}}{R}$$

$$\text{discharging current} = -\frac{V_{sat} - V_{ref}}{R}$$

If $V_{ref} > 0$, then $|I_{on}| < |I_{off}| \rightarrow T_{on} > T_{off} \Rightarrow D > 50\%$

If $V_{ref} < 0$, then $|I_{on}| > |I_{off}| \rightarrow T_{off} < T_{on} \Rightarrow D < 50\%$


$$C \Delta V = I \Delta t$$

$$\Rightarrow C \times \frac{2R_2 V_{sat}}{R_1} = \frac{V_{sat} - V_{ref}}{R} \times T_{on}$$

$$T_{on} = \frac{2R_2 R C V_{sat}}{R_1 [V_{sat} - V_{ref}]} = \frac{2R_2 R C}{R_1 \left[1 - \frac{V_{ref}}{V_{sat}} \right]}$$

$$\text{Hence } T_{off} = \frac{2R_2 R C}{R_1 \left[1 + \frac{V_{ref}}{V_{sat}} \right]}$$

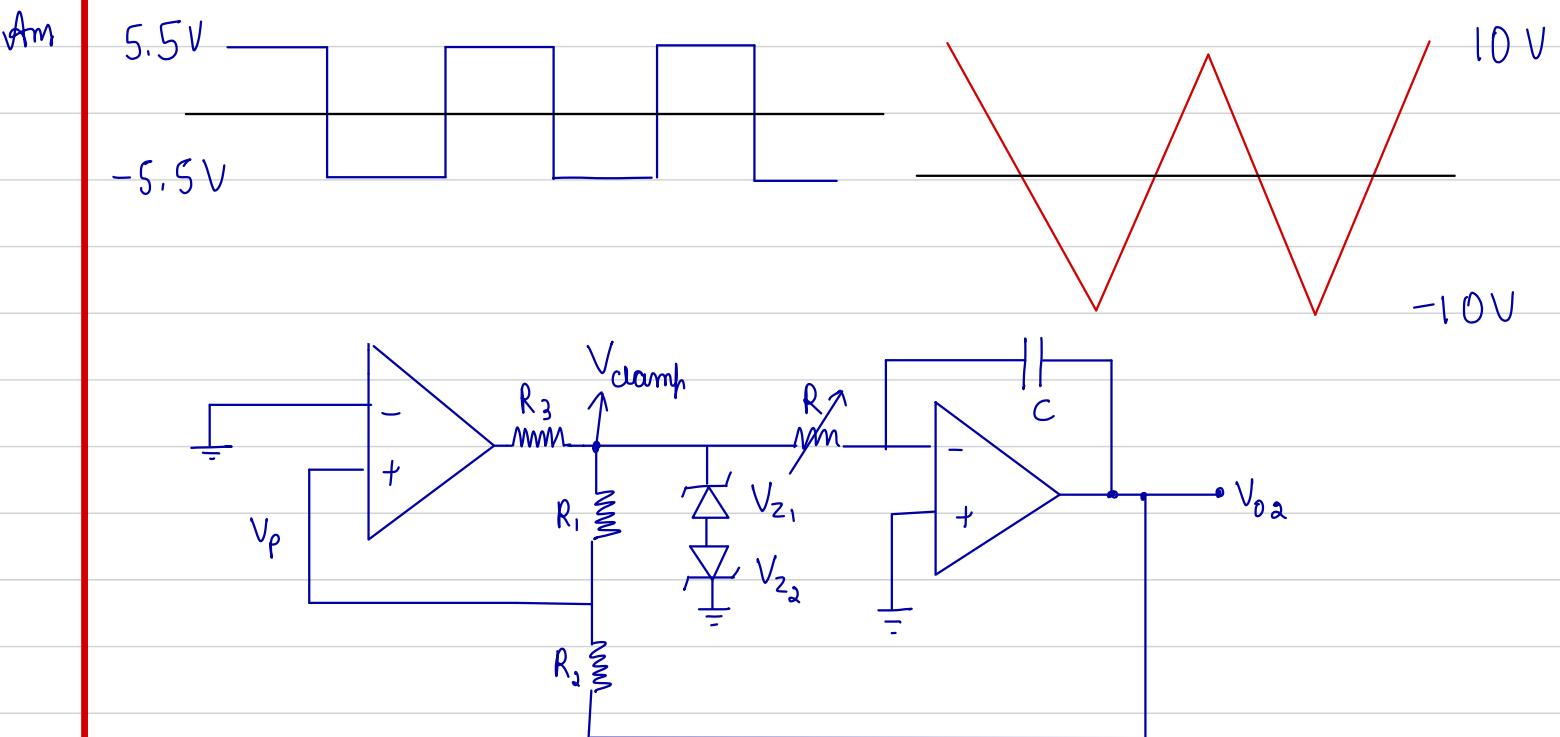Q1) Design a triangular waveform generator for approximately 5.5 V peak amplitude & a 10V peak amplitude triangular wave. Frequency is variable between 1 kHz & 2 kHz.



$$V_{\text{clamp}} = \pm 5.4V$$

$$V_{\text{tri}} = \pm 10V$$

$$V_{z_1} = V_{z_2} = 4.7V_2$$

$$\Rightarrow V_{UT} = 10V \quad V_{LT} = -10V$$

$$\Rightarrow \frac{R_2}{R_1} V_{\text{clamp}} = 10$$

$$\frac{R_2}{R_1} = \frac{10}{5.4} = 1.85 \quad \Rightarrow \quad R_2 = 1.85 R_1$$

$$\text{Let } R_2 = 10 \text{ k}\Omega \quad \Rightarrow \quad R_1 = 5.4 \text{ k}\Omega$$

$$f = \frac{R_1}{4R_2 RC}$$

$$\text{Let } 0.1 \text{ } \mu\text{F} \quad \Rightarrow \quad 1k \leq \frac{R_1}{4R_2 RC} \leq 2k$$

$$R_{\max} \text{ (at } f = 1 \text{ kHz)} = \frac{5.4 \text{ k}}{0.1 \times 10^{-6} \times 4 \times 10^3 \times 10^4}$$

$$\therefore R_{\max} = 1.35 \text{ k}\Omega_{\parallel}$$

$$R_{\min} \text{ (at } f = 2 \text{ kHz)} = 675 \Omega_{\parallel}$$

$$I_{\max} = \frac{5.4}{675} = 8 \text{ mA}$$

$$\Rightarrow \text{current through zener} = 6 \text{ mA}$$

$$\text{current through } R_1, E_1, R_2 = \frac{5.4 - (-10)}{R_1 + R_2} = 1 \text{ mA}_{\parallel}$$





$$\therefore \text{Total current} = 8 \text{ mA} + 6 \text{ mA} + 1 \text{ mA}_{\parallel}$$

$$= 15 \text{ mA}_{\parallel}$$


$$\therefore R_3 = \frac{12 - 5.4}{15 \times 10^{-3}} = 433 \Omega_{\parallel}$$

Precision
~~~~~ rectifier


Halfwave  
~~~~~ rectifier

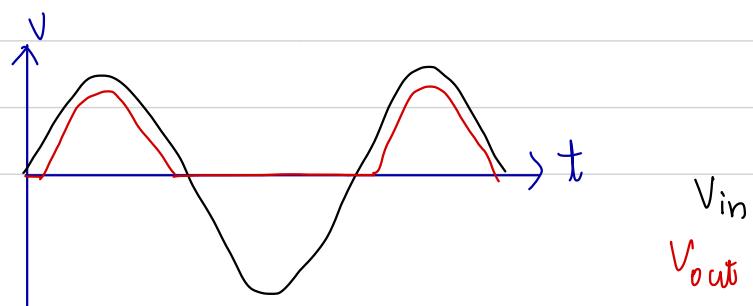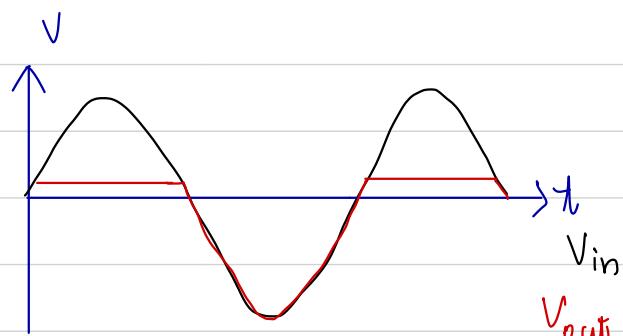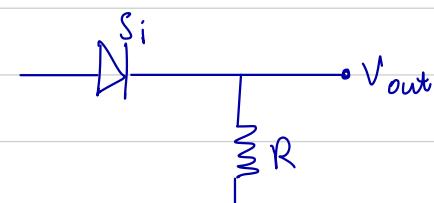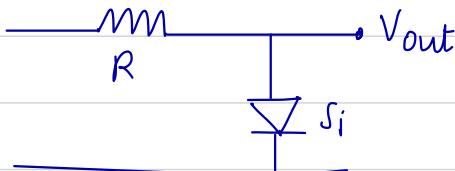

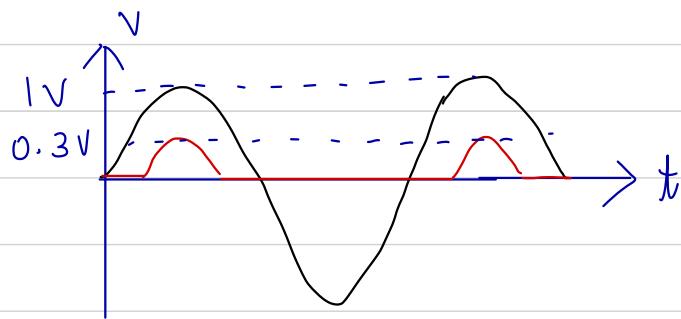
Suppose input to circuit 2 is $1V_{pp}$ sinusoid



V_o vs V_i

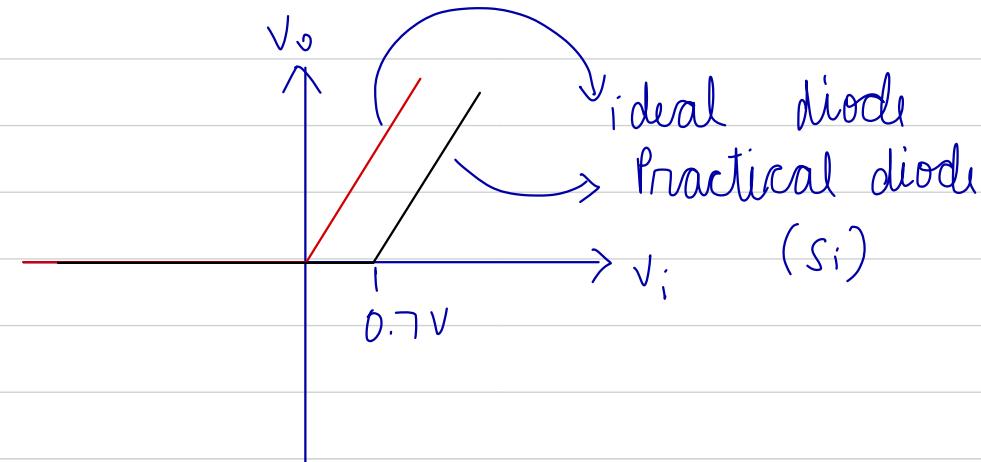


Halfwave precision rectifier

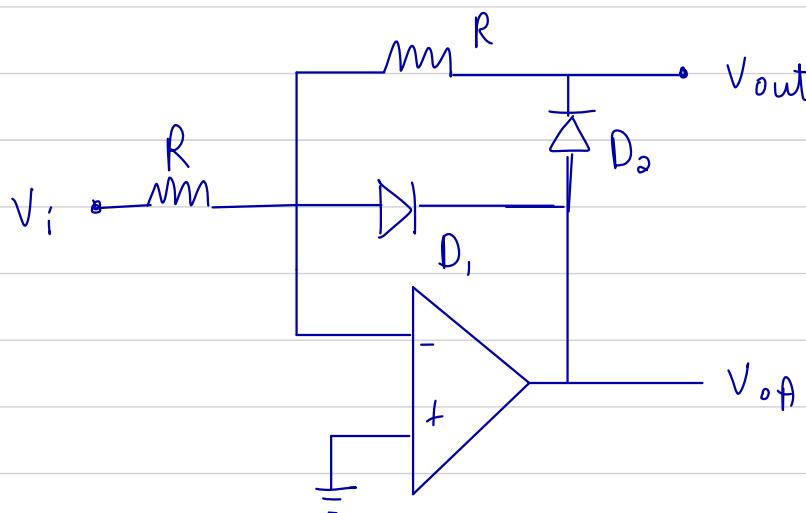


When $V_i > 0$, V_{D_2} in reverse bias

$$\Rightarrow V_{out} = 0$$

$$V_{oA} = -V_{D_1}$$

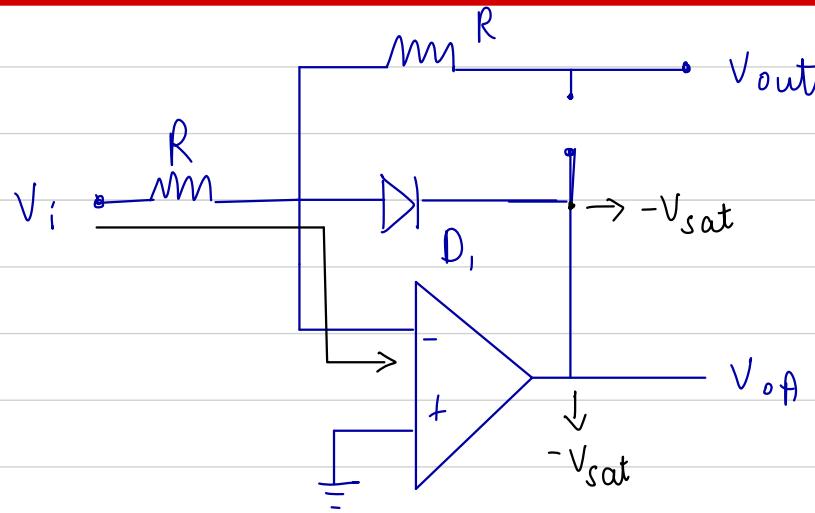

when $V_i < 0$


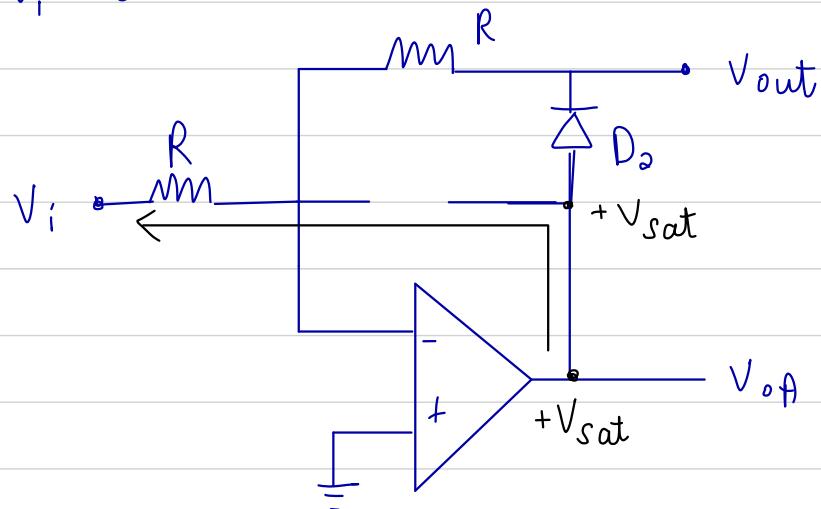



$$\Rightarrow V_{out} = -V_i$$

$$V_{oA} = V_{out} + V_{D_2}$$

$$\frac{V_{out} - 0}{R} = \frac{0 - V_i}{R}$$

$$\Rightarrow V_{out} = -V_i$$

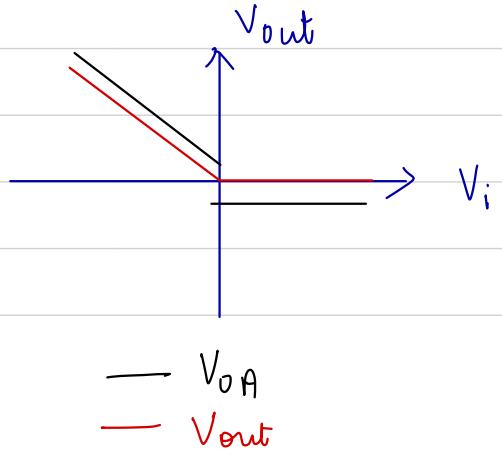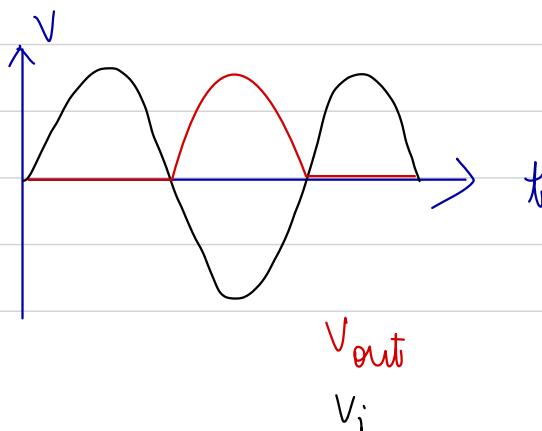

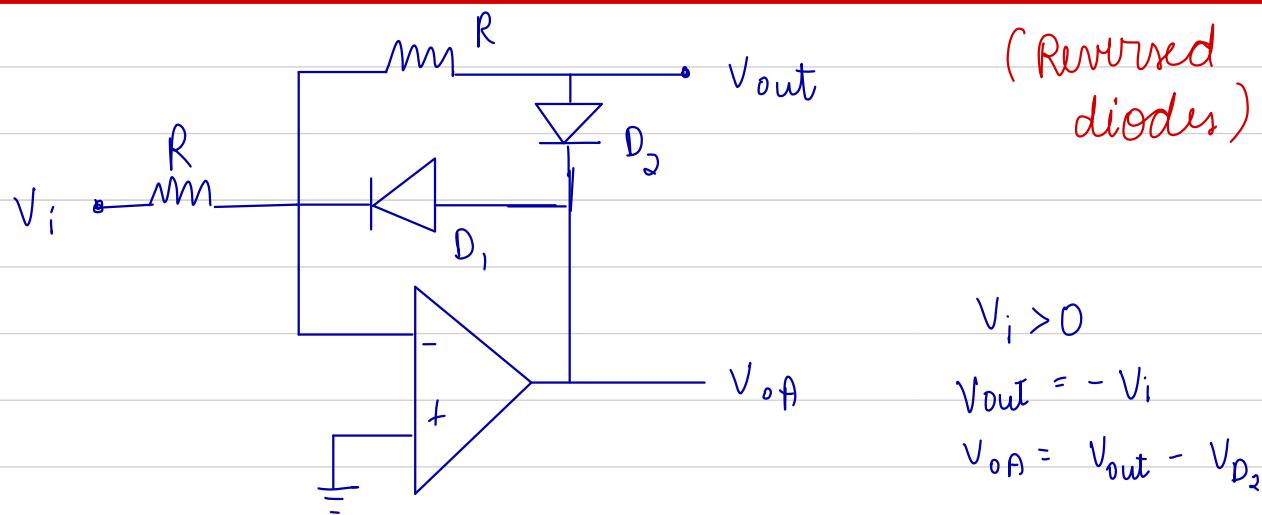



$$V_i > 0$$

$$V_{out} = -V_i$$


$$V_{OA} = V_{out} - V_{D_2}$$

$$V_i < 0$$

$$V_{out} = 0 \quad V_{OA} = V_{D_1}$$

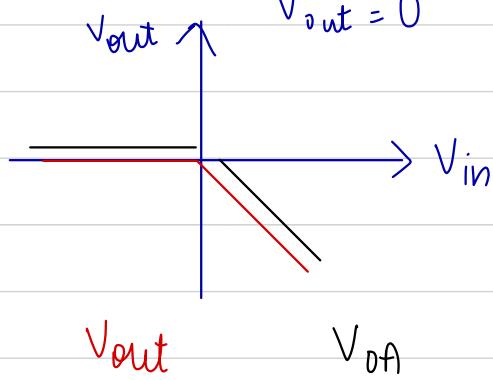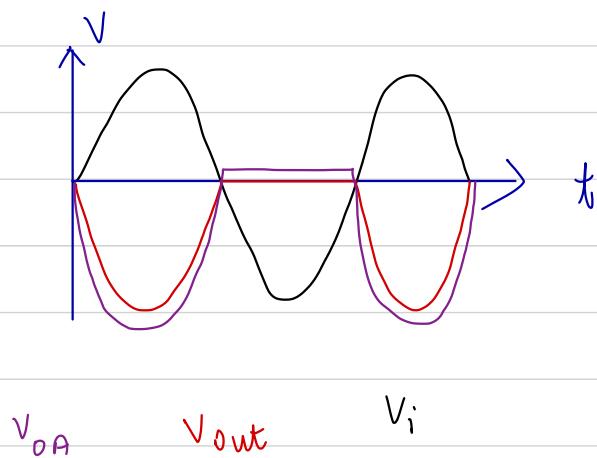

Full wave rectifier

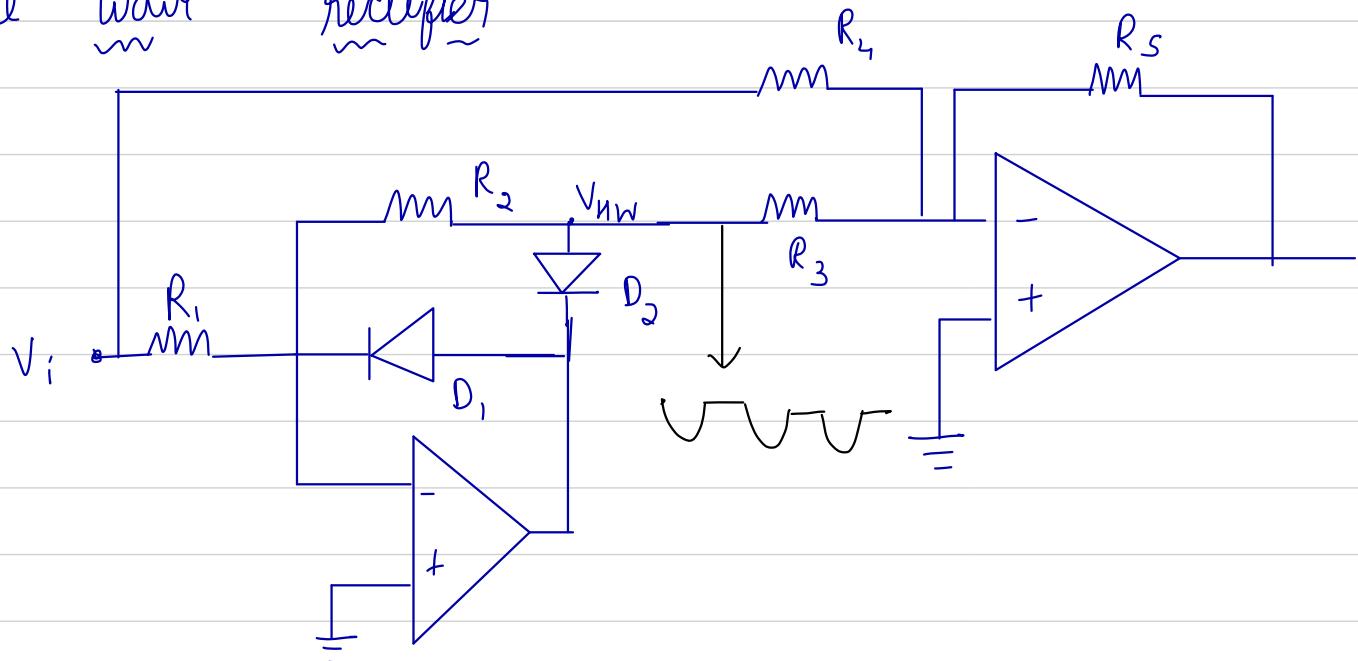

$$V_o = -\frac{R_4}{R_5} V_i - \frac{R_5}{R_3} V_{HW} \quad (\text{during +ve half cycle})$$

$$= -\frac{R_5}{R_4} V_i - \left(\frac{R_5}{R_3} \right) \left(-\frac{R_2}{R_1} \right) V_i$$

$$\Rightarrow \left[\frac{R_5 R_2}{R_3 R_1} - \frac{R_5}{R_4} \right] V_i$$

During -ve half cycle ,

$$V_o = -\frac{R_5}{R_4} V_i = -A_m V_i$$


$$\Rightarrow \frac{R_5 R_2}{R_3 R_1} - \frac{R_5}{R_4} = \frac{R_5}{R_4}$$

$$\rightarrow \frac{R_5 R_2}{R_3 R_1} = \frac{2 R_5}{R_4}$$

$$\text{Then } R_1 = R_2 = R_4 = R$$


$$R_3 = \frac{R}{2} \quad \text{&} \quad R_5 = A R$$

Then final circuit is :

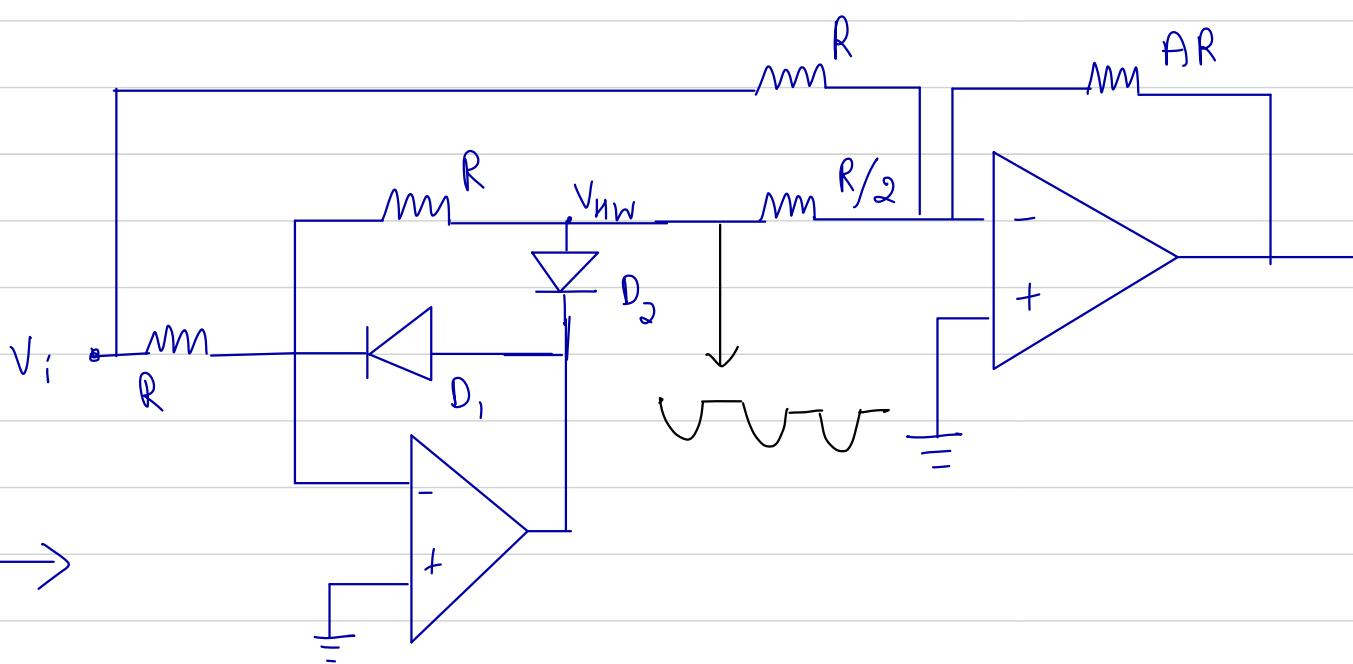

Where A = amplification factor for output.

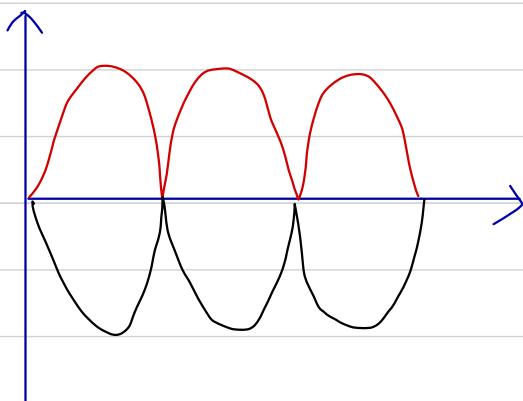
$$\text{Eg: } \text{If } V = V_m \sin \omega t \quad \xi(V_{\text{out}})_{\text{max}} = 2V_m \quad \text{then } A=2$$




Vout in above case


V_{out} with diodes reversed.

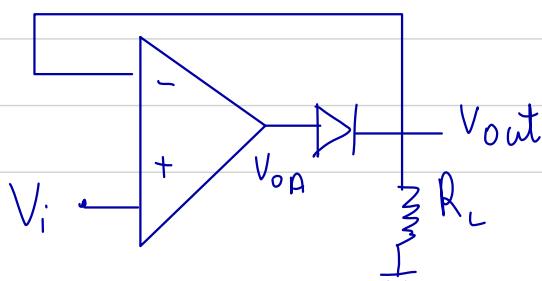Q1) For given circuit draw output waveform if $V_{in} = V_m \sin \omega t$



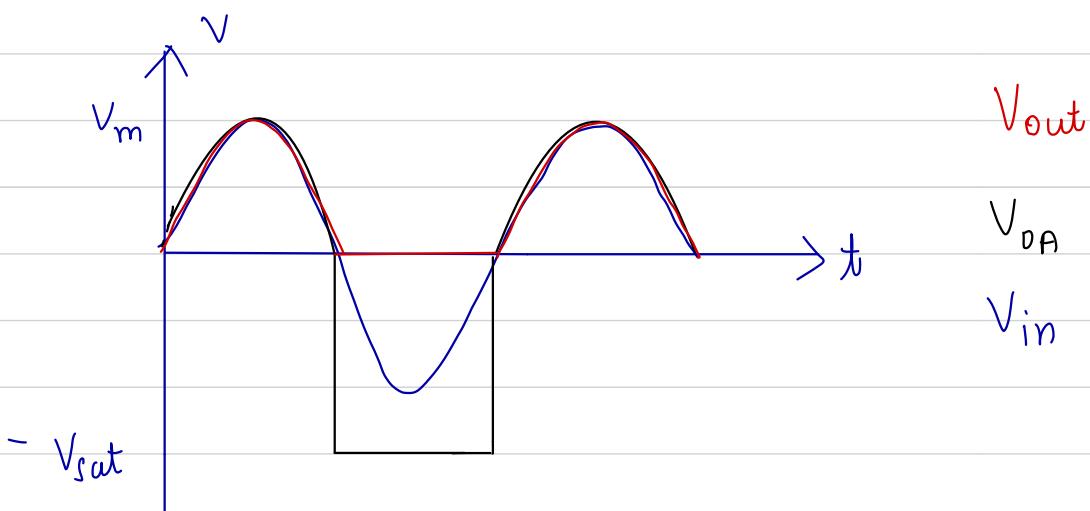

When direction of diode is reversed :

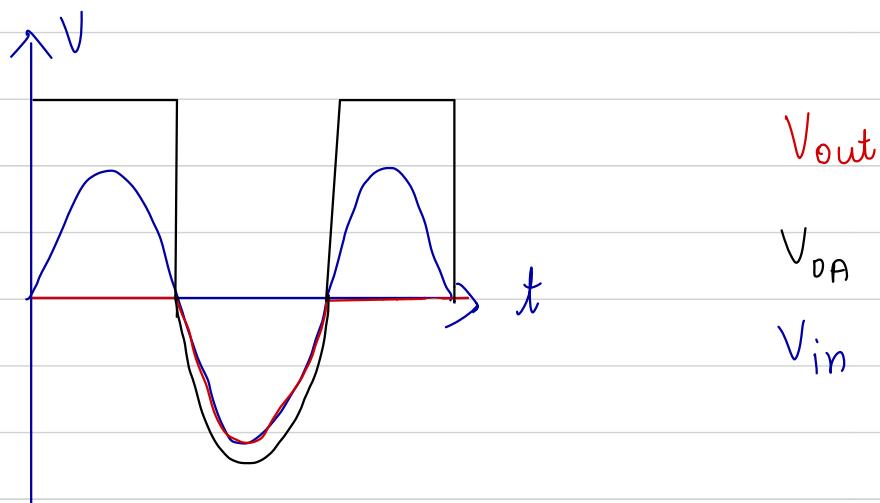

Q2) For given circuit draw output waveform

